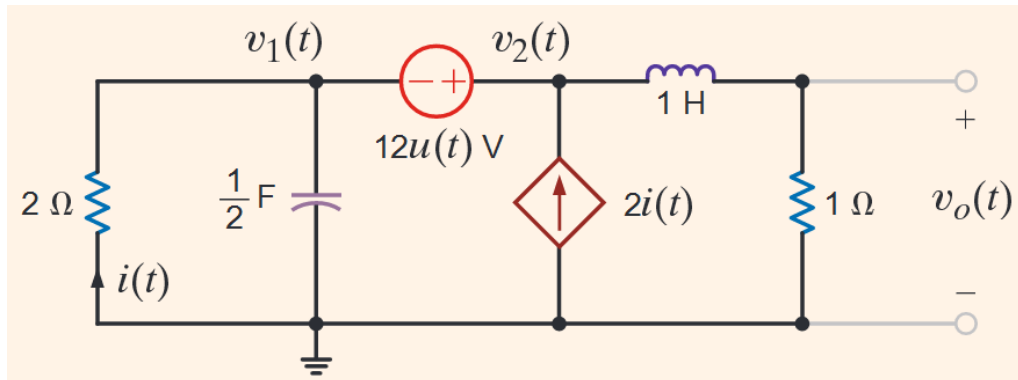



IZMIR KATIP CELEBI UNIVERSITY
DEPARTMENT OF BIOMEDICAL ENGINEERING
FINAL EXAM OF BME203 CIRCUIT THEORY

January 13, 2017


1- Find the output voltage for the following circuit. (30 points)



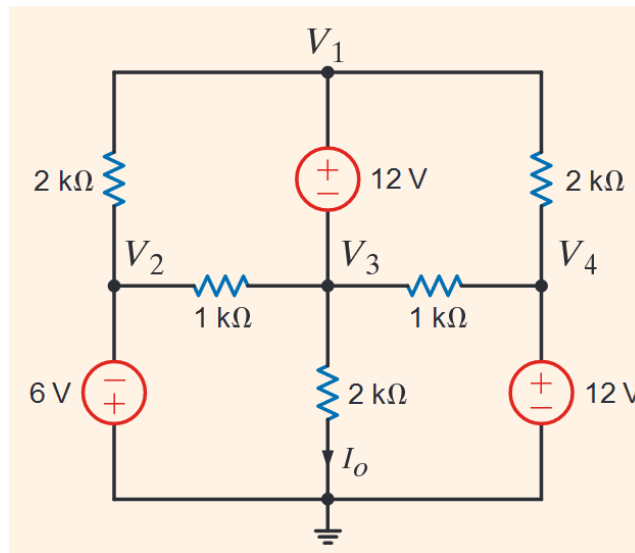2- Find the I_o for the following circuit. (30 points)



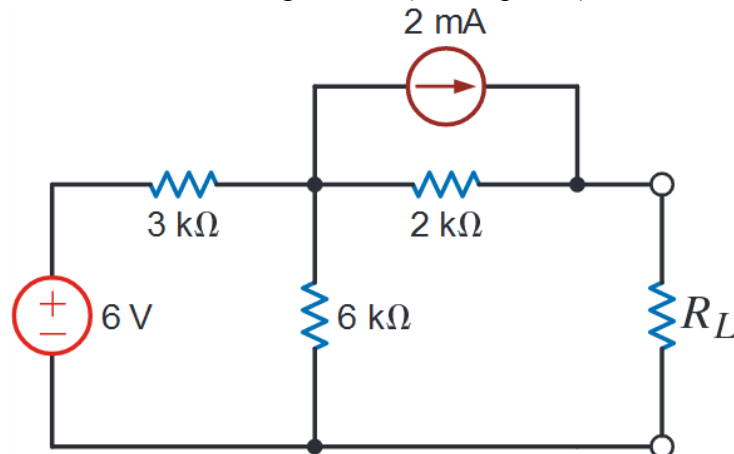3- Find (a) the value of load resistance for maximum power transfer and (b) the maximum power that can be transferred to the load in the following circuit. (2 x 20 points)




P.S. The duration is 105 minutes.

$f(t)$	$F(s)$
$\delta(t)$	1
$u(t)$	$\frac{1}{s}$
e^{-at}	$\frac{1}{s+a}$
t	$\frac{1}{s^2}$
$\frac{t^n}{n!}$	$\frac{1}{s^{n+1}}$
te^{-at}	$\frac{1}{(s+a)^2}$
$\frac{t^n e^{-at}}{n!}$	$\frac{1}{(s+a)^{n+1}}$
$\sin bt$	$\frac{b}{s^2 + b^2}$
$\cos bt$	$\frac{s}{s^2 + b^2}$
$e^{-at} \sin bt$	$\frac{b}{(s+a)^2 + b^2}$
$e^{-at} \cos bt$	$\frac{s+a}{(s+a)^2 + b^2}$


$f(t)$	$F(s)$
$Af(t)$	$AF(s)$
$f_1(t) \pm f_2(t)$	$F_1(s) \pm F_2(s)$
$f(at)$	$\frac{1}{a} F\left(\frac{s}{a}\right), a > 0$
$f(t - t_0)u(t - t_0), t_0 \geq 0$	$e^{-t_0 s} F(s)$
$f(t)u(t - t_0)$	$e^{-t_0 s} \mathcal{L}[f(t + t_0)]$
$e^{-at}f(t)$	$F(s + a)$
$\frac{d^n f(t)}{dt^n}$	$s^n F(s) - s^{n-1}f(0) - s^{n-2}f'(0) \cdots - s^0 f^{(n-1)}(0)$
$tf(t)$	$-\frac{dF(s)}{ds}$
$t^n f(t)$	$(-1)^n \frac{d^n F(s)}{ds^n}$
$\frac{f(t)}{t}$	$\int_s^\infty F(\lambda) d\lambda$
$\int_0^t f(\lambda) d\lambda$	$\frac{1}{s} F(s)$
$\int_0^t f_1(\lambda)f_2(t - \lambda) d\lambda$	$F_1(s)F_2(s)$

① For $t < 0$, to find initial values

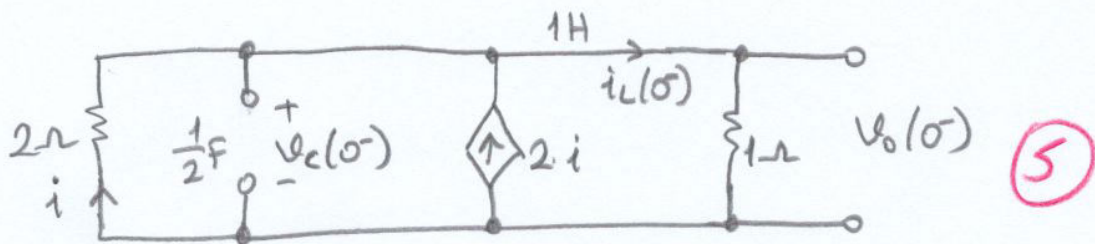

There is no independent source in the circuit.
Hence, $v_c(t^-) = 0$ V and $i_L(t^-) = 0$ A.

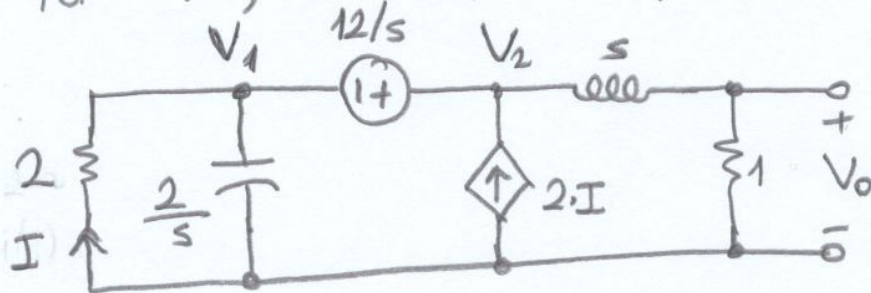For $t \geq 0$, the Laplace equivalent circuit



$$I = -\frac{V_1}{2} \quad V_2 - V_1 = \frac{12}{s} \quad V_o = \frac{V_2}{s+1} \cdot 1$$

$$V_1 = V_2 - \frac{12}{s}$$

Node equation for supernode of V_1 and V_2 :

$$\frac{V_1}{2} + \frac{V_1}{2/s} + (-2 \cdot I) + \frac{V_2}{s+1} = 0$$

$$\frac{V_1}{2} + \frac{s \cdot V_1}{2} - 2 \cdot \left(-\frac{V_1}{2}\right) + \frac{V_2}{s+1} = 0$$

$$V_1 \cdot \left(\frac{1}{2} + \frac{s}{2} + 1\right) + V_2 \cdot \left(\frac{1}{s+1}\right) = 0$$

$$\left(V_2 - \frac{12}{s}\right) \cdot \left(\frac{3+s}{2}\right) + V_2 \cdot \left(\frac{1}{s+1}\right) = 0$$



1
continued

$$V_2 \cdot \left(\frac{s+3}{2} + \frac{1}{s+1} \right) - \frac{12}{s} \cdot \frac{s+3}{2} = 0$$

$$V_2 \cdot \frac{s^2+4s+5}{2 \cdot (s+1)} = \frac{6 \cdot (s+3)}{s}$$

$$V_2 = \frac{12 \cdot (s+1) \cdot (s+3)}{s \cdot (s^2+4s+5)}$$

$$V_0 = \frac{V_2}{s+1} = \frac{12 \cdot (s+3)}{s \cdot (s^2+4s+5)}$$

5

$$V_0 = \frac{12 \cdot (s+3)}{s \cdot ((s+2)^2+1^2)} = \frac{A}{s} + \frac{B \cdot (s+2) + C}{s^2+4s+5}$$

$$12 \cdot (s+3) = A \cdot (s^2+4s+5) + s \cdot (B(s+2) + C)$$

$$12s+36 = A \cdot s^2 + 4A \cdot s + 5A + B \cdot s^2 + 2B \cdot s + C \cdot s$$

$$A+B=0$$

$$4A+2B+C=12$$

$$5A=36 \Rightarrow A = \frac{36}{5} = 7,2$$

$$B = -A = -7,2$$

$$C = 12 - 4A - 2B = -2,4$$

5

$$V_0 = \frac{7,2}{s} - 7,2 \cdot \frac{s+2}{(s+2)^2+1^2} - 2,4 \cdot \frac{1}{(s+2)^2+1^2}$$




1/continued

$$v_o(t) = 7,2 \cdot u(t) - 7,2 \cdot e^{-2t} \cdot \cos t \cdot u(t) - 2,4 \cdot e^{-2t} \cdot \sin t \cdot u(t)$$

$$\textcircled{5} \quad v_o(t) = 7,2 \cdot u(t) + \sqrt{7,2^2 + 2,4^2} \cdot e^{-2t} \cdot \cos\left(t + \tan^{-1}\left(-\frac{-2,4}{-7,2}\right)\right) \cdot u(t)$$
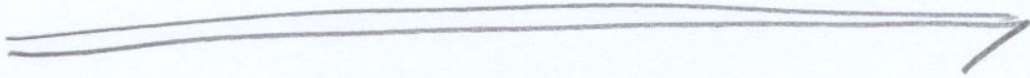
$$v_o(t) = (7,2 + 7,58 \cdot e^{-2t} \cdot \cos(t + 161,57^\circ)) \cdot u(t)$$



$$\textcircled{2} \quad V_2 - 0 = -6 \Rightarrow V_2 = -6V \quad \textcircled{5}$$

$$V_4 - 0 = 12 \Rightarrow V_4 = 12V \quad \textcircled{5}$$

$$V_1 - V_3 = 12 \Rightarrow V_3 = V_1 - 12 \Rightarrow V_1 = V_3 + 12 \quad \textcircled{5}$$

Node equation for supernode of V_1 and V_3 :

$$\textcircled{5} \quad \frac{V_1 - V_2}{2000} + \left(\frac{V_3 - V_2}{1000} + \frac{V_3}{2000} + \frac{V_3 - V_4}{1000} \right) + \frac{V_1 - V_4}{2000} = 0$$

$I_0 = \frac{V_3}{2000}$; so, to find V_3 is enough to solve question.

$$\frac{(V_3 + 12) - (-6)}{2000} + \left(\frac{V_3 - (-6)}{1000} + \frac{V_3}{2000} + \frac{V_3 - (12)}{1000} \right) + \frac{(V_3 + 12) - (12)}{2000} = 0$$

$$\textcircled{5} \quad V_3 + 18 + 2 \cdot (V_3 + 6) + V_3 + 2 \cdot (V_3 - 12) + V_3 = 0$$


$$7 \cdot V_3 + 6 = 0$$

$$V_3 = -\frac{6}{7} V$$

$$\textcircled{5} \quad I_0 = \frac{V_3}{2000} = -\frac{3}{7} \text{ mA}$$

③ Thanks to the maximum power transfer theorem,
 $R_L = R_{Th}$ for transferring maximum power to the load. (10)


②

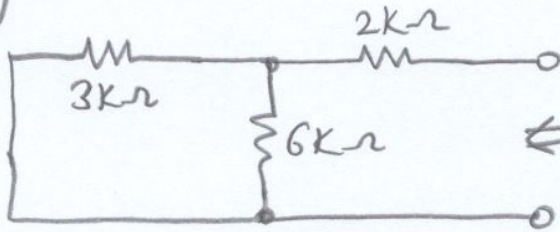

$$\begin{aligned} R_{Th} &= 2k\Omega + 3k\Omega // 6k\Omega \\ &= 2k\Omega + 2k\Omega \\ &= \underline{4k\Omega} \quad (10) \end{aligned}$$

So, $R_L = R_{Th} = \underline{4k\Omega}$

③

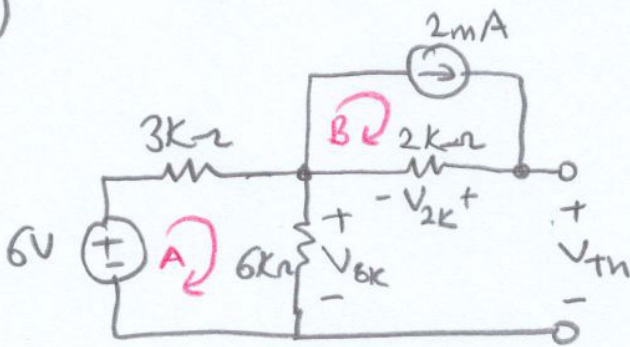


For loop A, $V_{6k} = \frac{6}{3000+6000} \cdot 6000 = 4V$

thanks to voltage-divider rule

For loop B, $V_{2k} = (2mA) \cdot (2k\Omega) = 4V$

thanks to Ohm's Law,

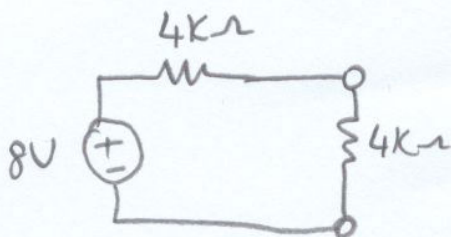$V_{Th} = V_{2k} + V_{6k} = \underline{8V} \quad (10)$



$$P_L = I_L^2 \cdot R_L = \frac{V_L^2}{R_L}$$

$$V_L = \frac{8}{4000+4000} \cdot 4000 = 4V$$

$$P_L = \frac{4^2}{4000} = \underline{4mW} \quad (10)$$