

Student ID: **ANSWER KEY**

Signature:

Name Surname:

IZMIR KATIP CELEBI UNIVERSITY | DEPARTMENT OF BIOMEDICAL ENGINEERING

MID-TERM EXAM OF BME206 ELECTRONIC CIRCUITS

April 22, 2024


Duration: 75 minutes for 4 questions.

Note: There is no extra paper, you should answer your questions on the given question.

Question #1: Draw the circuit defined by the following PSPICE code:

```
* C:\LTspice\examples\Educational\phaseshift.asc
Q1 OUT N004 N005 0 2N2222
R1 N001 OUT 10K
R2 N001 N004 100K
R3 N004 0 10K
R4 N003 0 10K
R5 N002 0 10K
C1 N005 0 1u
C2 N004 N003 .01u
R6 N005 0 1K
C3 N003 N002 .01u
C4 N002 OUT .01u
V1 N001 0 12
.model 2N2222 NPN
.lib C:\LTspice\lib\cmp\standard.bjt
.tran 1u 100m
* This is supplied for educational purposes by LTspice :)
.backanno
.end
```

1

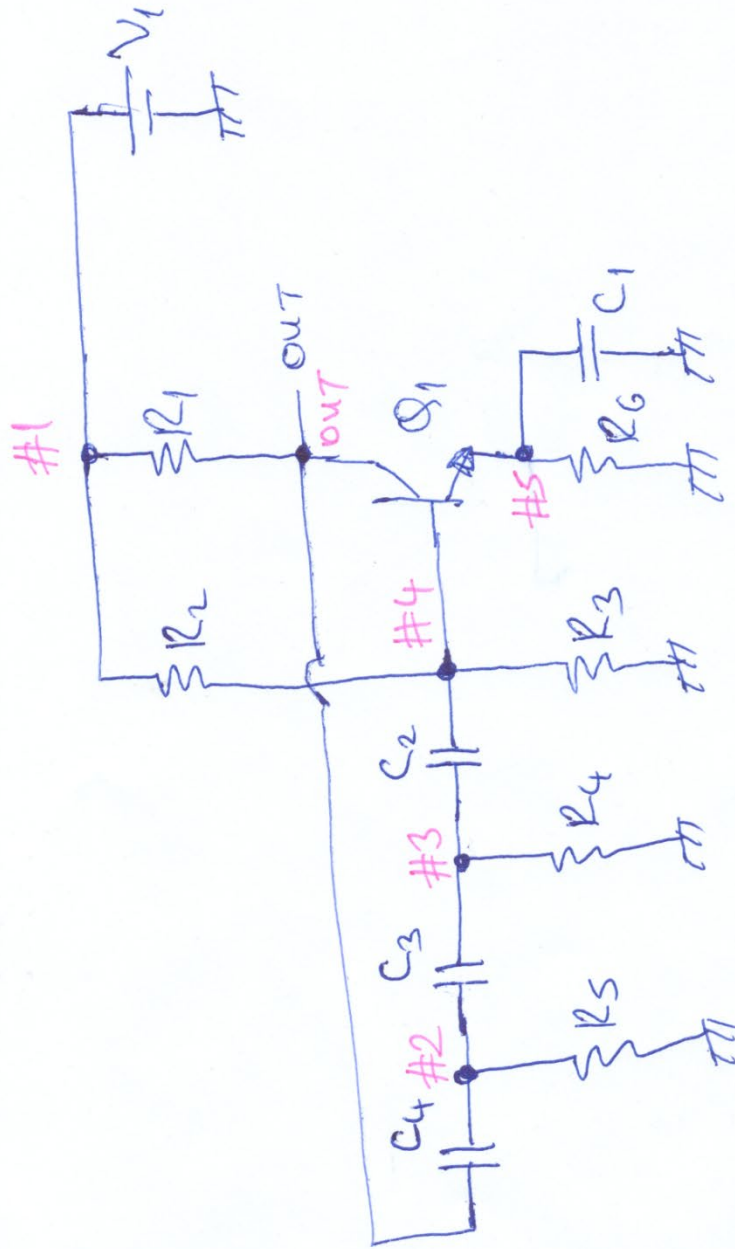

Student ID: **ANSWER KEY**
Name Surname:

Signature:

IZMIR KATIP CELEBI UNIVERSITY | DEPARTMENT OF BIOMEDICAL ENGINEERING


MID-TERM EXAM OF BME206 ELECTRONIC CIRCUITS

April 22, 2024

Duration: 75 minutes for 4 questions.


Note: There is no extra paper, you should answer your questions on the given question.

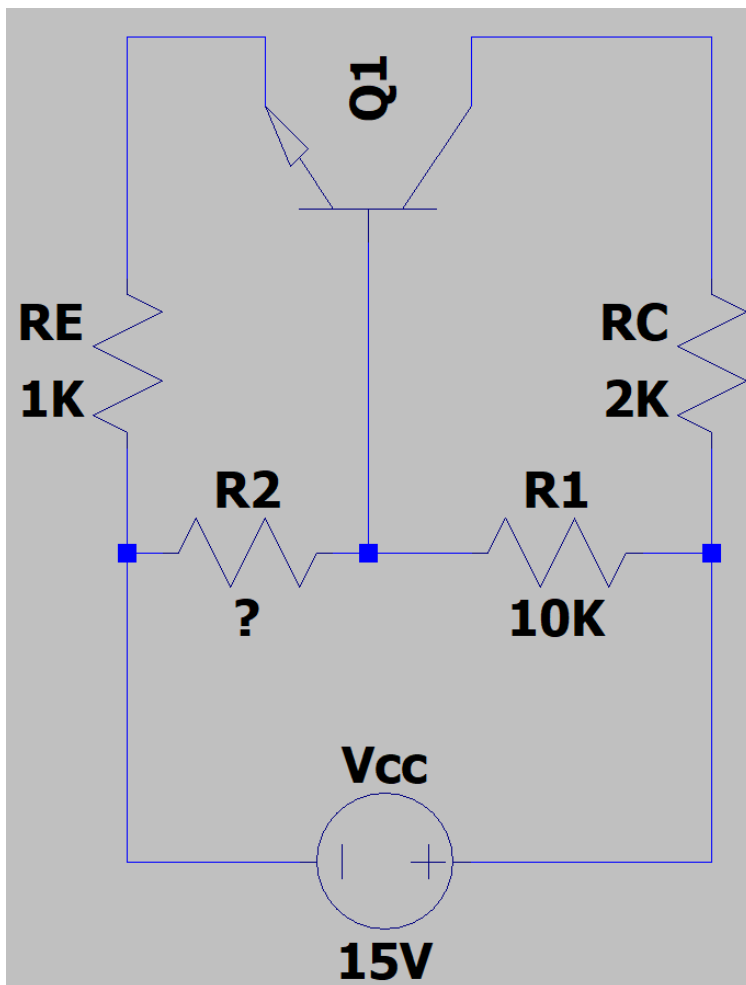Question #2: For the following BJT circuit, the transistor is a Silicon device ($V_{BEQ} = 0.7V$). If the $\beta=99$ and $I_{BQ} = 30 \mu A$, then please calculate the value of R_2 .



Name Surname:


② By redrawing the circuit:

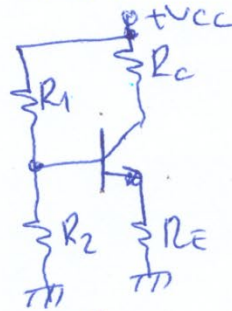

$$R_B = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$\text{and } V_B = \frac{R_2}{R_1 + R_2} \cdot V_{CC}$$

So, it becomes

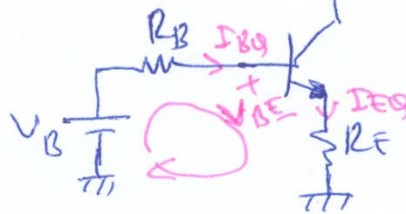

$$-V_B + R_B \cdot I_{BQ} + V_{BE} + R_E \cdot I_{EQ} = 0$$

$$-\frac{R_2}{R_1 + R_2} \cdot V_{CC} + \frac{R_1 \cdot R_2}{R_1 + R_2} \cdot I_{BQ} + V_{BE} + R_E \cdot (\beta + 1) \cdot I_{BQ} = 0$$

$$-\frac{R_2}{10000 + R_2} \cdot 15 + \frac{10000 \cdot R_2}{10000 + R_2} \cdot 30 \cdot 10^{-6} + 0,7 + 1000 \cdot (99 + 1) \cdot 30 \cdot 10^{-6} = 0$$

$$-15 \cdot \frac{R_2}{10000 + R_2} + 0,3 \cdot \frac{R_2}{10000 + R_2} = -0,7 - 3$$

$$-14,7 \cdot \frac{R_2}{10000 + R_2} = -3,7$$

$$\frac{R_2}{10000 + R_2} \approx 0,25 \Rightarrow R_2 = 0,25 \cdot R_2 + 2500$$

$$0,75 \cdot R_2 = 2500$$

$$\underline{\underline{R_2 = 3,3K}}$$


IZMIR KATIP CELEBI UNIVERSITY | DEPARTMENT OF BIOMEDICAL ENGINEERING
MID-TERM EXAM OF BME206 ELECTRONIC CIRCUITS

April 22, 2024

Duration: 75 minutes for 4 questions.

Note: There is no extra paper, you should answer your questions on the given question.

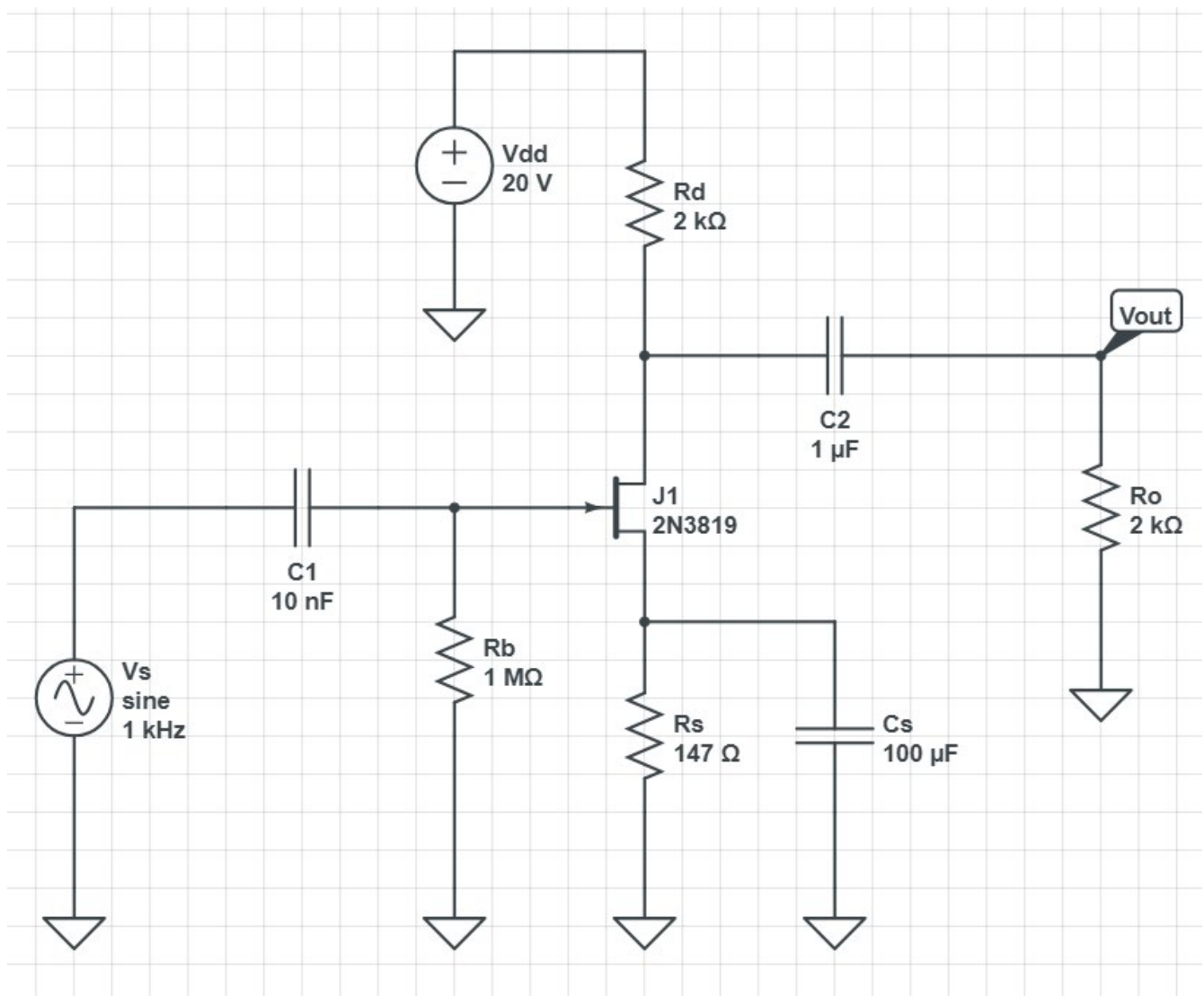Question #3: For the following JFET circuit, if $V_s = 1.5\text{ V}$ then please determine the AC voltage gain formula.




$$I_d = I_{dss} \left(1 - \frac{V_{gs}}{V_p} \right)^2$$

$V_p = -2\text{ V}$ and $I_{dss} = 2\text{ mA}$ and $g_m = 2\text{ mS}$ for 2N3819

3

A.C. equivalent circuit,

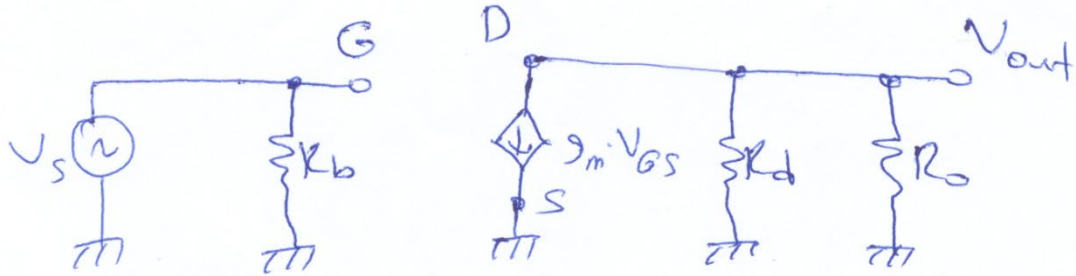

$$A_v = \frac{V_{out}}{V_s}$$

$$V_{GS} = V_s$$

$$V_{out} = -(R_d // R_o) \cdot g_m \cdot V_{GS}$$

$$V_{out} = -\frac{R_d \cdot R_o}{R_d + R_o} \cdot g_m \cdot V_s$$

$$\frac{V_{out}}{V_s} = A_v = -\frac{2000 \cdot 2000}{2000 + 2000} \cdot 2 \cdot 10^{-3} = -2$$

Student ID: **ANSWER KEY**
Name Surname:

Signature:

IZMIR KATIP CELEBI UNIVERSITY | DEPARTMENT OF BIOMEDICAL ENGINEERING


MID-TERM EXAM OF BME206 ELECTRONIC CIRCUITS

April 22, 2024

Duration: 75 minutes for 4 questions.

Note: There is no extra paper, you should answer your questions on the given question.

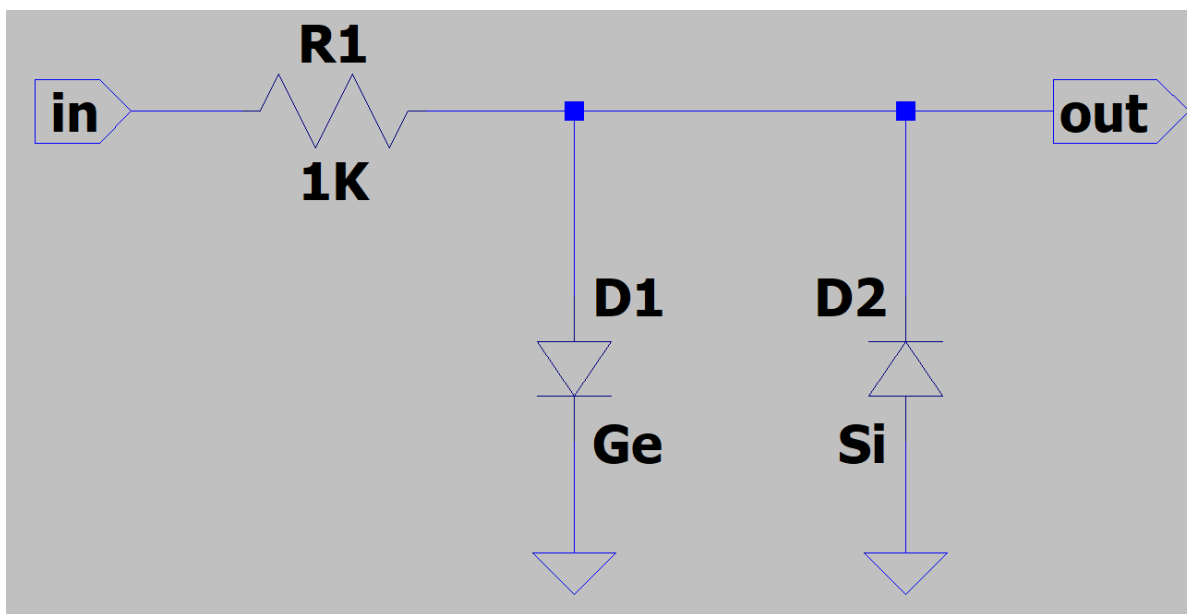Question #4: For the following circuit, please determine the voltage of the out node if the in node is 3 V sine.



Name Surname:

(4)

$$V_{GE} = 0,3 \text{ V}$$

$$V_{Si} = 0,7 \text{ V}$$

if $V_{in} > V_{Ge}$, $V_{out} = V_{Ge}$, (Ge:ON)

if $V_{in} < -V_{Si}$, $V_{out} = -V_{Si}$, (Si:ON)

otherwise, $V_{out} = V_{in}$, (both Ge and Si:OFF)

