# **Electronic Circuits**

Lecture 2.1: Basic Circuit Elements & Laplace (s) Domain Analysis

### **Electrical Quantities**

- Conductors are materials let electricity flow through them easily. Most metals are good conductors.
- Insulators are materials don't carry electricity well. We need insulators to protect people from flowing electricity. Rubber and plastics are good examples.
- Voltage (V) is the force that makes electrons flow. It's a difference in potential energy between two different points in a circuit. It's measured in volts (V).
- Current (I) is the rate of the flow of electrons. It's measured in amperes (amps, A).
- Power (P) indicates instantenous work capacity. It is measured in watts (W) and calculated by V x I.
- Resistance (R), reactance (X), and impedance (Z) are the measures of how a material resists to conduct electricity. A low resistance indicates a good conductor, a high resistance means a good insulator. It is measured in ohms (Ω).



#### Sources (DC versus AC)

- A Source is a device which converts mechanical, chemical, thermal or some other form of energy into electrical energy.
- The source can supply either voltage (V) or current (I) at given certain value (or formula) by giving other one in free form.
- In direct current (DC), the electric charge (current) only flows in one direction. Electric charge in alternating current (AC), on the other hand, changes direction periodically.



#### Sources (Voltage versus Current)

- An ideal voltage source is a two-terminal device whose voltage at any instant of time is constant and is independent of the current drawn from it.
- An ideal current source is a two-terminal circuit element which supplies the same current to any load resistance connected across its terminals
- They have different types depending on whether their values are dependent (or controlled) to the other component's electrical quantities:
  - Independent Voltage Source
  - Voltage-Dependent Voltage Source (VCVS)
  - Current-Dependent Voltage Source (CCVS)
  - Independent Current Source
  - Voltage-Dependent Current Source (VCCS)
  - Current-Dependent Current Source (CCCS)





DC current power supply power supply

**AC current** 

#### Sources (Ideal versus Practical)

- A practical voltage source is represented as an ideal voltage source connected with the small resistance in series.
- A practical current source is represented as an ideal current source connected with the high resistance in parallel.



#### Switches

- A switch changes its status open to close or vice versa at a specific time point.
- If there is no switch given in the circuit, we can assume that there is a switch closed at t=0.
- For this example, these two circuits are same for us. The switch had been opened from t = -∞ to t = 0<sup>-</sup> (just before t = 0) and closed at t = 0.



#### Voltage-Current Relations for R-L-C



 $V = I \times R$  is called Ohm's Law.

#### Resistors in Laplace (s) Domain



#### Capacitors in Laplace (s) Domain



#### Inductors in Laplace (s) Domain



#### Recipe For Laplace Transform Circuit Analysis

- Redraw the circuit (nothing about the Laplace transform changes the types of elements or their interconnections)
- Any voltages or currents with values given are Laplace-transformed using the functional and operational tables.
- Any voltages or currents represented symbolically, using i(t) and v(t), are replaced with the symbols I(s) and V(s).
- All component values are replaced with the corresponding complex impedance, Z(s).
- Use DC circuit analysis techniques to write the s-domain equations and solve them. Check your solutions with initial value theorem (IVT) and final value theorem (FVT).
- Inverse-Laplace transform s-domain solutions to get time-domain solutions. Check your solutions at t=0 and t=∞.

#### Example Analysis in Laplace (s) Domain

Example: There is no initial energy stored in this circuit. Find  $i_1(t)$  and  $i_2(t)$  for t > 0.



Copyright © 2008 Pearson Prentice Hall, Inc.





Copyright © 2008 Paarson Prentice Hall, Inc.

### Example Analysis in Laplace (s) Domain cont'd

$$I_{1}(s) = \frac{40s + 360}{s(s+2)(s+12)}$$

$$= \frac{K_{1}}{s} + \frac{K_{2}}{s+2} + \frac{K_{3}}{s+12}$$

$$\frac{336}{s} + \frac{10s}{11} + \frac{10s}{420} + \frac{10s}{12} + \frac{10s}{480}$$

$$K_{1} = \frac{40s + 360}{(s+2)(s+12)}\Big|_{s=0} = 15; \quad K_{2} = \frac{40s + 360}{s(s+12)}\Big|_{s=-2} = -14; \quad K_{3} = \frac{40s + 360}{s(s+2)}\Big|_{s=-12} = -1$$

$$\therefore \quad I_{1}(s) = \frac{15}{s} + \frac{-14}{s+2} + \frac{-1}{s+12} \quad i_{1}(t) = \pounds^{-1}\Big\{\frac{15}{s} + \frac{-14}{s+2} + \frac{-1}{s+12}\Big\}$$

$$= [15 - 14e^{-2t} - e^{-12t}]u(t) \text{ A}$$
The forced response is  $15u(t) \text{ A};$ 
The natural response is  $[-14e^{-2t} - e^{-12t}]u(t) \text{ A}$ 

#### Example Analysis in Laplace (s) Domain cont'd

$$I_{2}(s) = \frac{168}{s(s+2)(s+12)}$$

$$= \frac{K_{1}}{s} + \frac{K_{2}}{s+2} + \frac{K_{3}}{s+12}$$

$$\frac{336}{s} + \frac{10}{t_{1}} + \frac{42 \Omega}{t_{2}} + \frac{48 \Omega}{t_{2}}$$

$$K_{1} = \frac{168}{(s+2)(s+12)} \Big|_{s=0} = 7; \quad K_{2} = \frac{168}{s(s+12)} \Big|_{s=-2} = -8.4; \quad K_{3} = \frac{168}{s(s+2)} \Big|_{s=-12} = 1.4$$

$$\therefore \quad I_{2}(s) = \frac{7}{s} + \frac{-8.4}{s+2} + \frac{1.4}{s+12}$$

$$i_{2}(t) = \mathcal{L}^{1} \Big\{ \frac{7}{s} + \frac{-8.4}{s+2} + \frac{1.4}{s+12} \Big\}$$

$$= [7 - 8.4e^{-2t} + 1.4e^{-12t}]u(t) \text{ A}$$
The forced response is  $7u(t)$  A;

The natural response is  $[-8.4e^{-2t} - 1.4e^{-12t}]u(t)$  A.

# Example Analysis in Laplace (s) Domain: Initial Value Check

$$I_{1}(s) = \frac{40s + 360}{s^{3} + 14s^{2} + 24s}$$
$$\lim_{t \to 0} i_{1}(t) = \lim_{s \to \infty} sI_{1}(s)$$
$$= \lim_{s \to \infty} \frac{40s^{2} + 360s}{s^{3} + 14s^{2} + 24s}$$
$$= \lim_{1/s \to 0} \frac{(40/s) + (360/s^{2})}{1 + (14/s) + (24/s^{2})}$$
$$= 0 \text{ A(check!)}$$

$$I_{2}(s) = \frac{168}{s^{3} + 14s^{2} + 24s}$$
$$\lim_{t \to \infty} i_{1}(t) = \lim_{s \to \infty} sI_{1}(s)$$
$$= \lim_{s \to \infty} \frac{168s}{s^{3} + 14s^{2} + 24s}$$
$$= \lim_{1/s \to 0} \frac{(168/s^{2})}{1 + (14/s) + (24/s^{2})}$$
$$= 0 \text{ A(check!)}$$

# Example Analysis in Laplace (s) Domain: Final Value Check

$$I_{1}(s) = \frac{40s + 360}{s^{3} + 14s^{2} + 24s}$$
$$\lim_{t \to \infty} i_{1}(t) = \lim_{s \to 0} sI_{1}(s)$$
$$= \lim_{s \to 0} \frac{40s^{2} + 360s}{s^{3} + 14s^{2} + 24s}$$
$$= \lim_{s \to 0} \frac{40s + 360}{s^{2} + 14s + 24}$$
$$= \frac{360}{24} = 15 \text{ A(check!)}$$

$$I_{2}(s) = \frac{168}{s^{3} + 14s^{2} + 24s}$$
$$\lim_{t \to \infty} i_{1}(t) = \lim_{s \to 0} sI_{1}(s)$$
$$= \lim_{s \to 0} \frac{168s}{s^{3} + 14s^{2} + 24s}$$
$$= \lim_{s \to 0} \frac{168}{s^{2} + 14s + 24}$$
$$= \frac{168}{24} = 7 \text{ A(check!)}$$

#### Example Analysis in Laplace (s) Domain: t=0 Check

At t = 0, the circuit has no initial stored energy, so  $i_1(0) = 0$ and  $i_2(0) = 0$ . Now check the equations:

$$i_1(0) = (15 - 14 - 1)(1) = 0$$
  
 $i_2(0) = (7 - 8.4 + 1.4)(1) = 0$ 

#### Example Analysis in Laplace (s) Domain: $t=\infty$ Check

$$i_{1}(t) = (15 - 14e^{-2t} - e^{-12t})u(t)A \implies i_{1}(\infty) = 15 - 0 - 0 = 15A$$
$$i_{2}(t) = (7 - 8.4e^{-2t} + 1.4e^{-12t})u(t)A \implies i_{2}(\infty) = 7 - 0 - 0 = 7A$$

Draw the circuit for  $t = \infty$  and check these solutions.



#### LTS: Left To Students (Not homework, try yourself)

The switch in the circuit shown has been in position a for a long time. At t = 0, the switch is thrown to position b.

- a) Find  $I, V_1$ , and  $V_2$  as rational functions of s.
- b) Find the time-domain expressions for i,  $v_1$ , and  $v_2$ .

Answer: (a) I = 0.02/(s + 1250),  $V_1 = 80/(s + 1250),$  $V_2 = 20/(s + 1250);$ 

(b) 
$$i = 20e^{-1250t}u(t)$$
 mA,  
 $v_1 = 80e^{-1250t}u(t)$  V,  
 $v_2 = 20e^{-1250t}u(t)$  V.





# Thanks for listening ③

YALÇIN İŞLER Assoc. Prof.