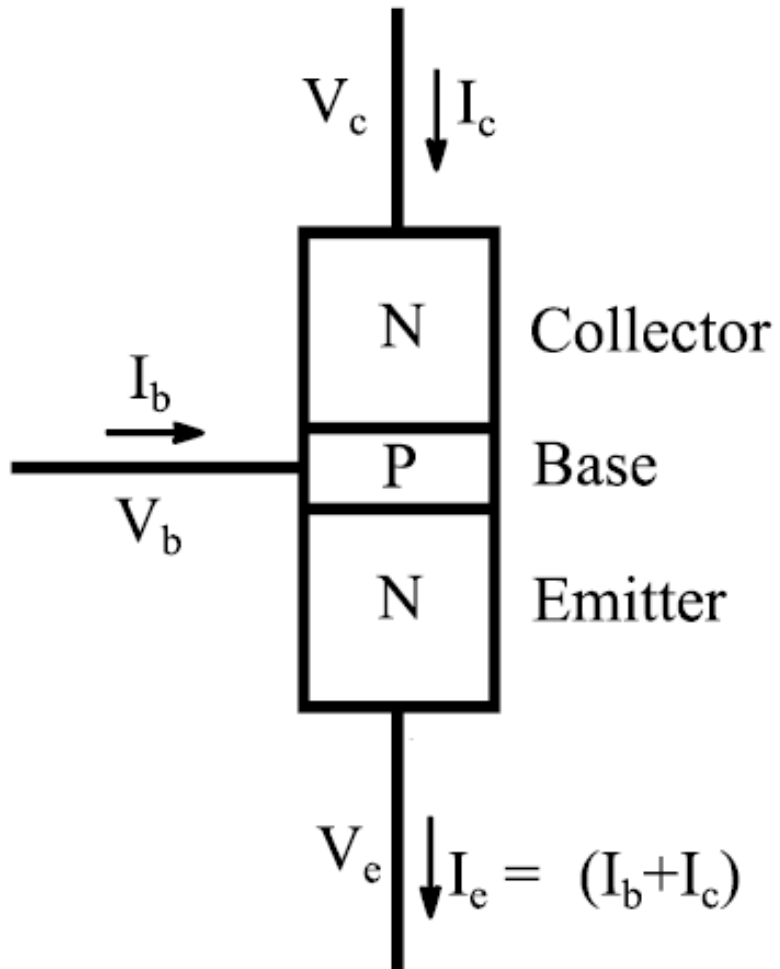




Electronic Circuits

Lecture 4.1: Bipolar Junction Transistor (BJTs)

NPN-Type BJT






$V_{be} \sim + 0.7V$ (Silicon)


$V_{be} \sim + 0.3V$ (Germanium)

$$I_e = \beta I_b$$

$$r_{e,ac} = \frac{26mV}{I_{e,dc}}$$

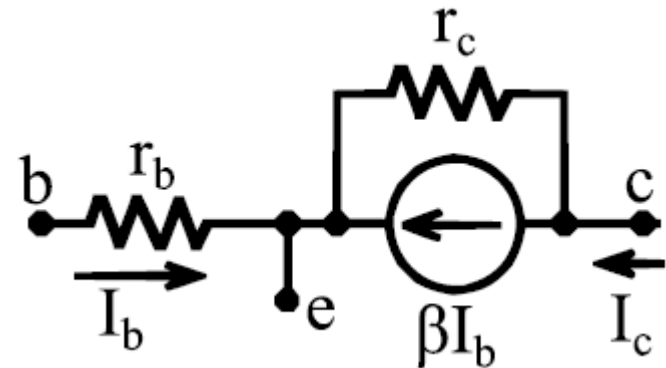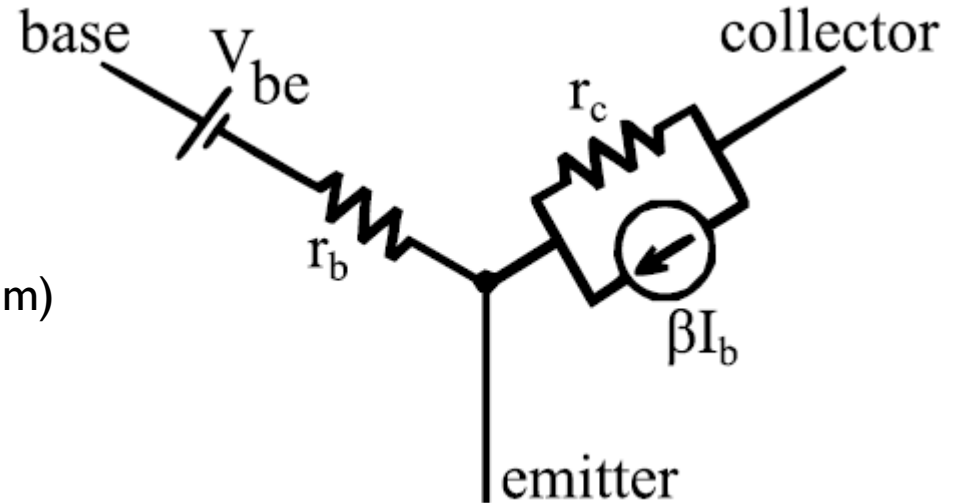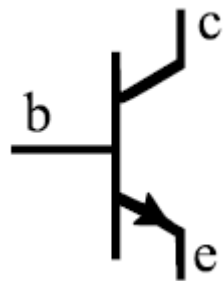

PNP-Type BJT



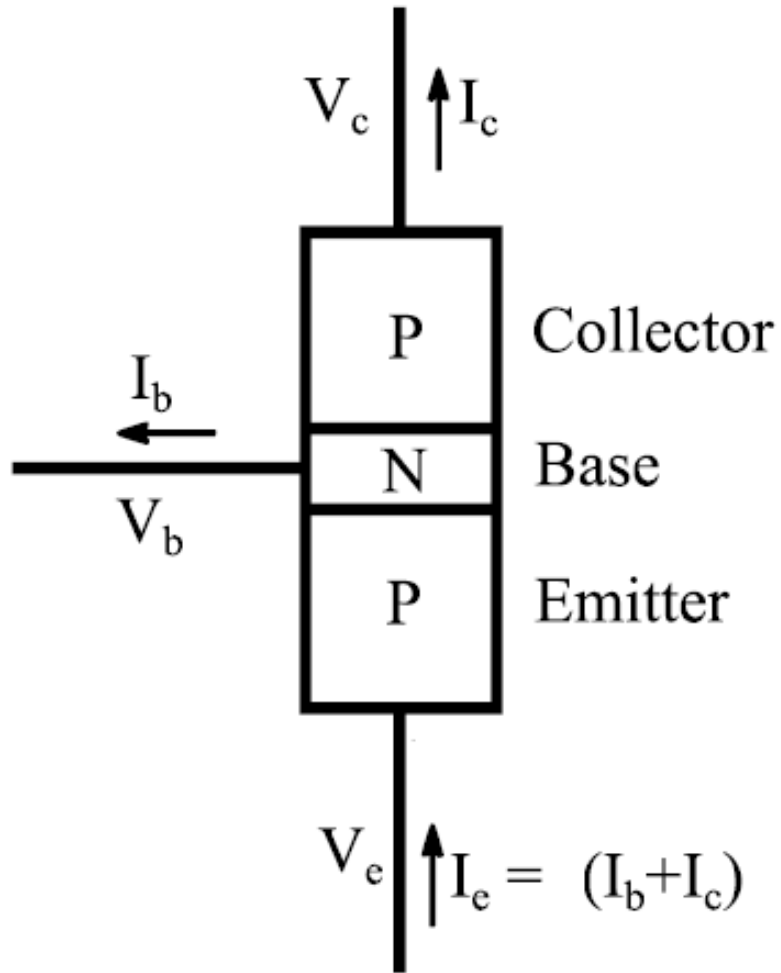


$V_{be} \sim + 0.7 \text{ V}$ (Silicon)


$V_{be} \sim + 0.3 \text{ V}$ (Germanium)

$$I_e = \beta I_b$$


$$r_{e,ac} = \frac{26 \text{ mV}}{I_{e,dc}}$$

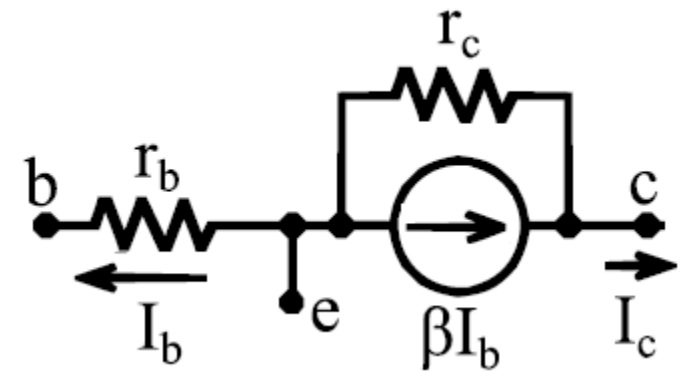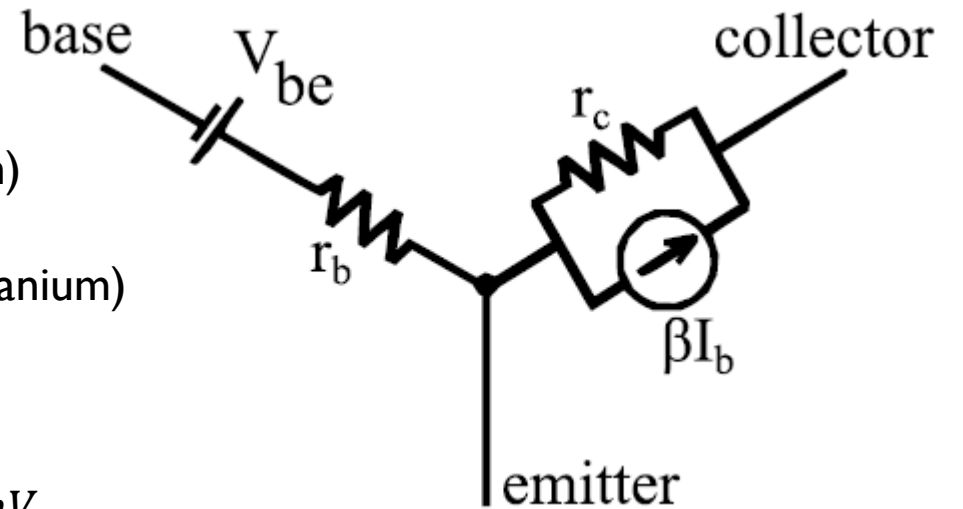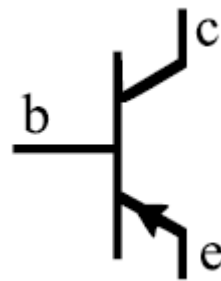


BJT V-I Characteristics

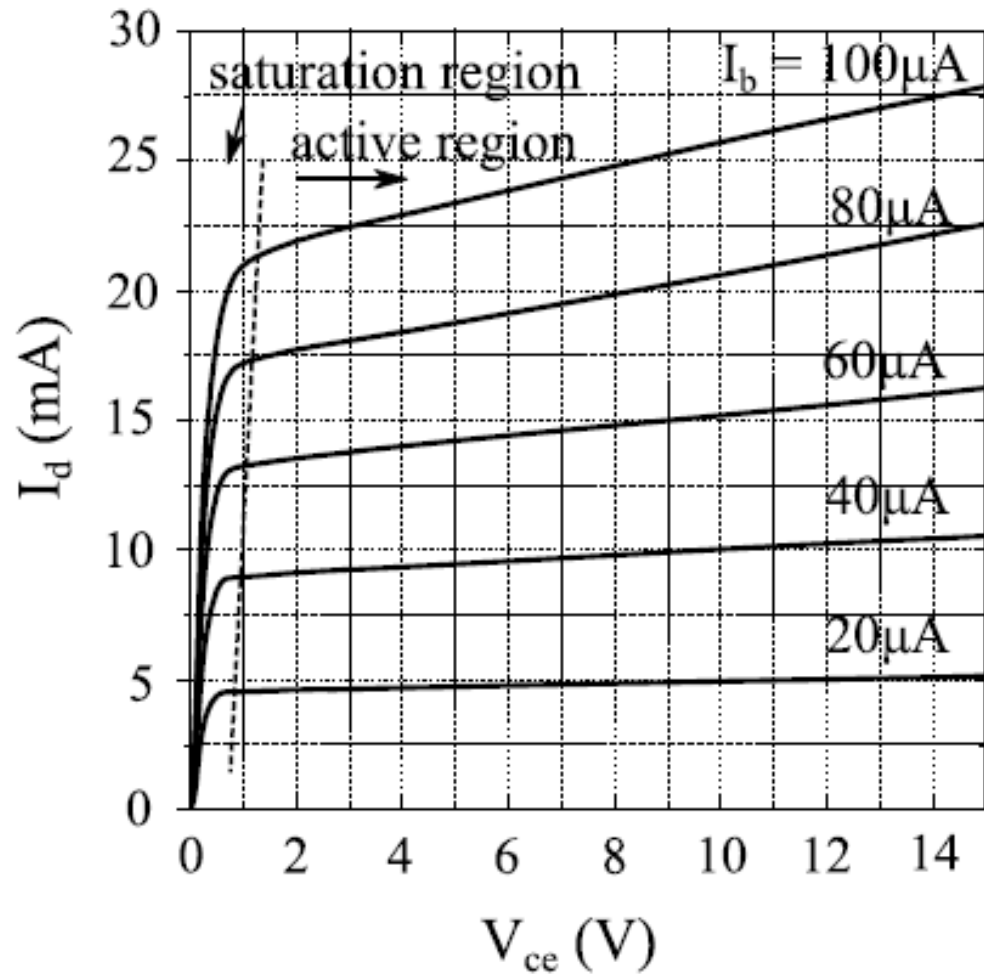

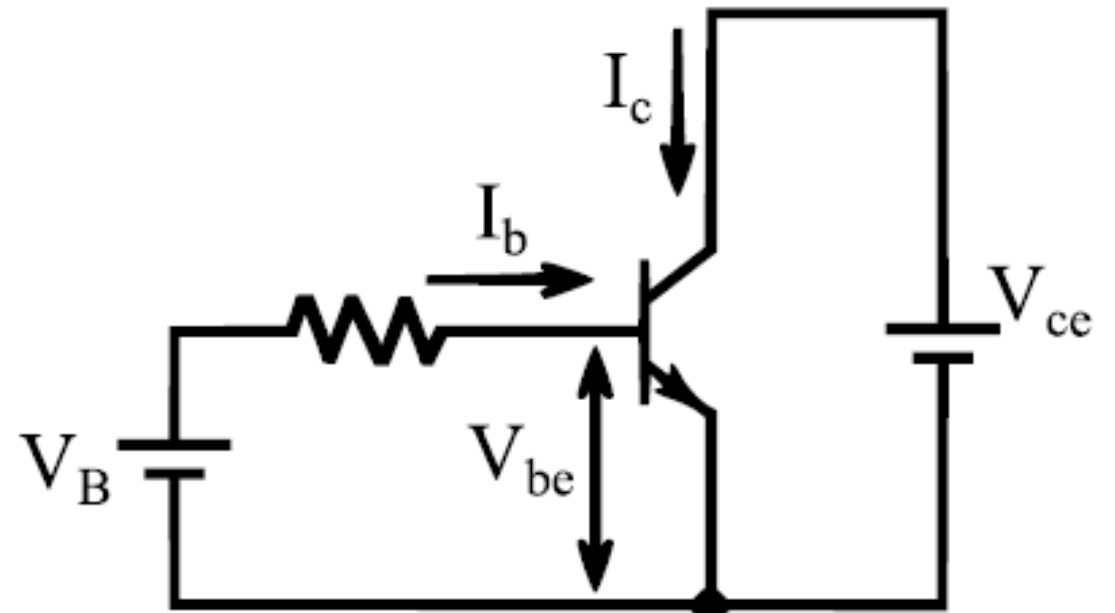
For PNP, all the voltages and currents are reversed 😊



BJT Analysis Example #1

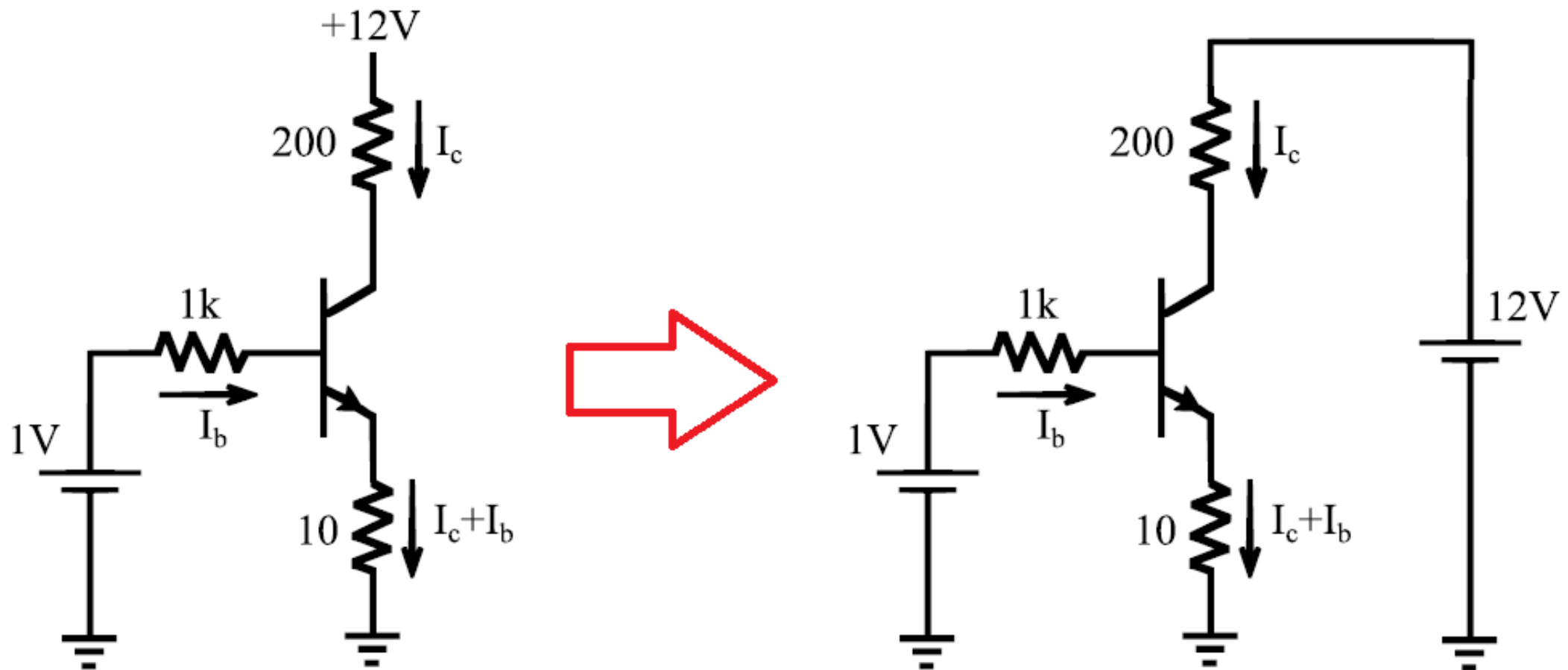

BJT Analysis Example #1: DC Analysis

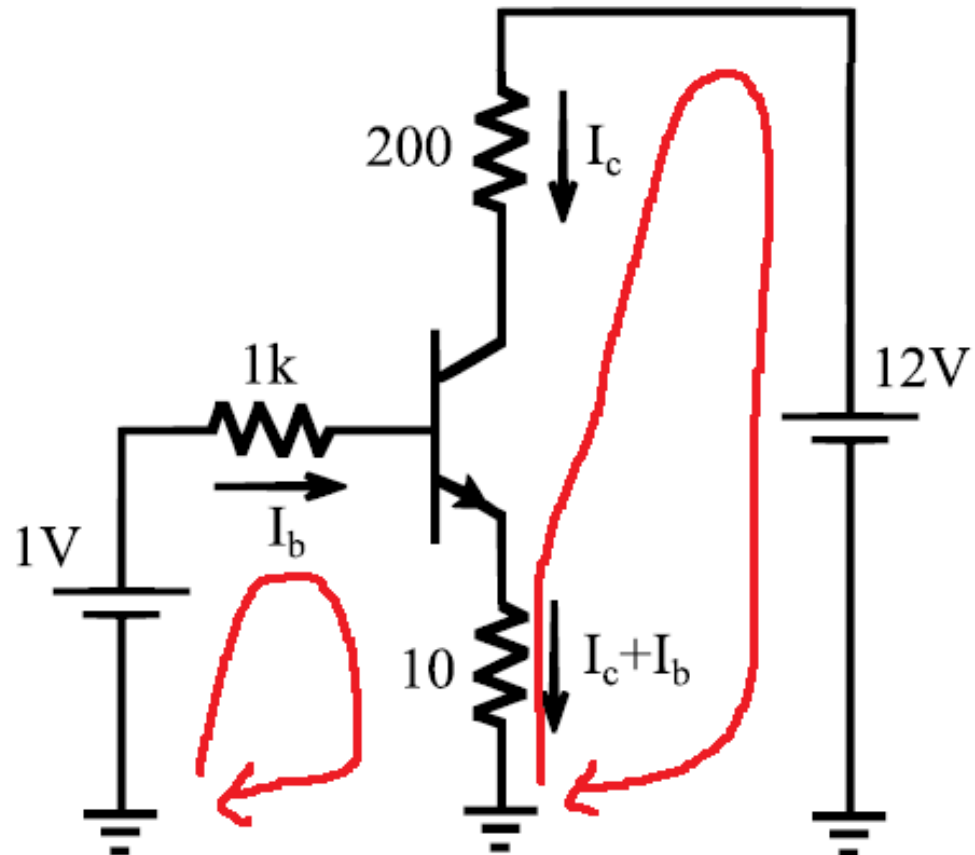

$$-1 + 1000 * I_b + V_{be} + 10 * (I_b + I_c) = 0$$

$$-10 * (I_b + I_c) - V_{ce} - 200 * I_c + 12 = 0$$

$$I_c = \beta * I_b$$

From the catalogue, for example,

$$V_{be} \sim 0.7 \text{ V}$$


$$\beta = 200$$

$$-1 + 1000 * I_b + 0.7 + 10 * (\beta + 1) * I_b = 0$$


$$-10 * (\beta + 1) * I_b - V_{ce} - 200 * \beta * I_b + 12 = 0$$

We can find I_b , I_c , I_e , V_c , and in general, V_c is the output point.

BJT Analysis Example #2: DC Analysis

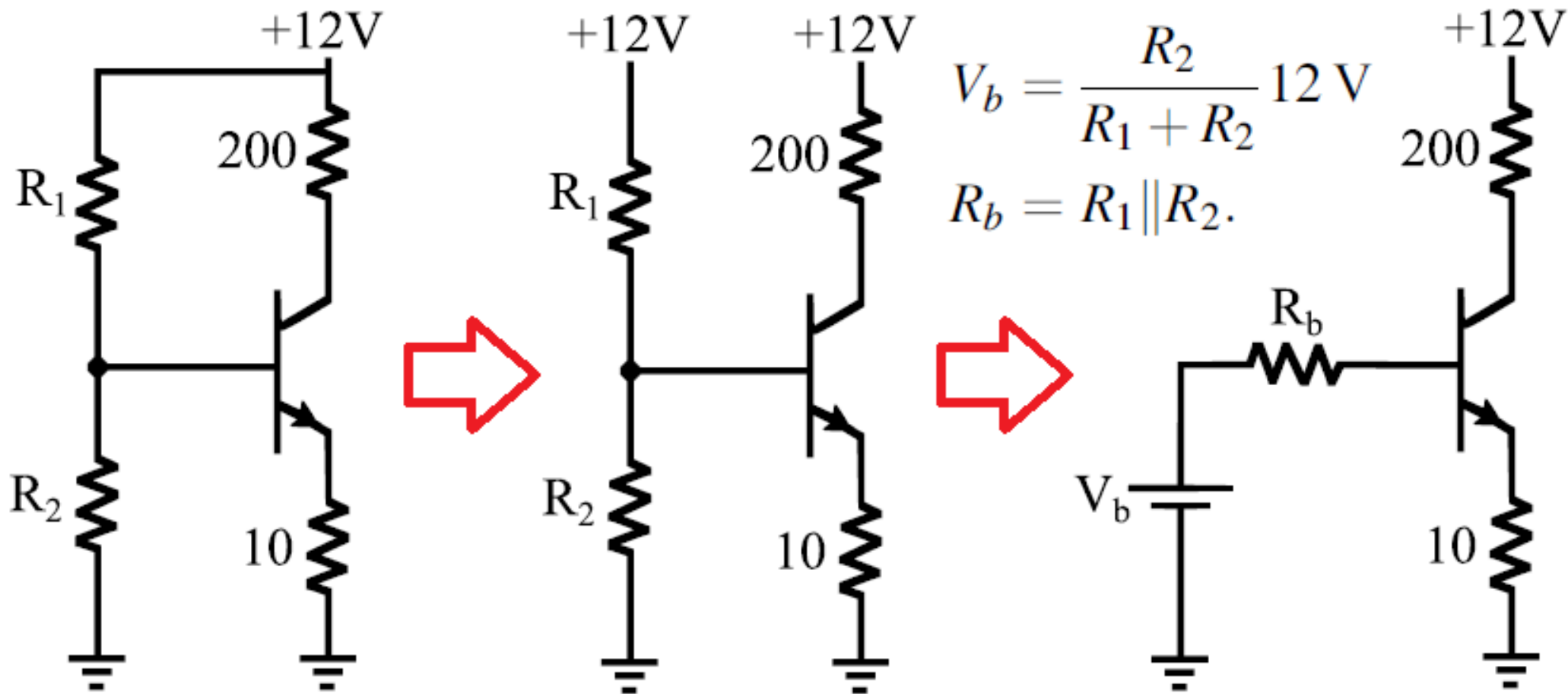

BJT Analysis Example #3: DC Analysis

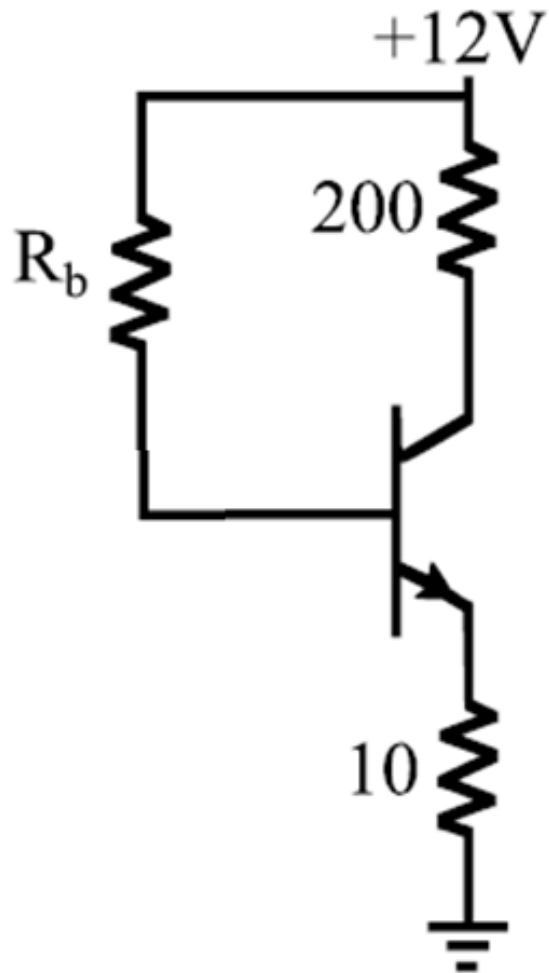

$$-12 + R_b * I_b + V_{be} + 10 * (I_b + I_c) = 0$$

$$-10 * (I_b + I_c) - V_{ce} - 200 * I_c + 12 = 0$$

$$I_c = \beta * I_b$$

From the catalogue, for example,

$$V_{be} \sim 0.7 \text{ V}$$


$$\beta = 200$$

$$-12 + R_b * I_b + 0.7 + 10 * (\beta + 1) * I_b = 0$$


$$-10 * (\beta + 1) * I_b - V_{ce} - 200 * \beta * I_b + 12 = 0$$

We can find I_b, I_c, I_e, V_c , and in general, V_c is the output point.


Basic BJT Amplifiers

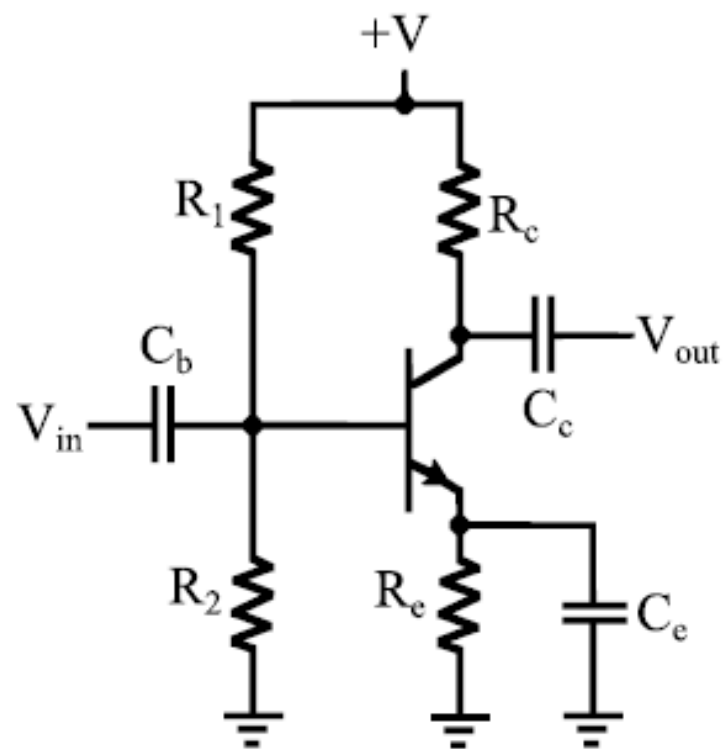

Common Emitter


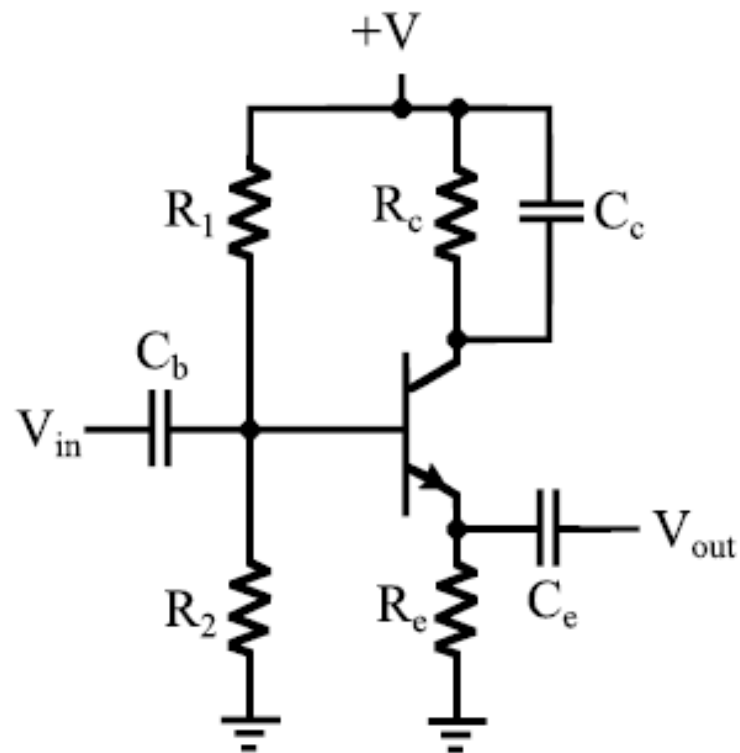


Common Collector
(Emitter Follower)

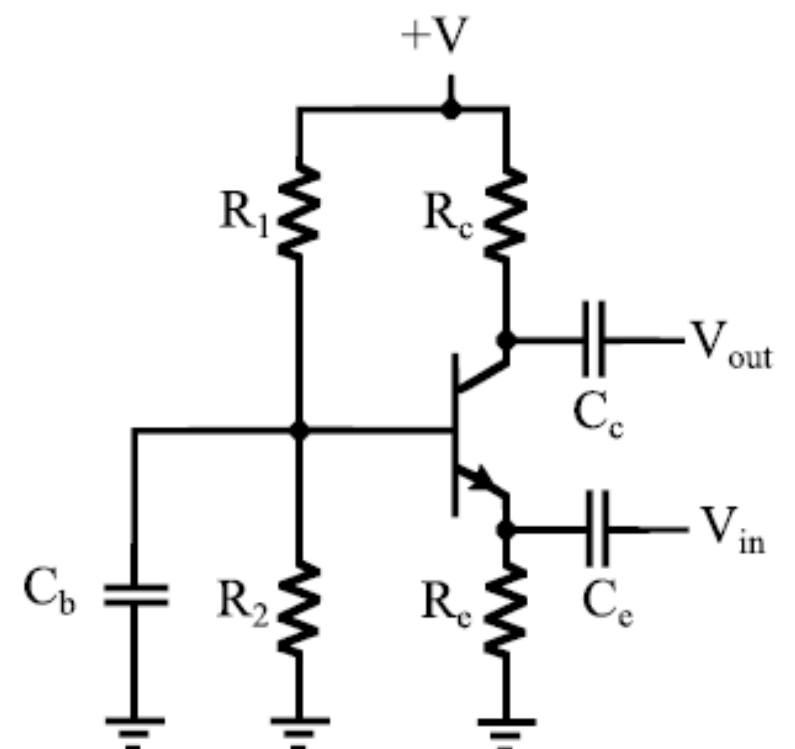

Common Base

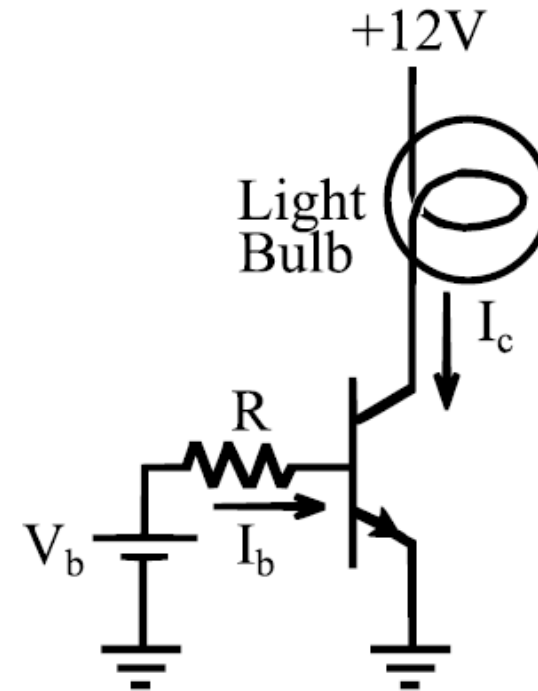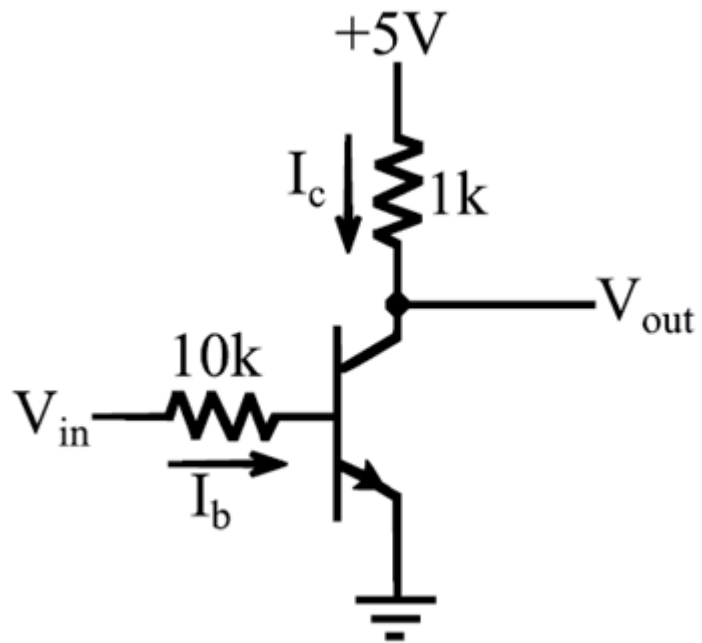Using the Saturation Region (ON / OFF Switching)





Thanks for
listening 😊

YALÇIN İŞLER

Assoc. Prof.