


Electronic Circuits

Lecture 4.2: Analysis of Common-Emitter Configuration BJT Amplifier

Amplifier Analysis

- DC Analysis
 - $C \rightarrow$ open, $L \rightarrow$ short, find r_e that is one of AC equivalent circuit parameters.
- AC Analysis (Mid-Frequency Analysis)
 - $C_s \rightarrow$ short, $L_s \rightarrow$ open, DC sources eliminated, find A_v .
- AC Analysis (Low-Frequency Analysis)
 - DC sources eliminated, C_s and L_s are NOT eliminated, find f_c lower corner frequencies for HPF.
- AC Analysis (High-Frequency Analysis)
 - DC sources eliminated, C_s and L_s are eliminated, but new C_s are added, find f_c higher corner frequencies for LPF.
- Warning: This list possibly doesn't fit to Electronics-based department lectures.


Common-Emitter Amplifier: Circuit

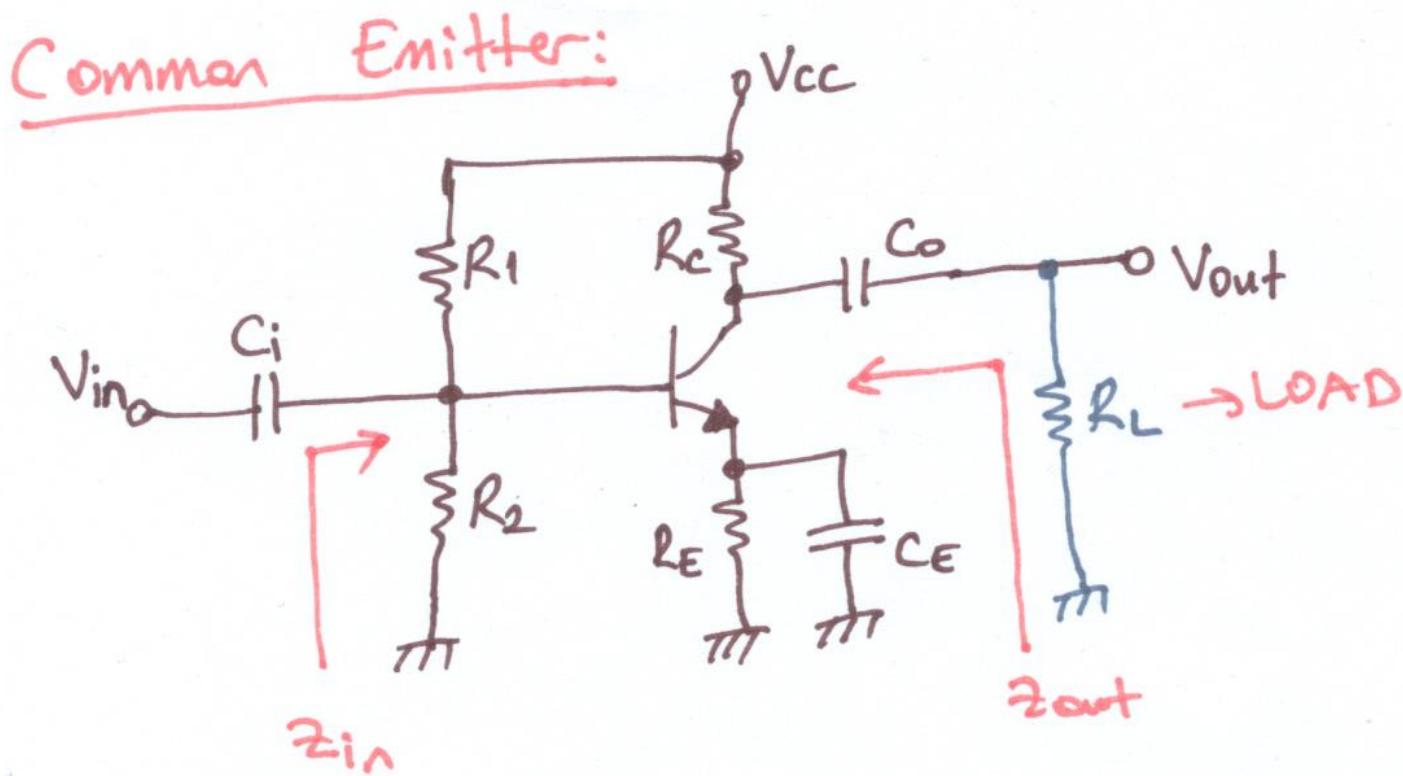

$$A_v = \frac{V_{out}}{V_{in}} \quad (\text{Voltage gain})$$

Common-Emitter Amplifier: DC Analysis (1)

#1: DC Analysis:

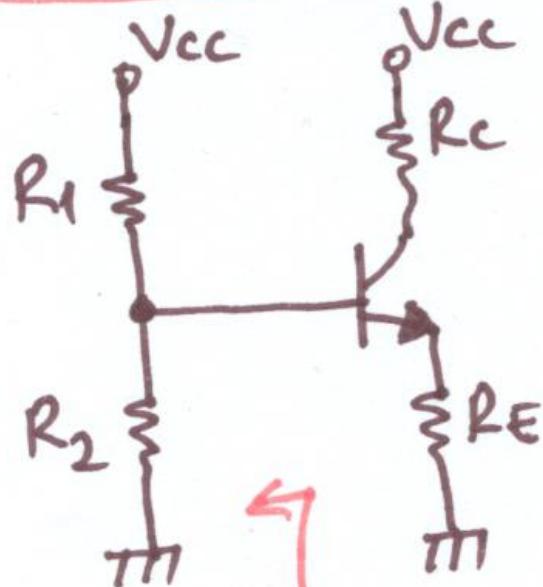

Thevenin
equivalent?

To determine DC operating point.


- All capacitors are open circuit.
- All inductors are short circuit.
- The main aim is to determine r_e !
- Other goals are I_{BQ} , I_{CQ} , I_{EQ} , V_{CEQ} , V_{CQ} .

$$I_E = I_B + I_C$$

$$I_C = \beta \cdot I_B$$

$$r_e = \frac{26 \text{ mV}}{I_{EQ} \text{ mA}}$$

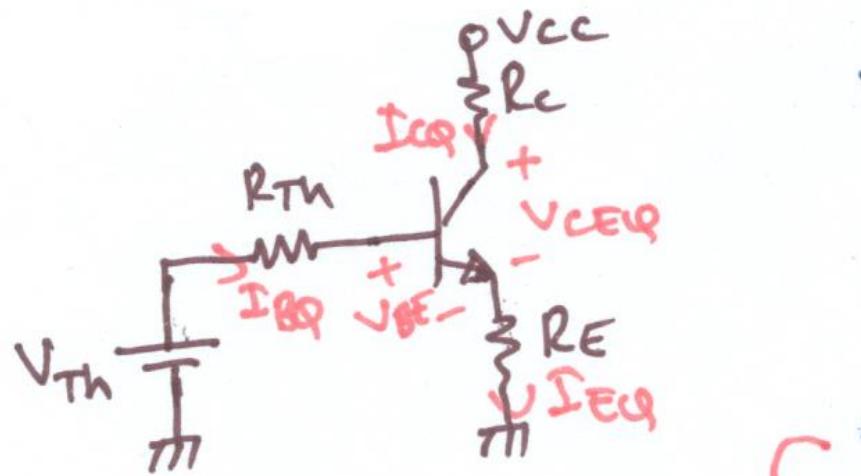Common-Emitter Amplifier: DC Analysis (2)



$$V_{Th} = \frac{R_2}{R_1 + R_2} \cdot V_{CC}$$

$$R_{Th} = R_1 // R_2 = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$-V_{Th} + R_{Th} \cdot I_{BQ} + V_{BE} + R_E \cdot I_{EQ} = 0$$

$$-R_E \cdot I_{EQ} - V_{CEQ} - R_C \cdot I_{CQ} + V_{CC} = 0$$

Find I_{BQ}

Find V_{CEQ}

Find I_{CQ}

Find I_{EQ}

Find R_E

$$I_{CQ} = \beta \cdot I_{BQ}$$

$$I_{EQ} = I_{CQ} + I_{BQ} = (\beta + 1) \cdot I_{BQ}$$

$$r_e = \frac{26 \text{ mV}}{I_{EQ} \text{ mA}} \Omega$$

Common-Emitter Amplifier: AC Analysis (1)



#2: AC Analysis:

(Mid-Frequency Analysis)

To determine desired AC behavior.

- All capacitors are short circuit.
- All inductors are open circuit.
- The aim is to determine A_v , Z_{in} , Z_{out} !
- DC sources are eliminated by voltages are short circuit and currents are open circuit.
- We can use small-signal equivalent BJT model.
- r_e is from DC analysis!

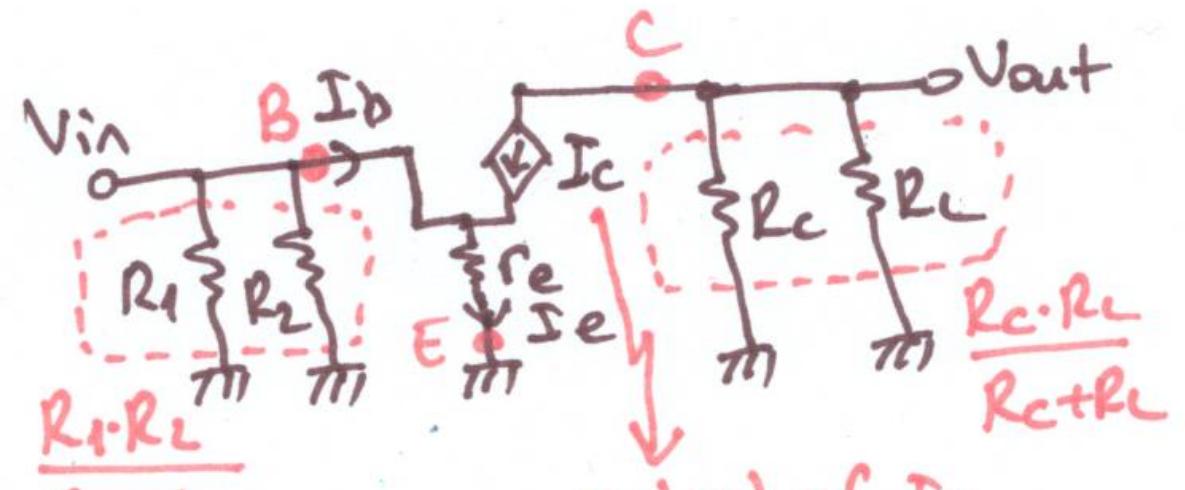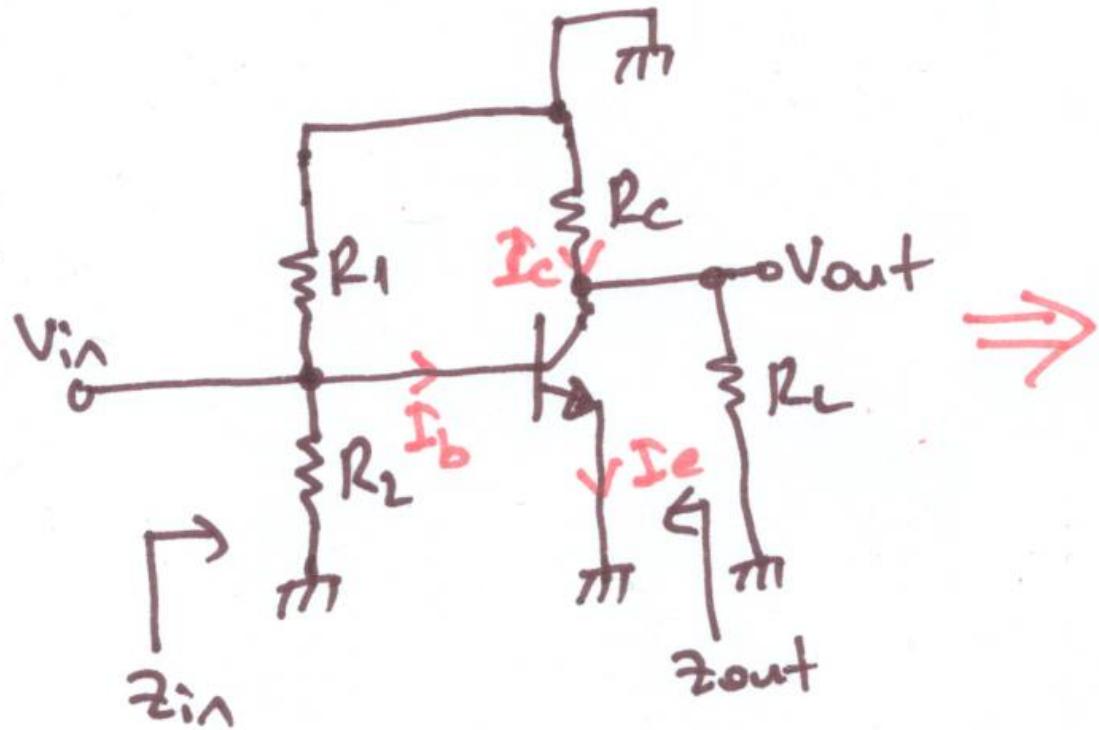Common-Emitter Amplifier: AC Analysis (2)



instead of I_c ,
 $\beta \cdot I_b$ preferred!

Common-Emitter Amplifier: AC Analysis (3)

$$V_{in} = r_e \cdot I_e$$

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_c \cdot R_L}{(R_c + R_L) \cdot r_e}$$

$$V_{out} = \frac{R_c \cdot R_L}{R_c + R_L} \cdot (-I_c)$$

$$Z_{in} = R_1 \parallel R_2 \parallel ((\beta+1) \cdot r_e)$$

The r_e is on the E side, so its effect on the B side is amplified by $(\beta+1)$.


$$Z_{out} = R_c$$

Since current source has resistance of ∞ and R_L is the load not the part of the amplifier itself.

Common-Emitter Amplifier: Low-Frequency Analysis (1)

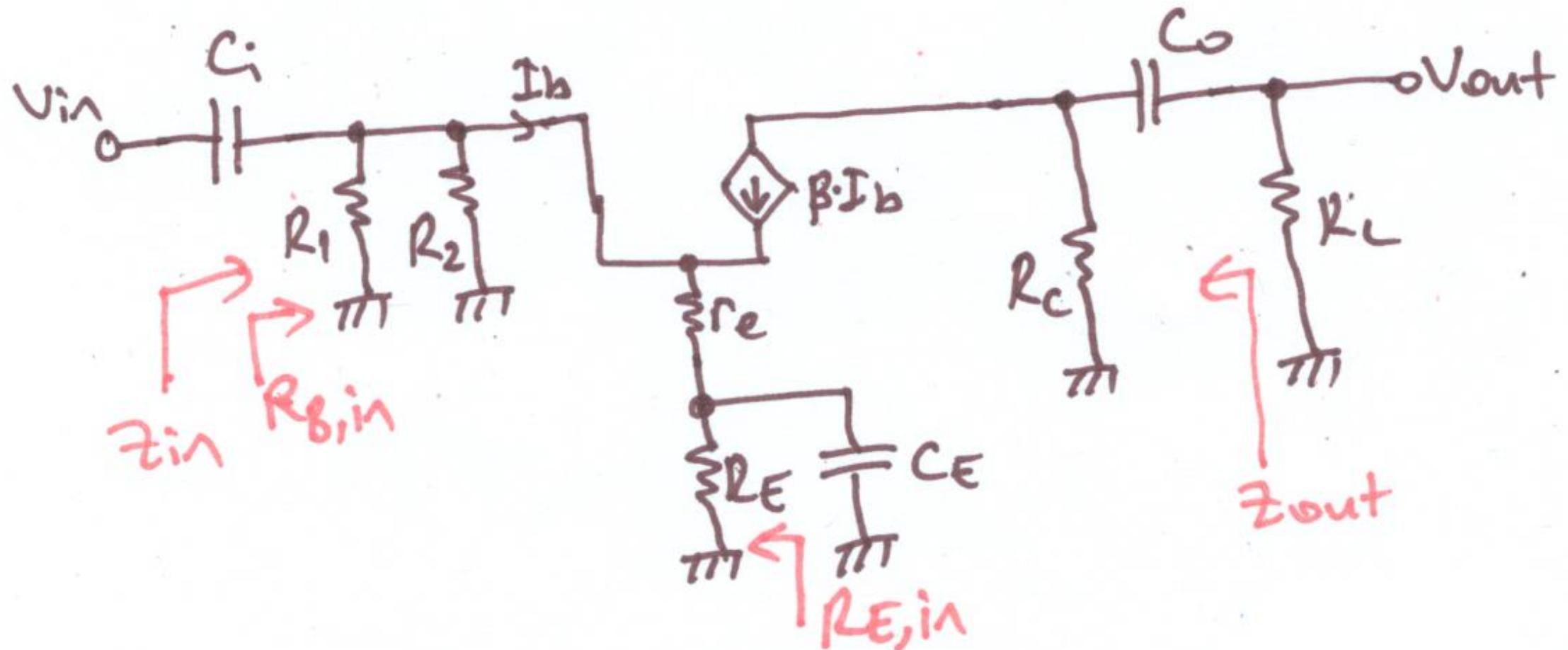- #3: LOW-FREQUENCY ANALYSIS: - AC analysis, too.
- But frequency is not enough high to make capacitors short- and inductors open-circuit.
 - Sources are eliminated, too.
 - We can use the model again.
 - We interested in local R-C sub-circuits!

Common-Emitter Amplifier: Low-Frequency Analysis (2)



Common-Emitter Amplifier: Low-Frequency Analysis (3)


$$f_{C1} = \frac{1}{2\pi \cdot (R_C + R_L) \cdot C_0}$$

$$f_{C2} = \frac{1}{2\pi \cdot R_{B,in} \cdot C_i}$$

$$R_{B,in} = R_{Th} \parallel ((\beta+1) \cdot r_e)$$

$$f_{C3} = \frac{1}{2\pi \cdot R_{E,in} \cdot C_E}$$

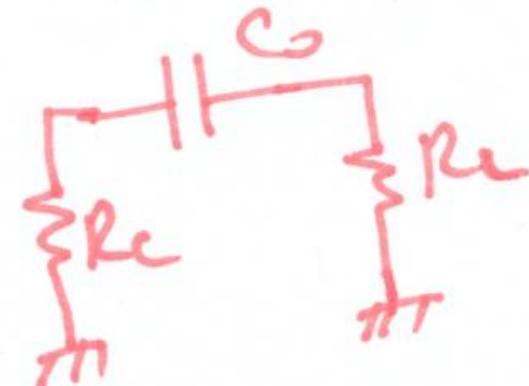
$$R_{E,in} = R_E \parallel (r_e + \frac{R_{Th}}{\beta+1})$$



Common-Emitter Amplifier: Low-Frequency Analysis (4)

- There are some assumptions to simplify. But the more accurate result can be found via s-domain analysis.


If $f_{c2} < f_{c1} < f_{c3}$,

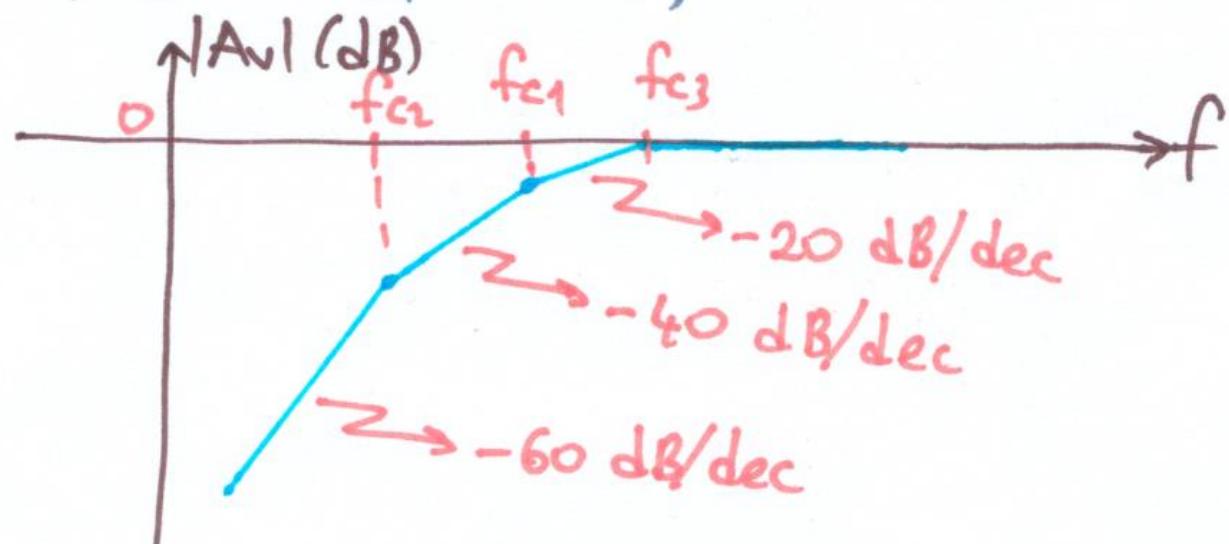

Common-Emitter Amplifier: High-Frequency Analysis (1)

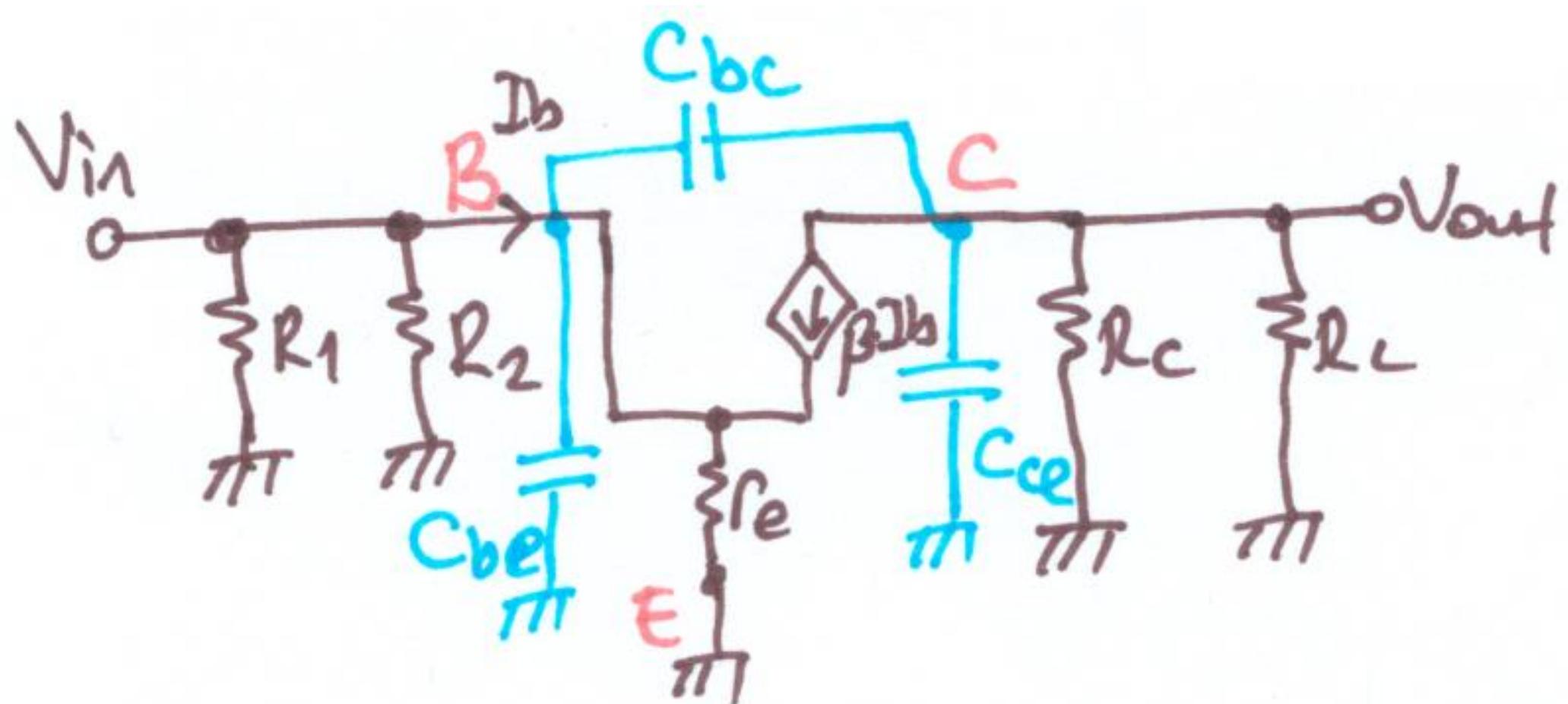- #4: High-Frequency Analysis: - AC analysis, too.
- In fact β (or h_{fe}) is the function of frequency!
 - All capacitors are short-circuit.
 - All inductors are open-circuit.
 - All DC sources are eliminated.
 - But we have new capacitors between BJT leads: C_{be}, C_{bc}, C_{ce}
 - We interested in local R-C sub-circuits!

Common-Emitter Amplifier: High-Frequency Analysis (2)




Common-Emitter Amplifier: High-Frequency Analysis (3)

* Miller Theorem: If there is a capacitor from input to output, we can add extra capacitor to the input and extra capacitor to the output by eliminating this capacitor.

$$C_{M,i} = (1 - A_v) \cdot C_{bc}$$

$$C_{M,o} = \left(1 - \frac{1}{A_v}\right) \cdot C_{bc}$$

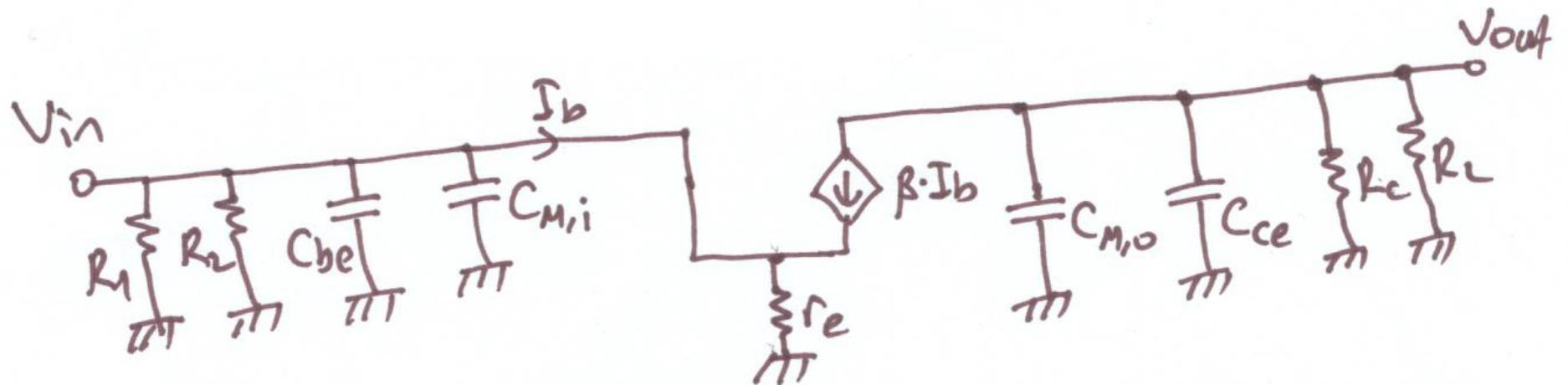
Common-Emitter Amplifier: High-Frequency Analysis (4)



$$f_{C4} = \frac{1}{2 \cdot \pi \cdot (R_1 // R_2 // ((\beta + 1) \cdot r_e)) \cdot (C_{be} + C_{M,i})}$$

$$f_{C5} = \frac{1}{2 \cdot \pi \cdot (R_C // R_L) \cdot (C_{M,o} + C_{ce})}$$

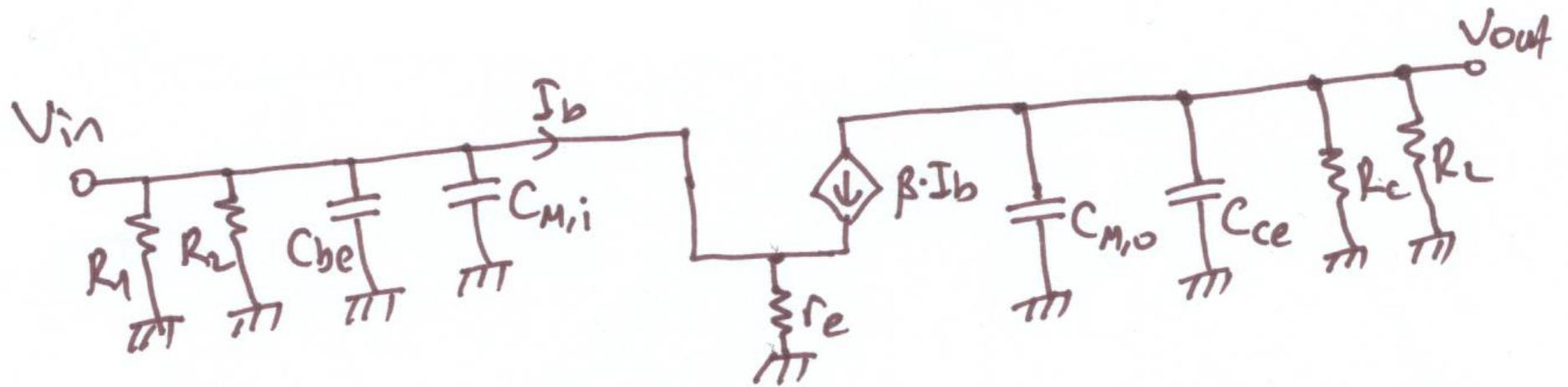
Common-Emitter Amplifier: High-Frequency Analysis (5)



$$f_{C4} = \frac{1}{2 \cdot \pi \cdot (R_1 // R_2 // ((\beta + 1) \cdot r_e)) \cdot (C_{be} + C_{M,i})}$$


$$f_{C5} = \frac{1}{2 \cdot \pi \cdot (R_c // R_L) \cdot (C_{M,o} + C_{ce})}$$

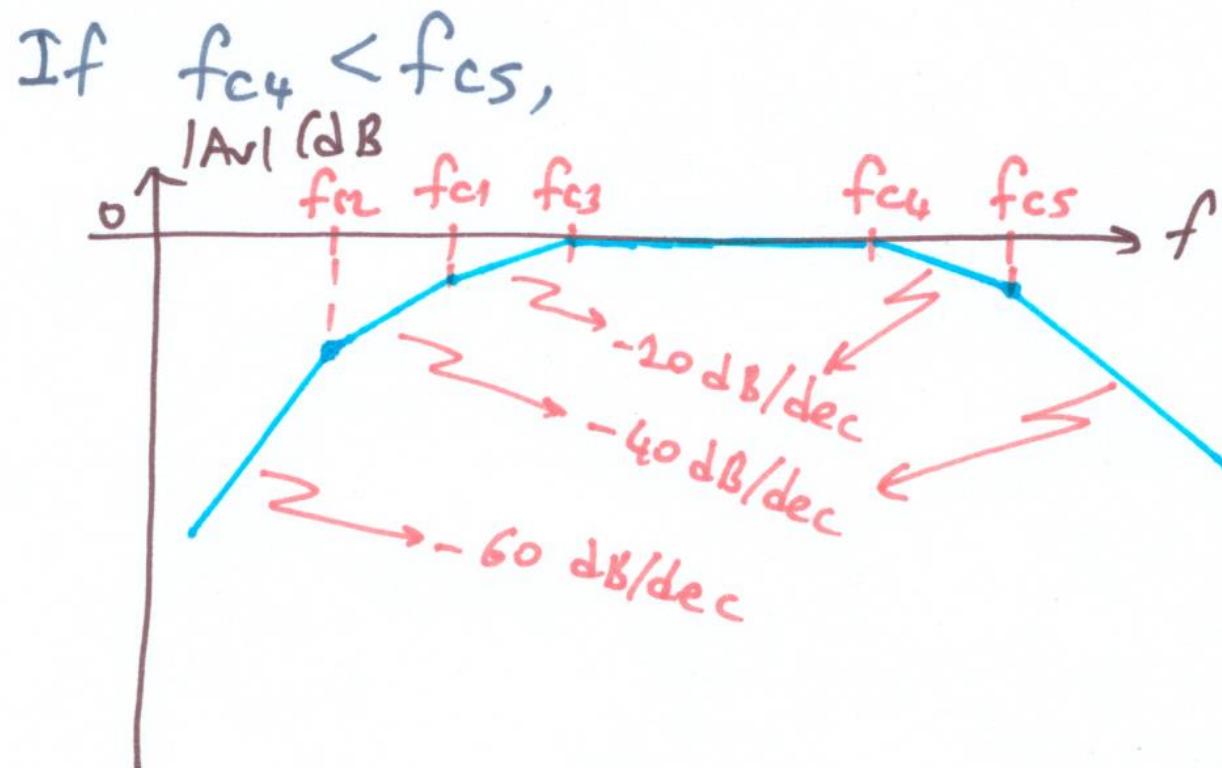Common-Emitter Amplifier: High-Frequency Analysis (6)



The complete frequency-response of a
common-emitter BJT amplifier.

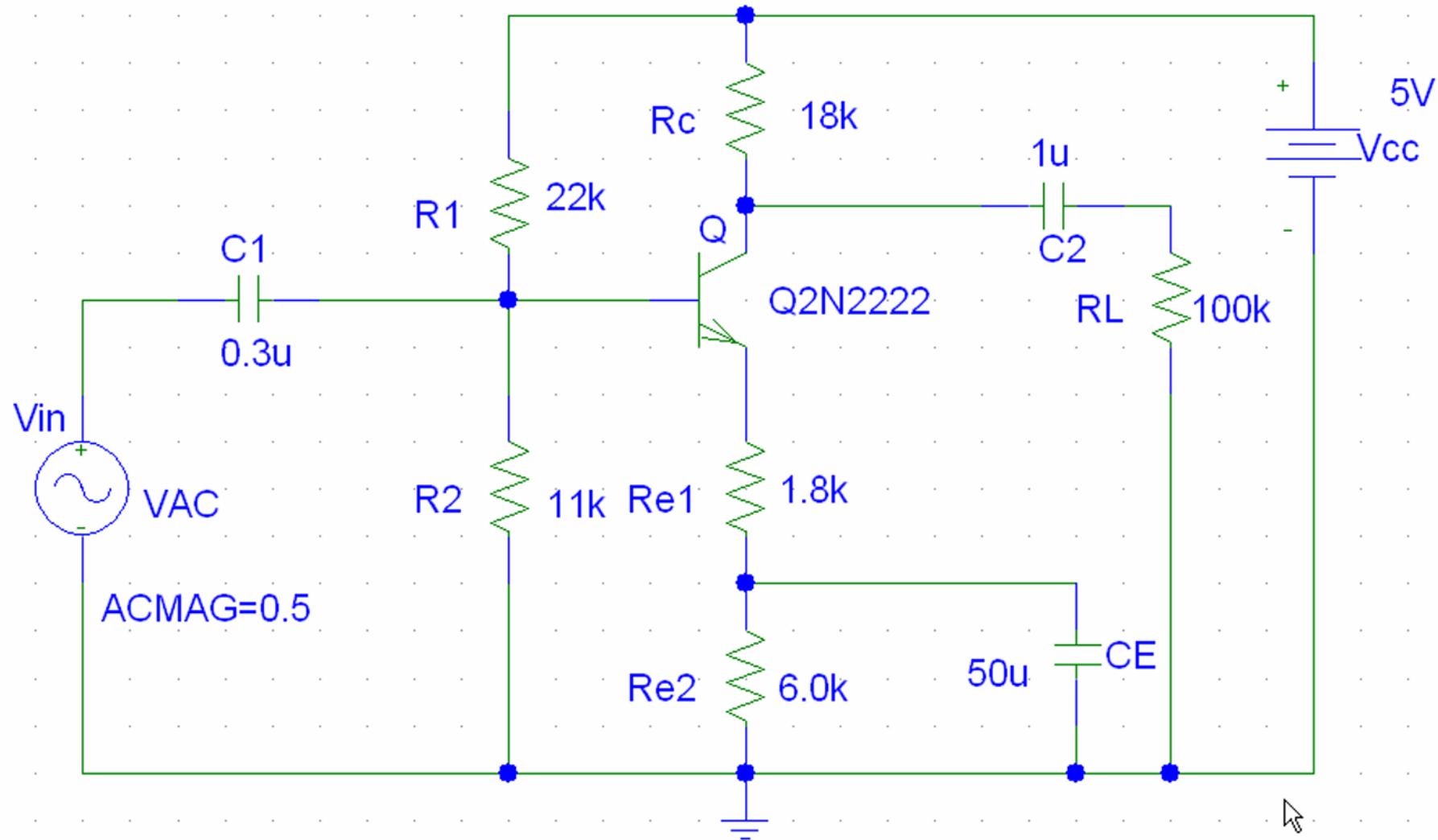Common-Emitter Amplifier: LTspice Example (1)




Common-Emitter Amplifier: LTspice Example (2)

Note that:

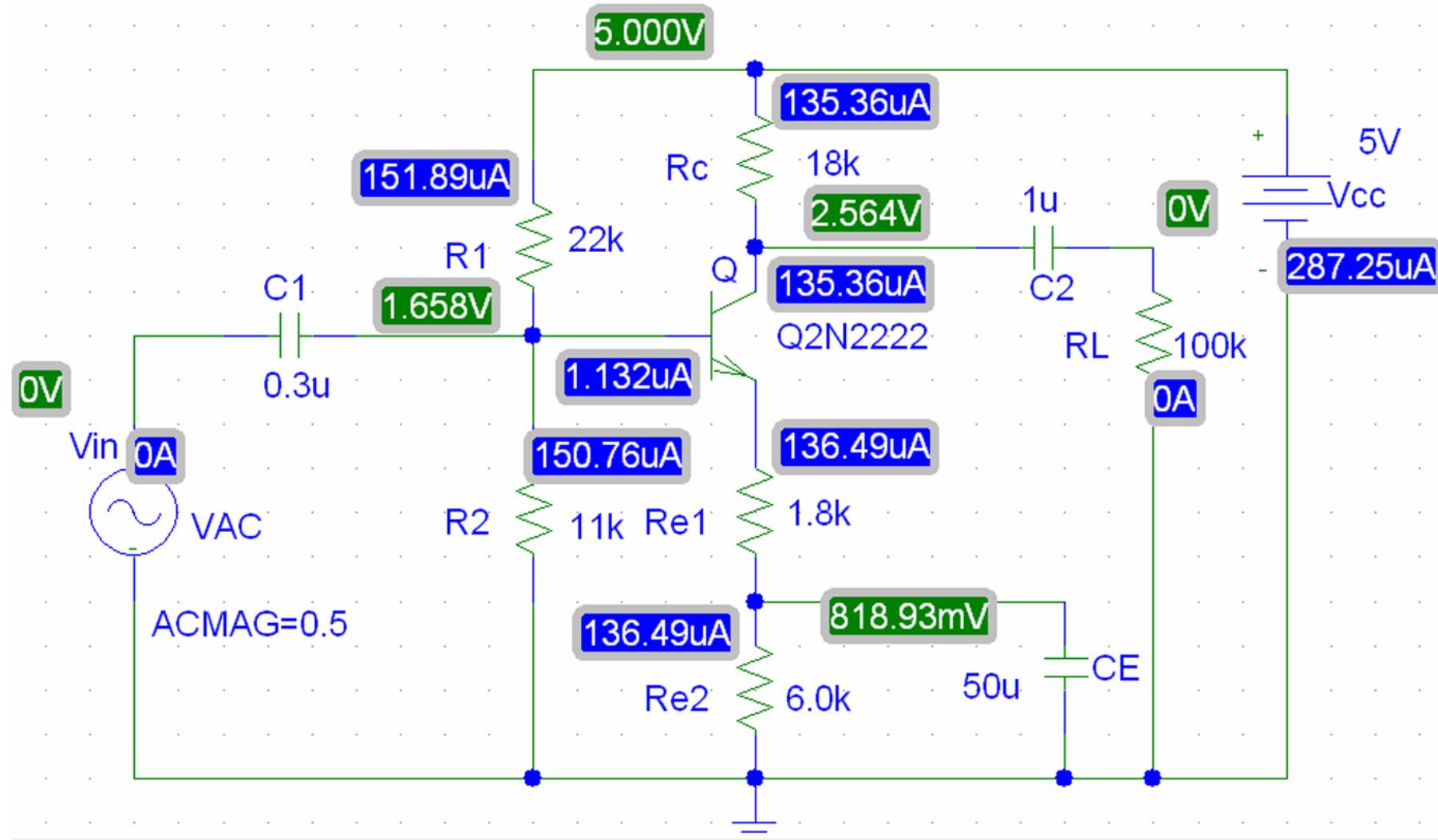- (a) Input signal is VAC (instead of usual VSIN) in the circuit since we need frequency response of the output voltage. AC Sweep is done only with VAC with only amplitude specified. Different frequency will be applied by the simulator.
- (b) To ease the limitation of power supply by IOBoard, V_{CC} is supplied by 5V source.
- (c) The load resistance in the circuit is chosen $100k\Omega$. This value may be significantly different from your assigned work. You, I mean, you need to do some work too. Right?
- (d) Why those values of resistors? Try to answer by DC analysis. Find expected voltage gain from the DC analysis.
- (e) Why those values of capacitors? Perform AC analysis and find expected low and high cutoff frequencies.


Common-Emitter Amplifier: LTspice Example (3)




Common-Emitter Amplifier: LTspice Example (4)

AC Sweep

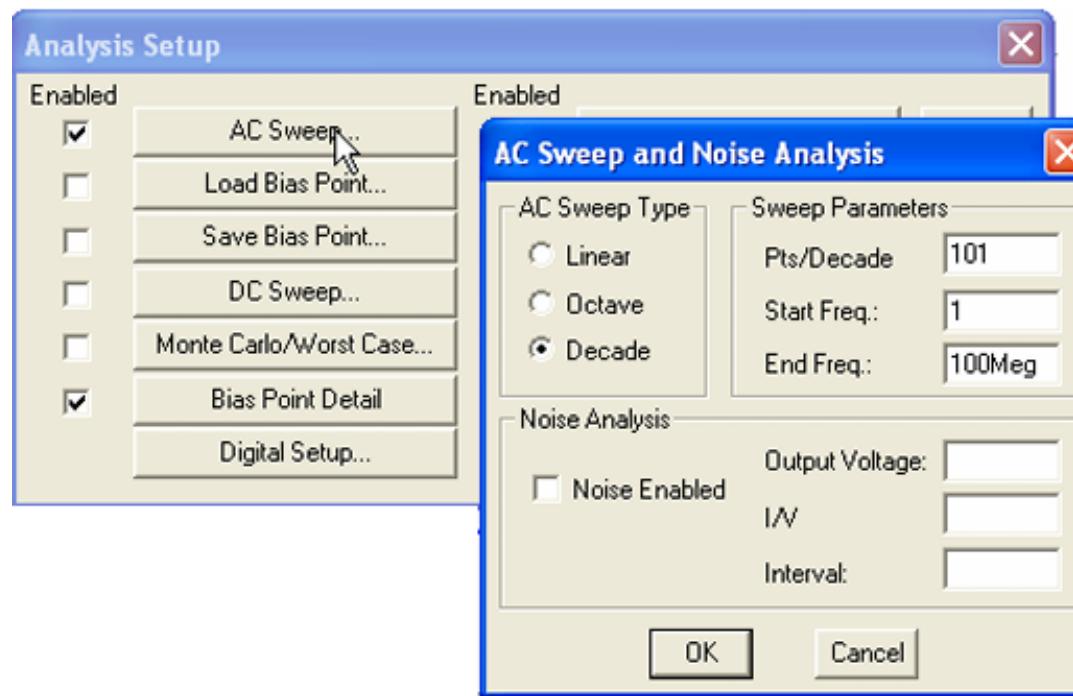
To do AC Sweep, your AC source must be VAC. You decide only ACMAG (AC magnitude), and I picked 0.5 in the circuit above. In the AC Sweep we have to assign our frequency band of interest. Here I set from 0 to 100MHz.



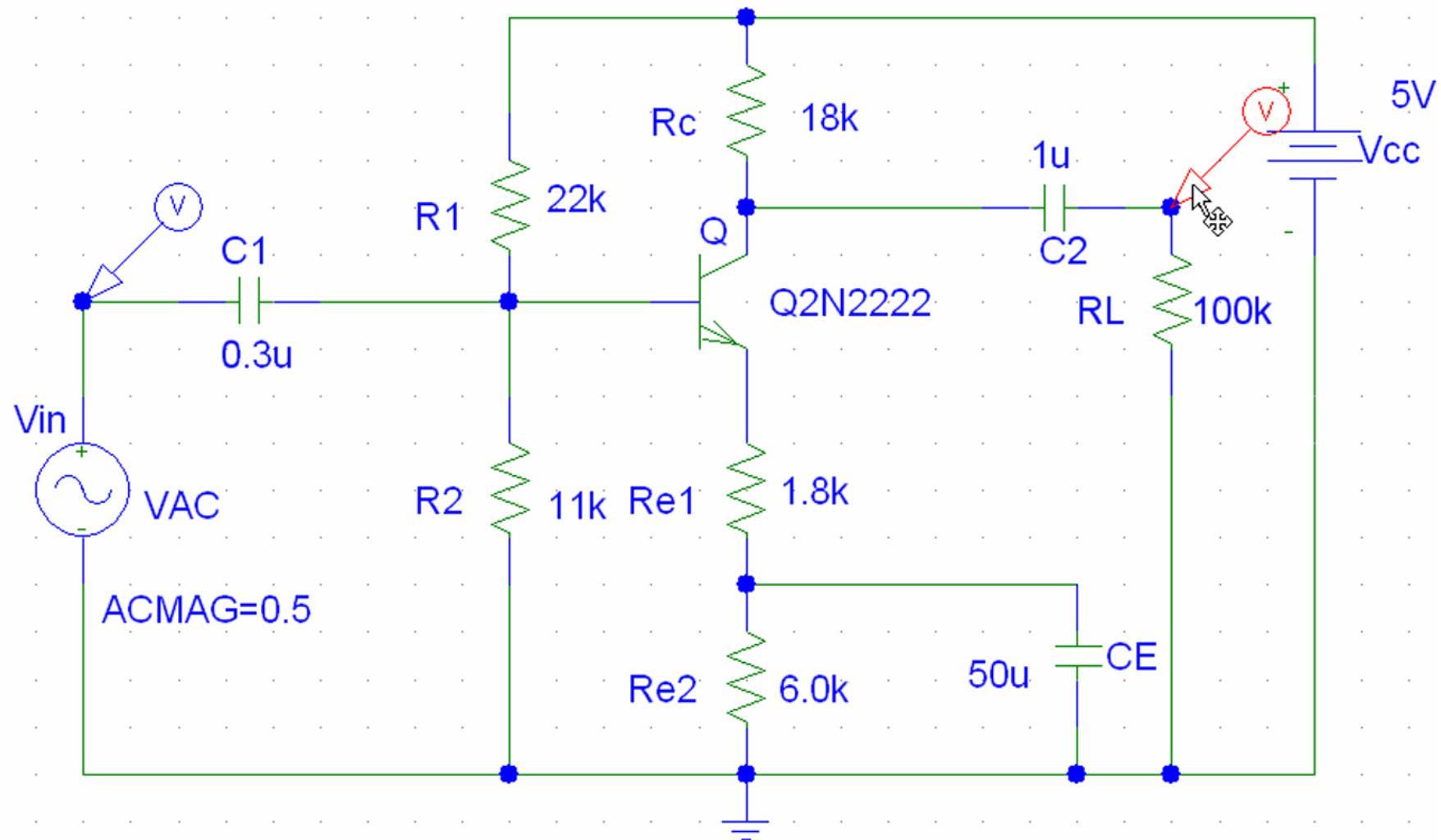Common-Emitter Amplifier: LTspice Example (5)



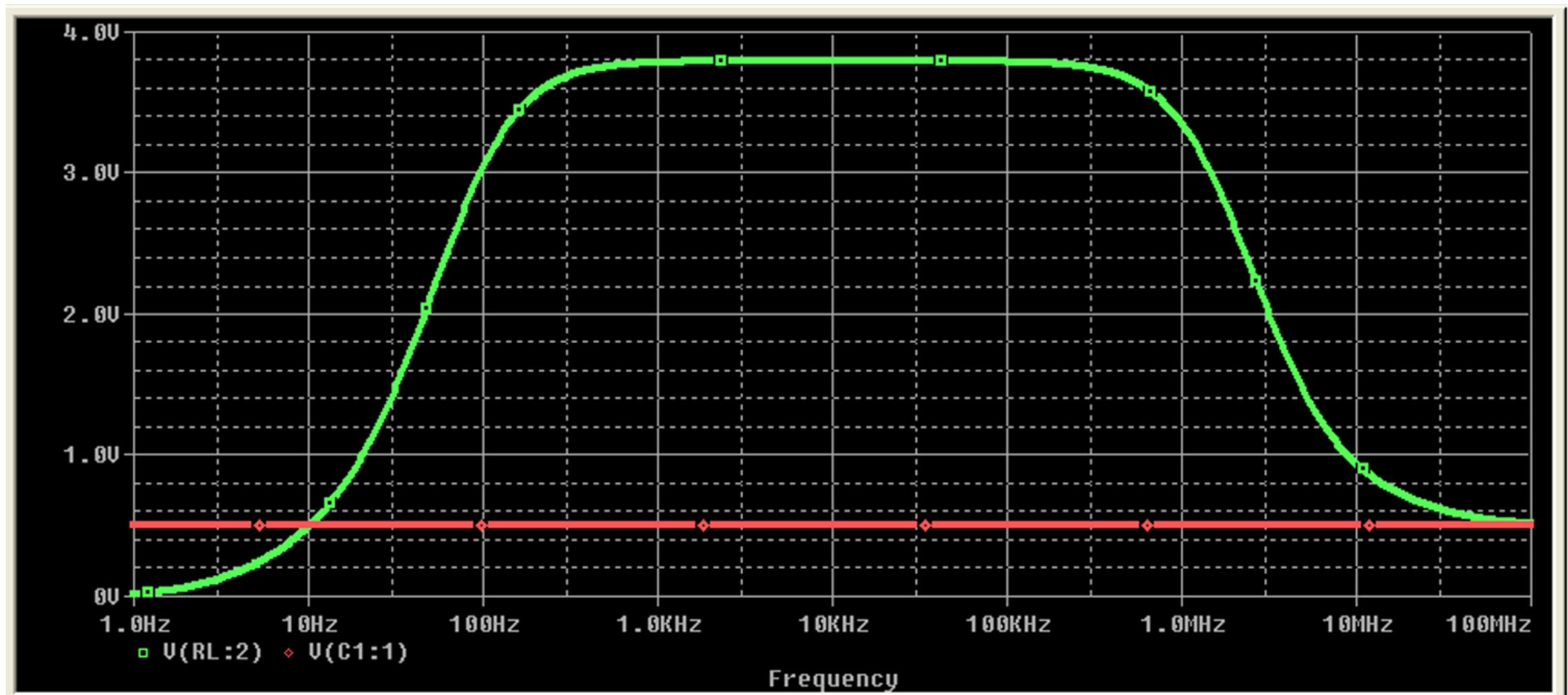Common-Emitter Amplifier: LTspice Example (6)



Common-Emitter Amplifier: LTspice Example (7)

The green tracing is the voltage at the load and red, the input voltage, at each of the frequency at the range of 0 - 100MHz. What is the low cutoff frequency? What is the high cutoff frequency? What is the mid-band voltage gain?

How can you change the cutoff frequencies by changing capacitor values?

How do you change the gain by changing resistor values?

Do you see the influence of load, so called "load effect"?

Common-Emitter Amplifier: 2N2222 Catalogue (1)

Absolute Maximum Ratings ($T_a = 25^\circ\text{C}$)

Parameter		Symbol	Value	Unit
Collector Base Voltage 2N2222 2N2222A		V_{CBO}	60	V
			75	
Collector Emitter Voltage 2N2222 2N2222A		V_{CEO}	30	V
			40	
Emitter Base Voltage 2N2222 2N2222A		V_{EBO}	5	V
			6	
Collector Current		I_C	600	mA
Power Dissipation		P_{tot}	625	mW
Junction Temperature		T_j	150	$^\circ\text{C}$
Storage Temperature Range		T_{stg}	- 55 to + 150	$^\circ\text{C}$

Common-Emitter Amplifier: 2N2222 Catalogue (2)

Characteristics at $T_a = 25^\circ\text{C}$

Parameter	Symbol	Min.	Max.	Unit
DC Current Gain at $V_{CE} = 10 \text{ V}$, $I_C = 0.1 \text{ mA}$ at $V_{CE} = 10 \text{ V}$, $I_C = 1 \text{ mA}$ at $V_{CE} = 10 \text{ V}$, $I_C = 10 \text{ mA}$ at $V_{CE} = 10 \text{ V}$, $I_C = 150 \text{ mA}$ at $V_{CE} = 10 \text{ V}$, $I_C = 500 \text{ mA}$	h_{FE} h_{FE} h_{FE} h_{FE} h_{FE}	35 50 75 100 30	300 - - - -	- - - - -
Collector Base Cutoff Current at $V_{CB} = 50 \text{ V}$ at $V_{CB} = 60 \text{ V}$	I_{CBO}	2N2222 2N2222A	- - -	10 10 nA
Collector Base Breakdown Voltage at $I_C = 10 \mu\text{A}$	$V_{(BR)CBO}$	2N2222 2N2222A	60 75	- -


Common-Emitter Amplifier: 2N2222 Catalogue (3)


Characteristics at $T_a = 25^\circ\text{C}$

Parameter	Symbol	Min.	Max.	Unit
Collector Emitter Saturation Voltage at $I_C = 150 \text{ mA}$, $I_B = 15 \text{ mA}$	2N2222	-	0.4	V
	2N2222A	-	0.3	
	2N2222	-	1.6	
	2N2222A	-	1	
Base Emitter Saturation Voltage at $I_C = 150 \text{ mA}$, $I_B = 15 \text{ mA}$	2N2222	-	1.3	V
	2N2222A	0.6	1.2	
	2N2222	-	2.6	
	2N2222A	-	2	
Gain Bandwidth Product at $I_C = 20 \text{ mA}$, $V_{CE} = 20 \text{ V}$, $f = 100 \text{ MHz}$	f_T	250	-	MHz

Left to Students

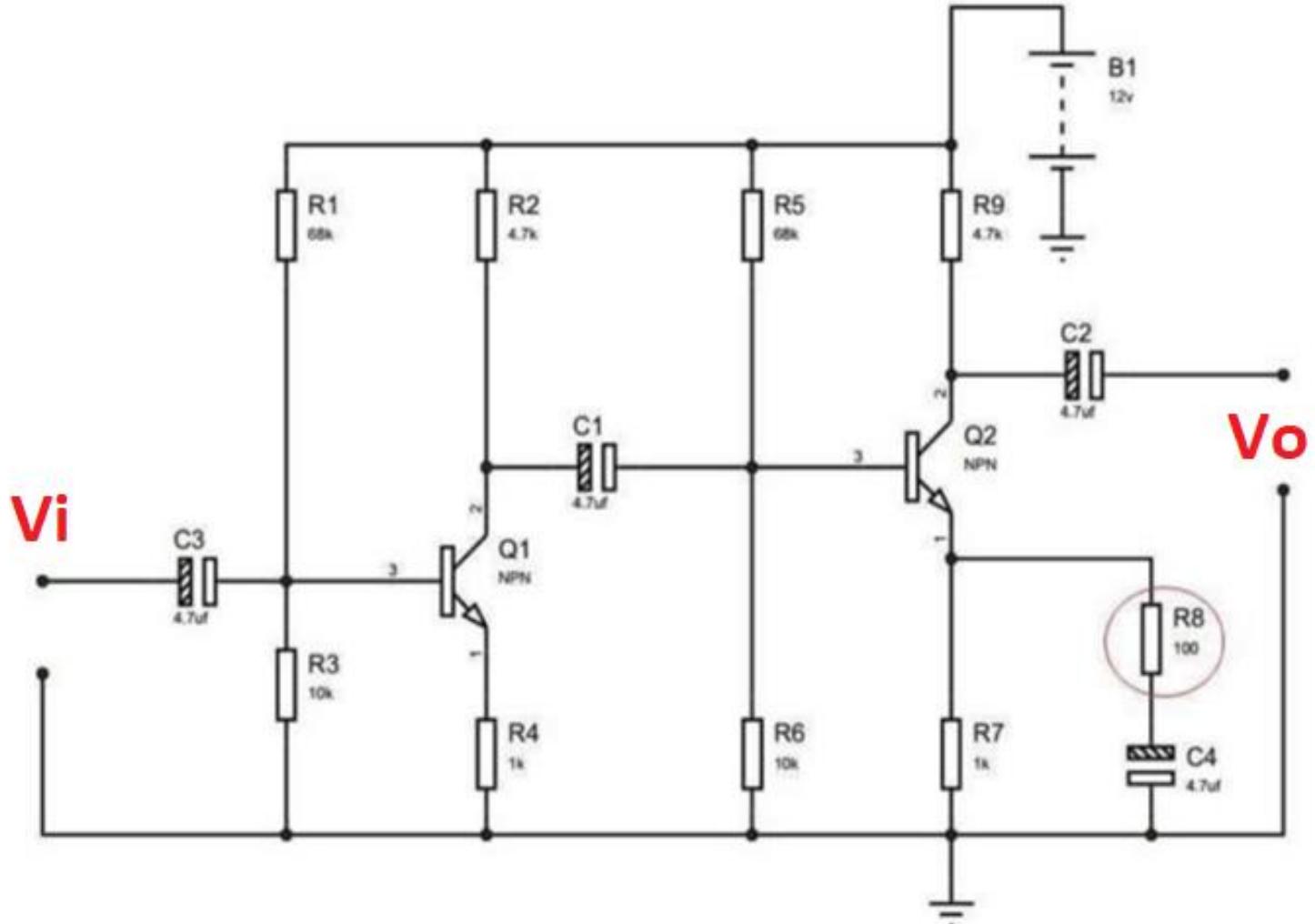- If we add an extra resistor (R_s) in series of the V_{in} , what will be change in equations?
- If we remove the C_E capacitor , what will be change in equations?
- If we connect two amplifiers in cascade connection (see the circuit on the right), what will be change in equations? Is there any change in corner frequencies?



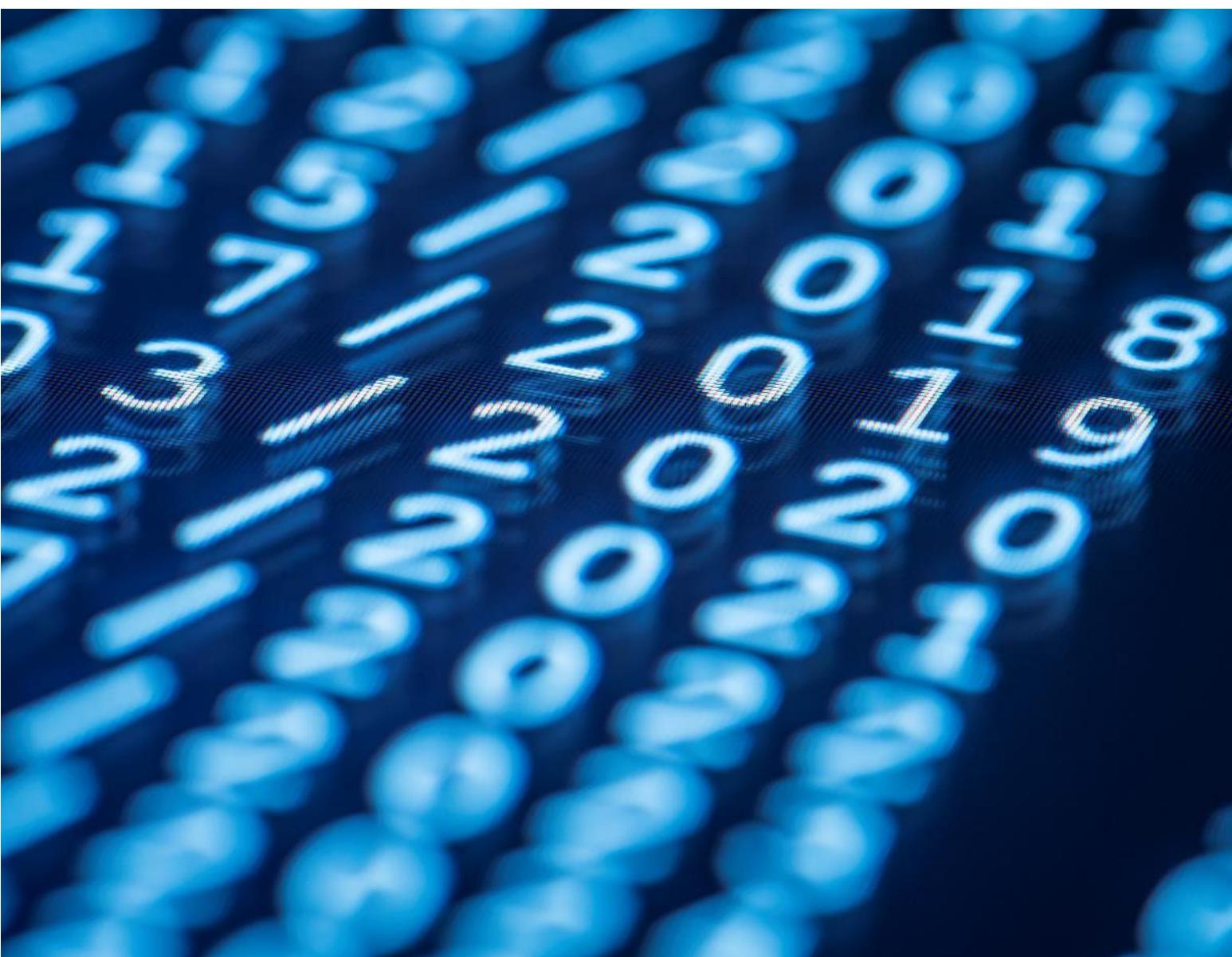

Thanks for
listening 😊

YALÇIN İŞLER

Assoc. Prof.