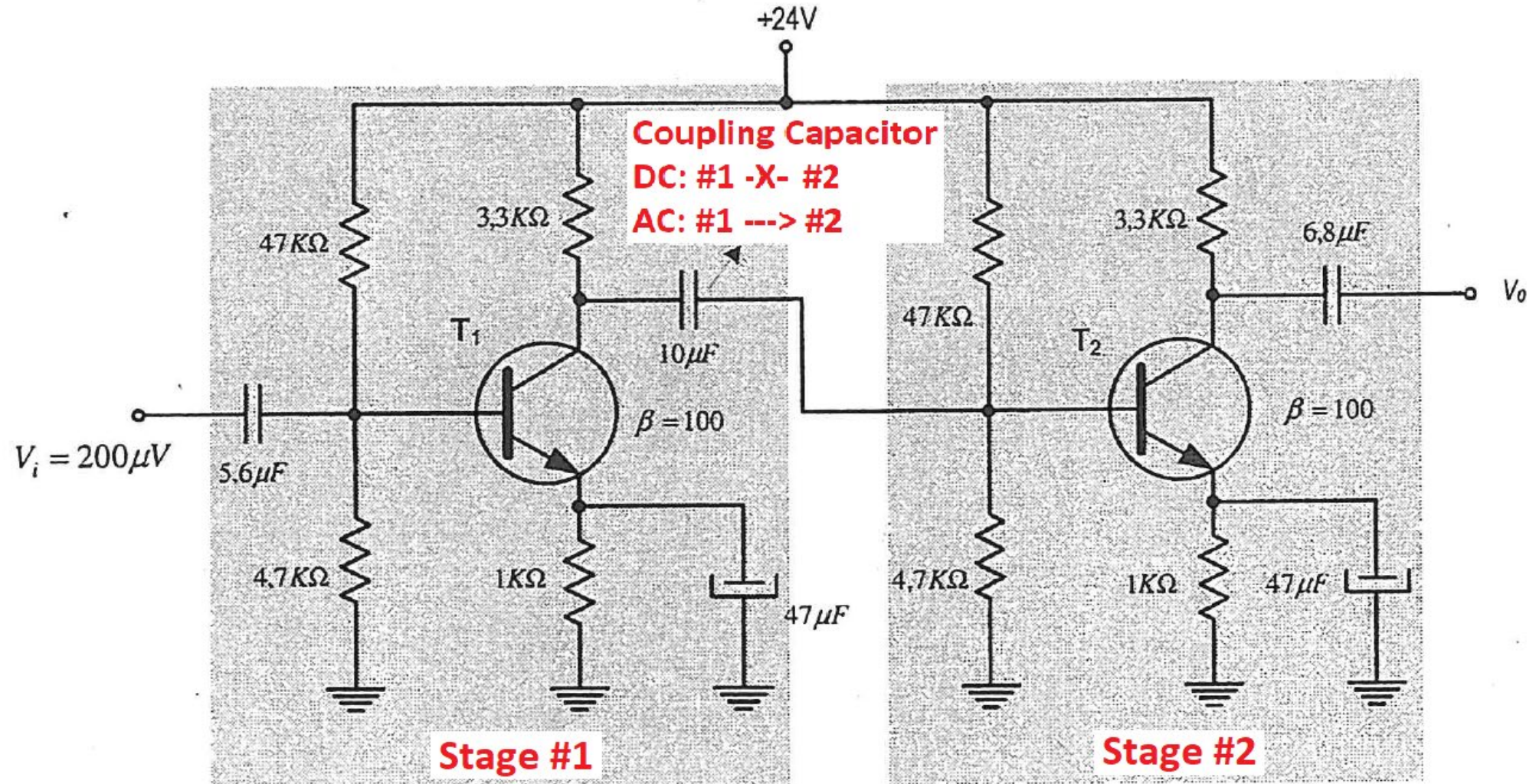




# Electronic Circuits


Lecture 5.2: Cascade Connection

# Cascade Connection




# Cascade Connection Example (1)

Cascade Connection:

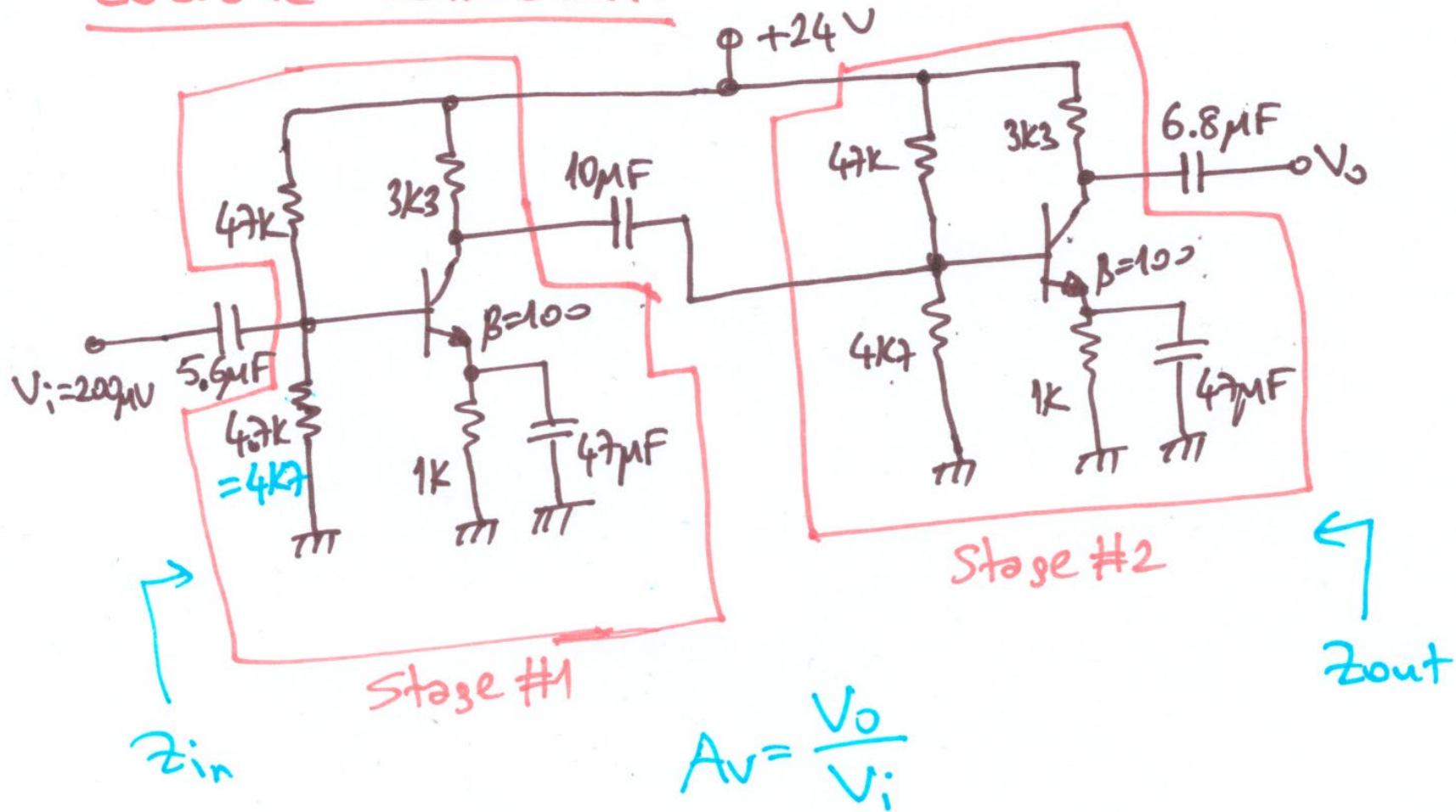

## Cascade Connection Example (2)
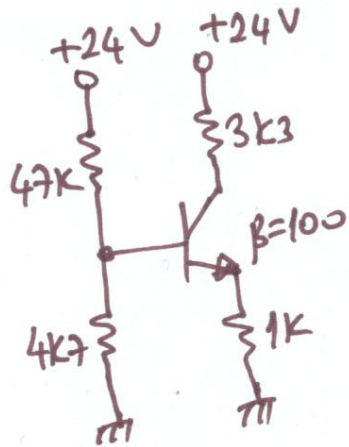
#1: DC Analysis: Both stages are same, so single DC analysis is enough ☺



$$R_{B1} = R_{B2} = \frac{47k \cdot 4k}{47k + 4k} = 4,27k\Omega$$

$$V_{B1} = V_{B2} = \frac{4k}{4k + 47k} \cdot (+24V) = 2,17V$$


$$I_{B1} = I_{B2} = \frac{2,17V - 0,7V}{4,27k + (\beta + 1) \cdot 1k} = 14\mu A$$

$$I_{E1} = I_{E2} = (\beta + 1) \cdot I_{B1} = 101 \cdot 14\mu A = 1,41\mu A$$

$$r_e = r_{e1} = r_{e2} = \frac{26mV}{1,41\mu A} = 18,44\Omega$$

## Cascade Connection Example (3)

### #2: AC Analysis:

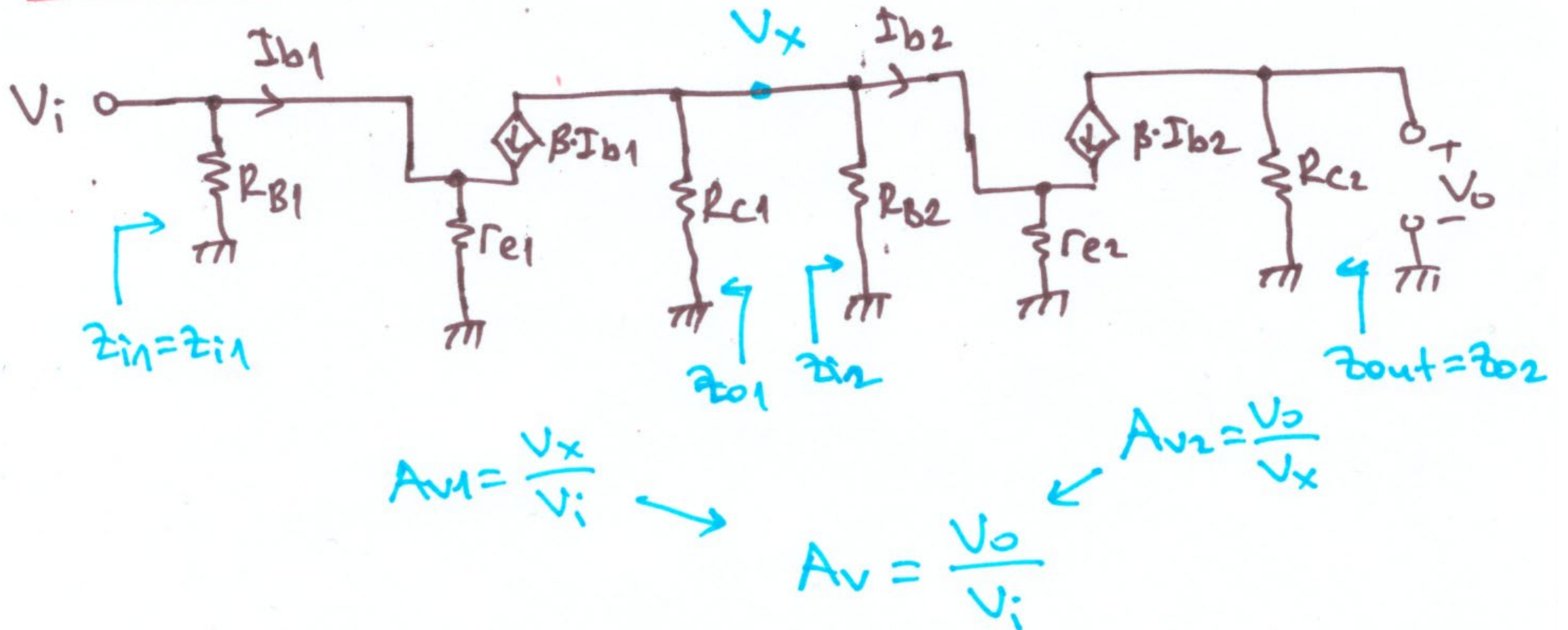

## Cascade Connection Example (4)

$$z_{i1} = R_{B1} // ((\beta+1) \cdot r_{e1}) = 1,29 \text{ k}\Omega \Rightarrow z_{in} = z_{i1} = \underline{1,29 \text{ k}\Omega}$$

$$z_{o1} = R_{C1} = 3,3 \text{ k}\Omega$$

$$z_{i2} = R_{B2} // ((\beta+1) \cdot r_{e2}) = 1,29 \text{ k}\Omega$$

$$z_{o2} = R_{C2} = 3,3 \text{ k}\Omega \Rightarrow z_{out} = z_{o2} = \underline{3,3 \text{ k}\Omega}$$

!  $z_{i2}$  is the load resistor of the stage #1.

## Cascade Connection Example (5)

$$I_{b1} = \frac{v_i}{(\beta+1) \cdot r_{e1}} \quad \text{and} \quad v_x = - (r_{o1} // r_{i2}) \cdot \beta \cdot I_{b1}$$

$$\text{So, } \frac{v_x}{v_i} = A_{v1} = - \frac{(3\text{k}\Omega // 1\text{k}\Omega) \cdot 100}{101 \cdot 18,44} = -49,8$$

$$I_{b2} = \frac{v_x}{(\beta+1) \cdot r_{e2}} \quad \text{and} \quad v_o = - r_{o2} \cdot \beta \cdot I_{b2}$$

$$\text{So, } \frac{v_o}{v_x} = A_{v2} = - \frac{3\text{k}\Omega \cdot 100}{101 \cdot 18,44} = -177,19$$

$$A_v = \frac{v_o}{v_i} = (-177,19) \cdot (-49,8) = \underline{8824}$$

## Cascade Connection Example (6)


ALTERNATIVELY, Block Analysis:

After DC analysis, we found  $r_e = 18.44 \Omega$



## Cascade Connection Example (7)

### #2 AC Analysis of a single stage:

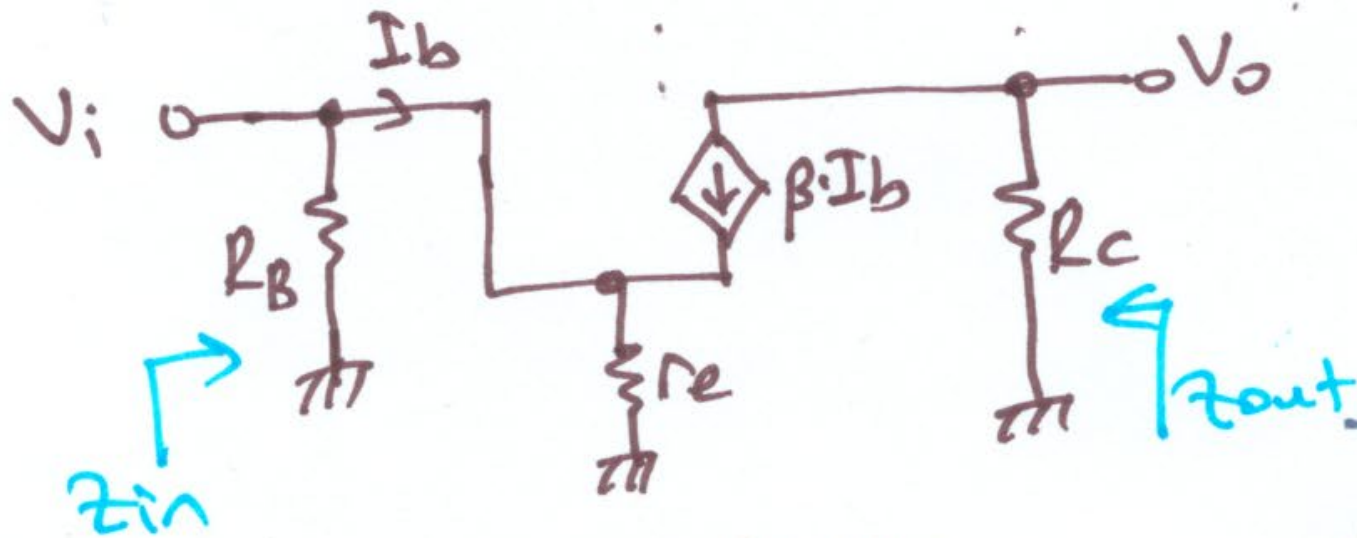

$$z_{in} = R_B \parallel ((\beta + 1) \cdot r_e) = 1,29 \text{ k}\Omega$$

$$I_b = \frac{V_i}{(\beta + 1) \cdot r_e}$$


$$V_o = -R_C \cdot \beta \cdot I_b$$

$$A_v = \frac{V_o}{V_i} = -\frac{\beta \cdot R_C}{(\beta + 1) \cdot r_e} = -177,19$$

$$z_{out} = R_C = 3,3 \text{ k}\Omega$$


## Cascade Connection Example (8)

#3 Block Analysis:

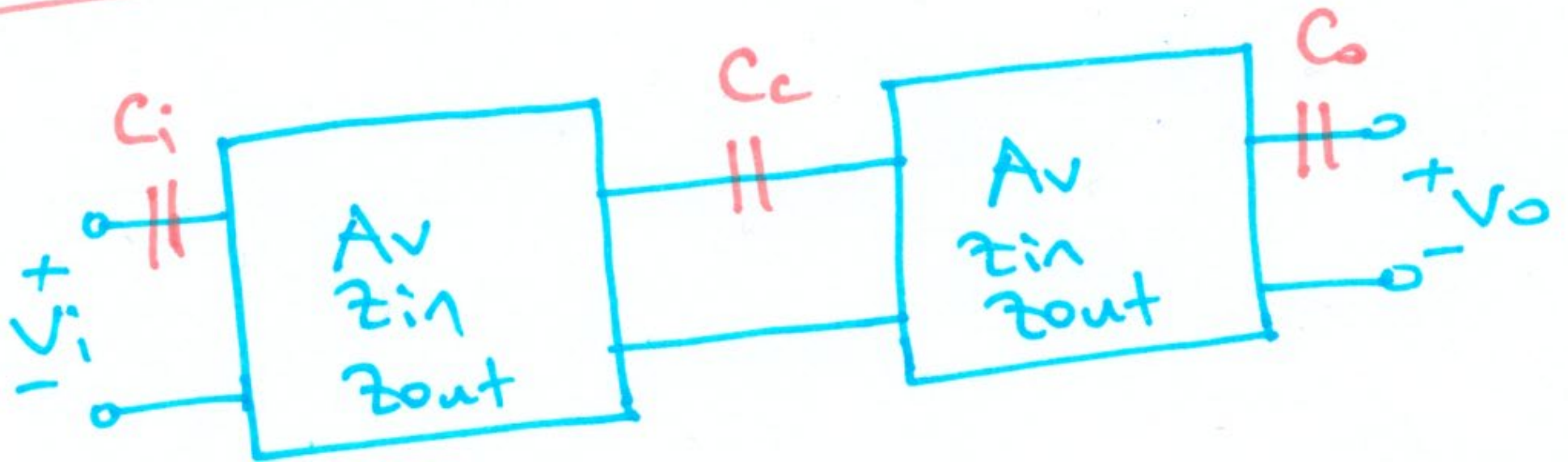

## Cascade Connection Example (9)

AC equivalent:

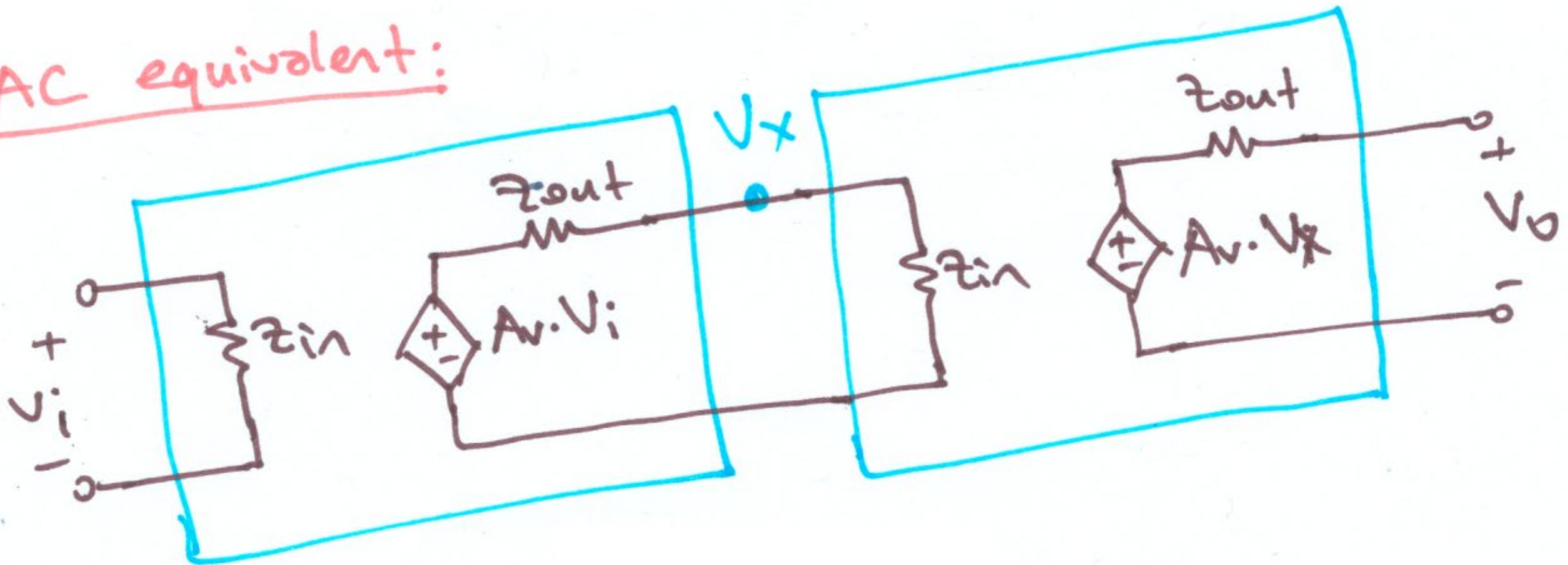

## Cascade Connection Example (10)

$$V_x = \frac{z_{in}}{z_{in} + z_{out}} \cdot A_v \cdot V_i$$

$$V_o = A_v \cdot V_x = A_v \cdot A_v \cdot \frac{z_{in}}{z_{in} + z_{out}} \cdot V_i$$

$$A_v = \frac{V_o}{V_i} = (177,19) \cdot (-177,19) \cdot \frac{1,29K}{1,29K + 3,3K} \approx 8824$$

As a result, if you know  $z_{in}$ ,  $z_{out}$ , and  $A_v$  characteristics of an amplifier, you can reach simple calculations at all.



Thanks for  
listening 😊

YALÇIN İŞLER

Assoc. Prof.