

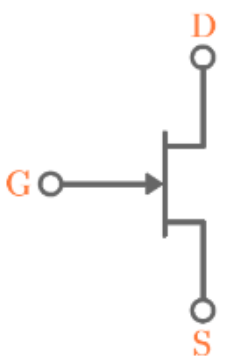
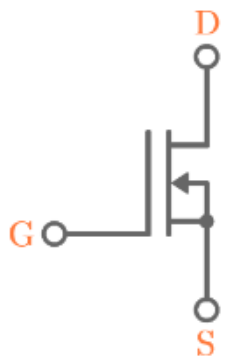
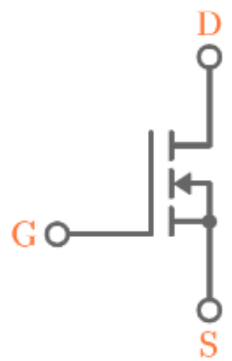


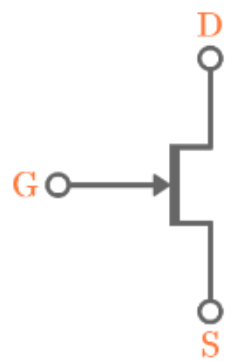


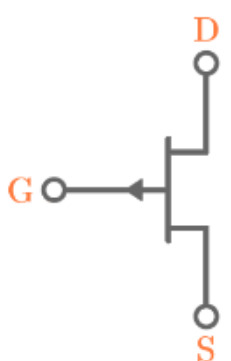

# Electronic Circuits

Lecture 5.1: Field Effect Transistor (FET)



# Field Effect Transistors (FETs)

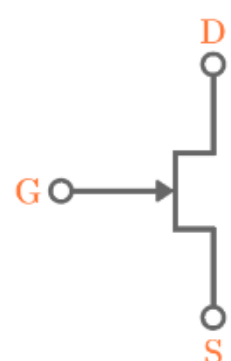JFET	MOSFET		MESFET (n-channel)
	(Depletion)	(Enhancement)	
			
n-channel	n-channel	n-channel	Depletion
			
p-channel	p-channel	p-channel	Enhancement


# Formulas

Drain Current	$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$
Gate to Source Voltage	$V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right)$
Power Dissipation	$P_D = V_{DS} I_D$
Resistance at a particular level of $V_{GS}$	$r_d = \frac{r_o}{\left(1 - \frac{V_{GS}}{V_P}\right)^2}$
Drain Current (MOSFET/MESFET Enhancement type)	$I_D = k (V_{GS} - V_T)^2$ $k = \frac{I_{D(ON)}}{(V_{GS(ON)} - V_T)^2}$

# N-Channel FET

  

## N-Channel FET (AC Equivalent Circuit)

 


gate – source ~ open circuit

$$I_d = I_{dss} \left( 1 - \frac{V_{gs}}{V_p} \right)^2$$

$$g_m = \left. \frac{dI_d}{dV_{gs}} \right|_{V_{ds} \text{ at operating point}}$$

$$r_d = \left. \frac{dV_{ds}}{dI_d} \right|_{V_{gs} \text{ at operating point}}$$

# FET Analysis Example #1: DC Analysis

 

$$R_g * 0 + V_{gs} + R_s * I_d = 0$$

$$I_d = I_{dss} \left( 1 - \frac{V_{gs}}{V_p} \right)^2$$


---

$$I_d - I_{dss} \left( 1 + \frac{R_s * I_d}{V_p} \right)^2 = 0$$

---

We can find  $I_d$ ,  $V_{gs}$ ,  $V_{ds}$ , and in general,  $V_d$  is the output point.

# FET Analysis Example #1: AC Analysis

 

$$V_{out} = -R_d * I_d$$

$$V_{out} = r_d * (I_d - g_m * V_{gs}) + R_s * I_d$$

$$V_{in} = V_{gs} + R_s * I_d$$


---

$$V_{in} = V_{gs} - R_s * \frac{V_{out}}{R_d}$$

---

We can find  $V_{gs}$ ,  $V_{ds}$ ,  $I_d$ , and in general,  $V_d$  is the output point.

# Fixed-Bias Configuration

 

Gate to Source Voltage


$$V_{GS} = -V_{GG}$$

Drain to Source Voltage

$$V_{DS} = V_{DD} - I_D R_D$$



# Self Bias Configuration

 


Gate to Source Voltage

$$V_{GS} = -I_D R_S$$

Drain to Source Voltage

$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

# Voltage-Divider Bias Configuration

 

Gate Terminal Voltage

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD}$$


Gate to Source Voltage

$$V_{GS} = V_G - I_D R_S$$

Drain to Source Voltage

$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

# Common Gate Configuration

 

Gate to Source Voltage

$$V_{GS} = V_{SS} - I_D R_S$$

Drain to Source Voltage

$$V_{DS} = V_{DD} + V_{SS} - I_D (R_S + R_D)$$



Thanks for  
listening 😊

YALÇIN İŞLER

Assoc. Prof.