
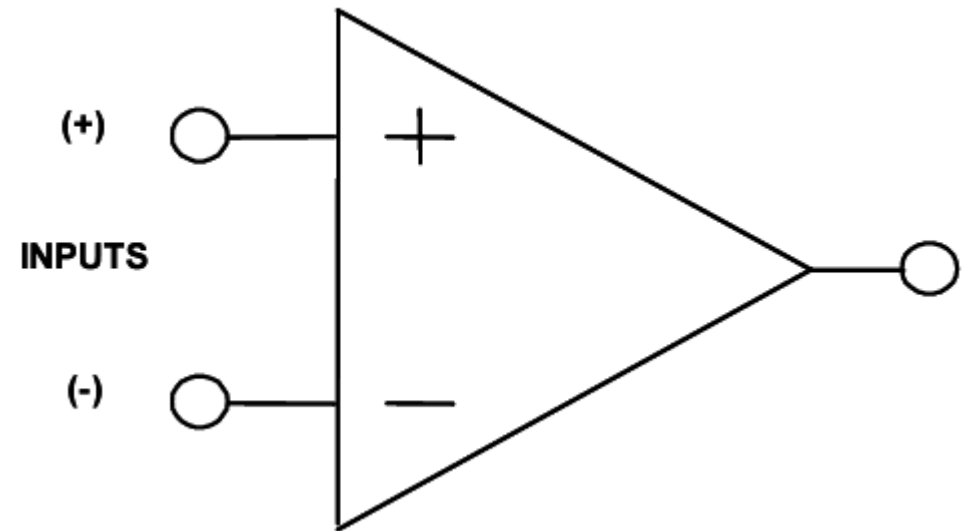


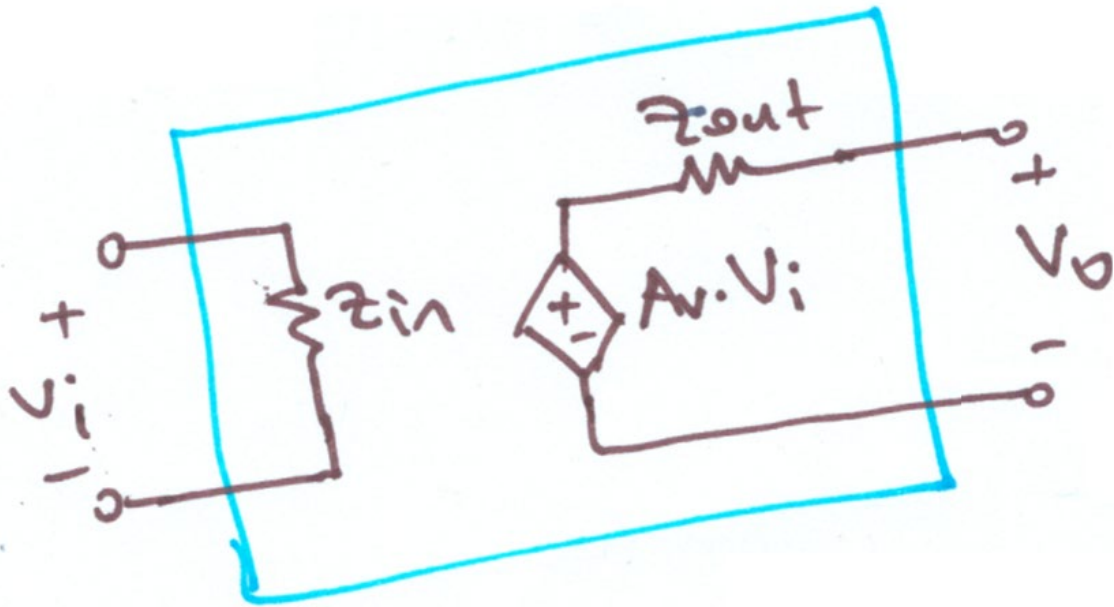

Electronic Circuits


Lecture 8.1: Operational Amplifiers (OPAMPs)

Amplifier Block and Ideal Opamp are EQUAL




$Z_{in} \rightarrow \infty$
 $A_v \rightarrow \infty$
 $Z_{out} \rightarrow 0$

Ideal Opamp Properties

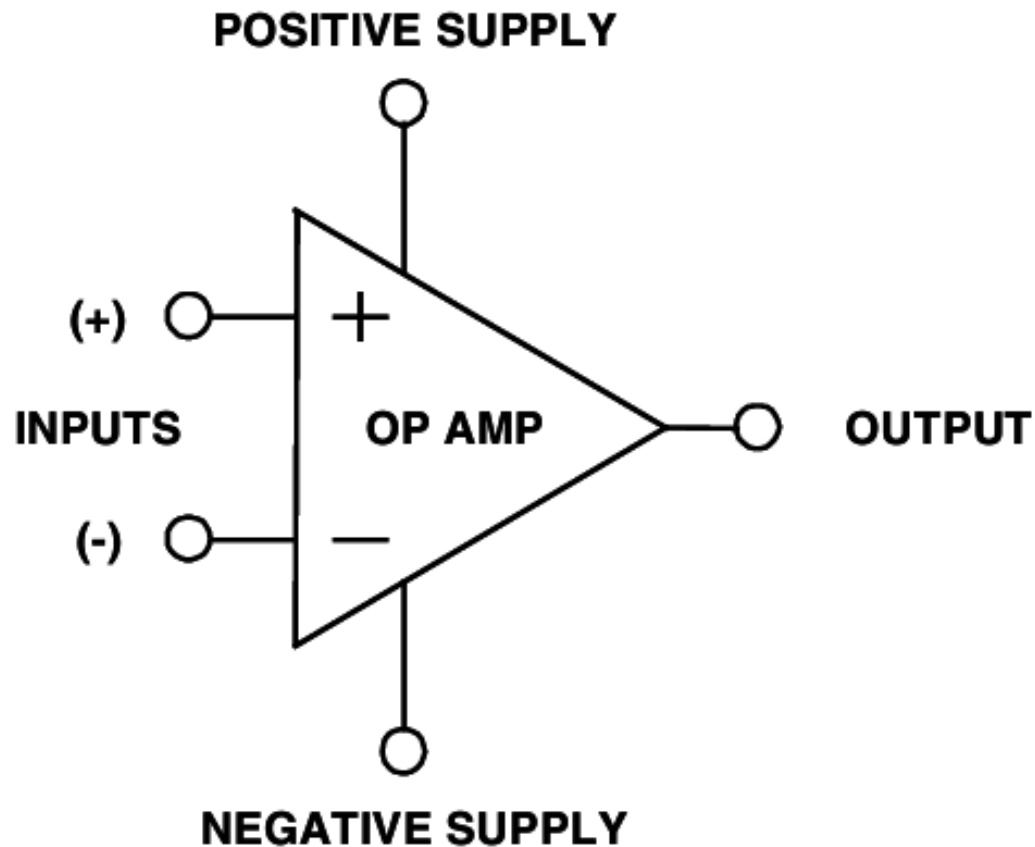

- **IDEAL OP AMP ATTRIBUTES**
 - Infinite Differential Gain
 - Zero Common Mode Gain
 - Zero Offset Voltage
 - Zero Bias Current
 - Infinite Bandwidth
- **OP AMP INPUT ATTRIBUTES**
 - Infinite Impedance
 - Zero Bias Current
 - Respond to Differential Voltages
 - Do Not Respond to Common Mode Voltages
- **OP AMP OUTPUT ATTRIBUTES**
 - Zero Impedance

Comparator

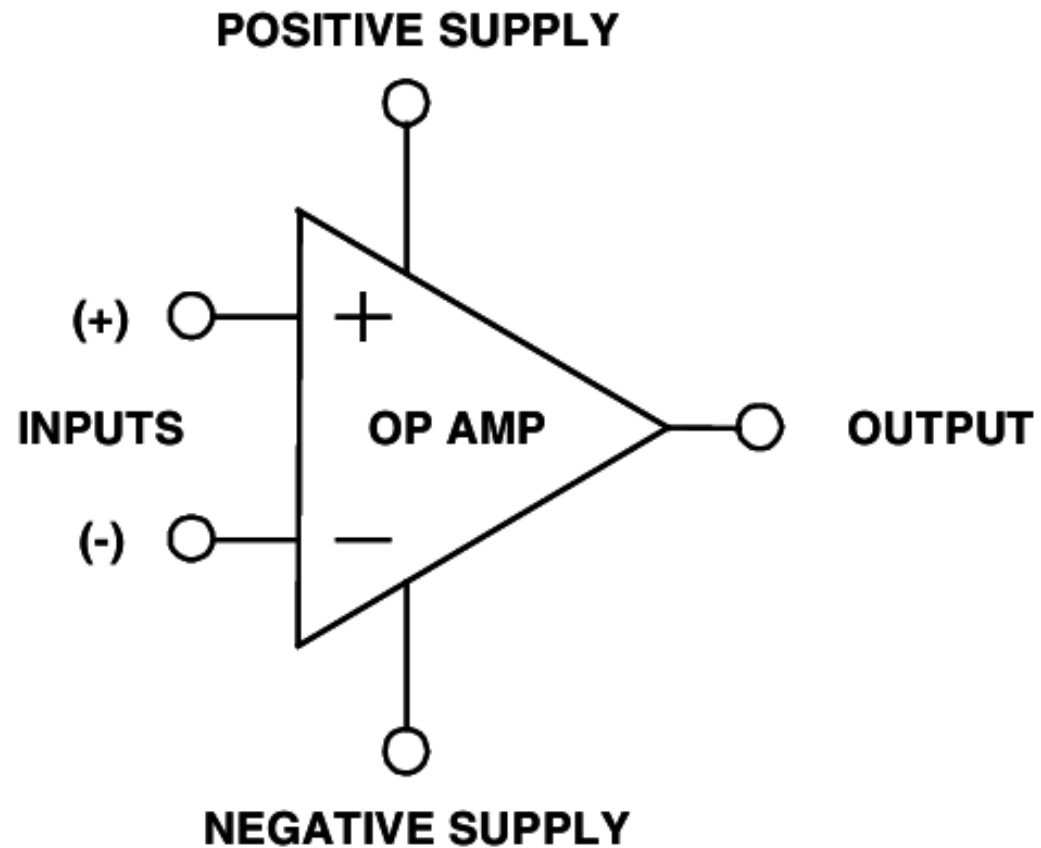


- $V_{out} \approx \text{POSITIVE SUPPLY} - 2 \text{ volts}$ if $V_{in(+)} > V_{in(-)}$
- $V_{out} \approx \text{NEGATIVE SUPPLY} + 2 \text{ volts}$ if $V_{in(-)} > V_{in(+)}$
- $V_{out} \approx 0 \text{ volts}$ if $V_{in(+)} = V_{in(-)}$ where almost impossible

Basic Properties for Feedback Connection

- Basic Properties:
 - $V_{in(+)} \approx V_{in(-)}$
 - $i_{in(+)} \approx 0$
 - $i_{in(-)} \approx 0$
- Since its voltage gain is so high that a feedback connection (from output to input(s)) is used in general.

Buffer (Voltage Follower)

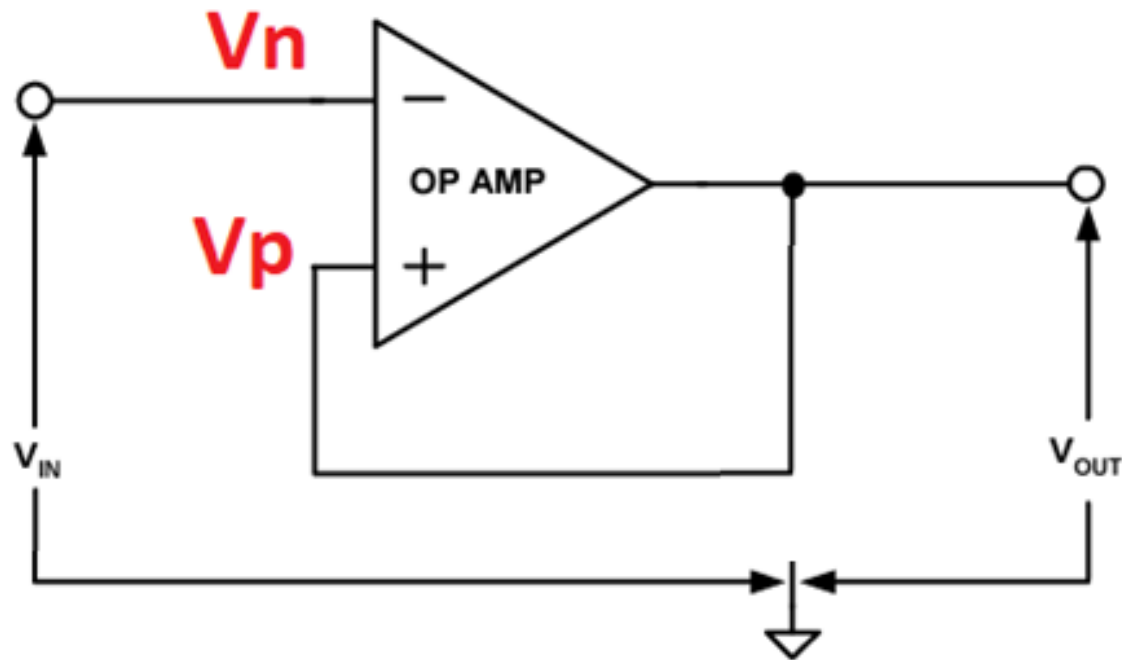

$$V_n = V_p$$


$$V_p = V_{IN}$$

$$V_n = V_{OUT}$$

$$V_{IN} = V_{OUT}$$


$$A_v = \frac{V_{OUT}}{V_{IN}} = 1$$

Left To Students (1)

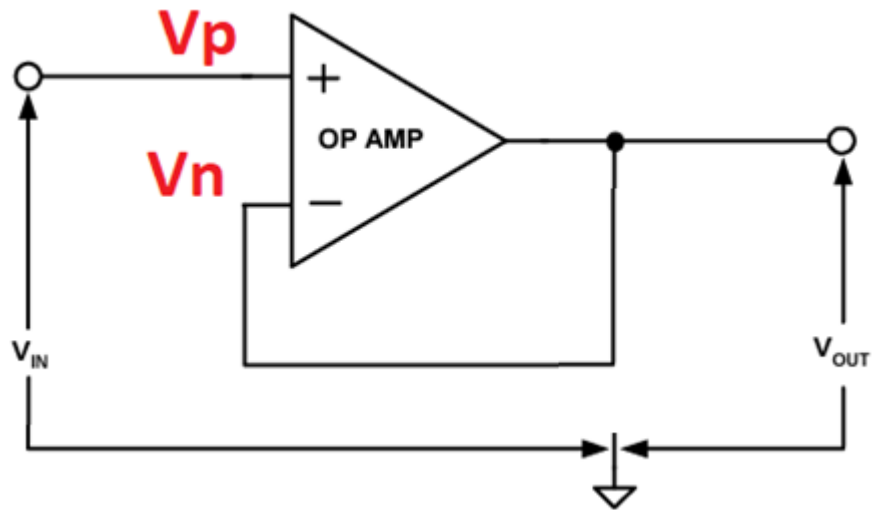

- $A_v = ?$

Inverting Amplifier

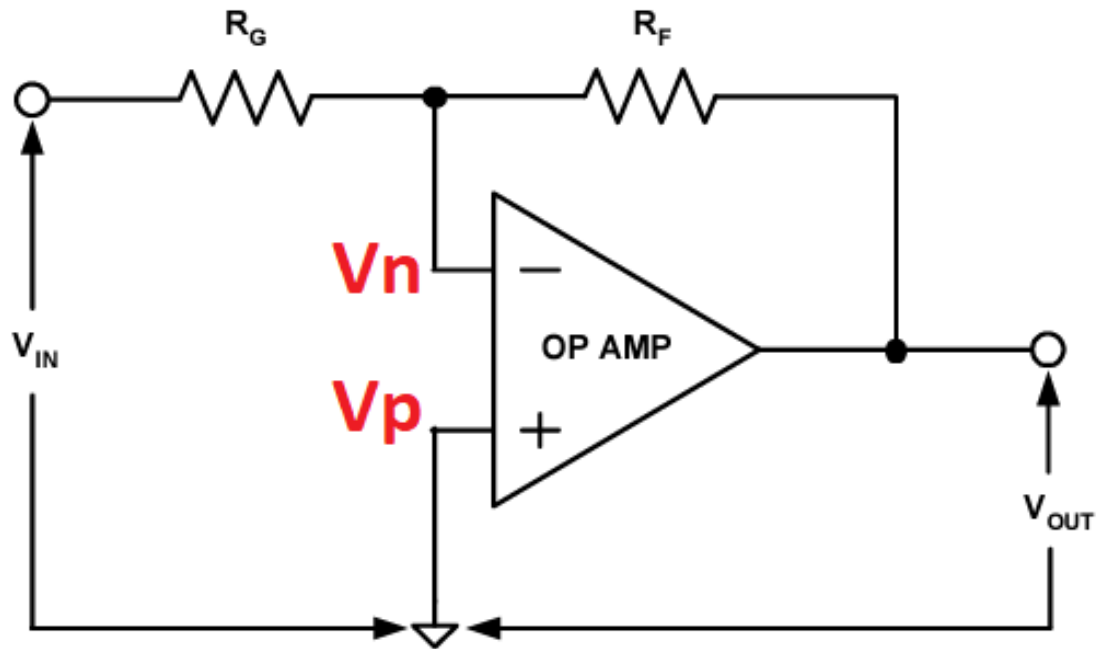


$$V_n = V_p = GND = 0$$

$$\frac{V_{IN} - V_n}{R_G} = \frac{V_n - V_{OUT}}{R_F}$$

$$\frac{V_{IN}}{R_G} = \frac{-V_{OUT}}{R_F}$$


$$A_v = \frac{V_{OUT}}{V_{IN}} = -\frac{R_F}{R_G}$$

Left To Students (2)

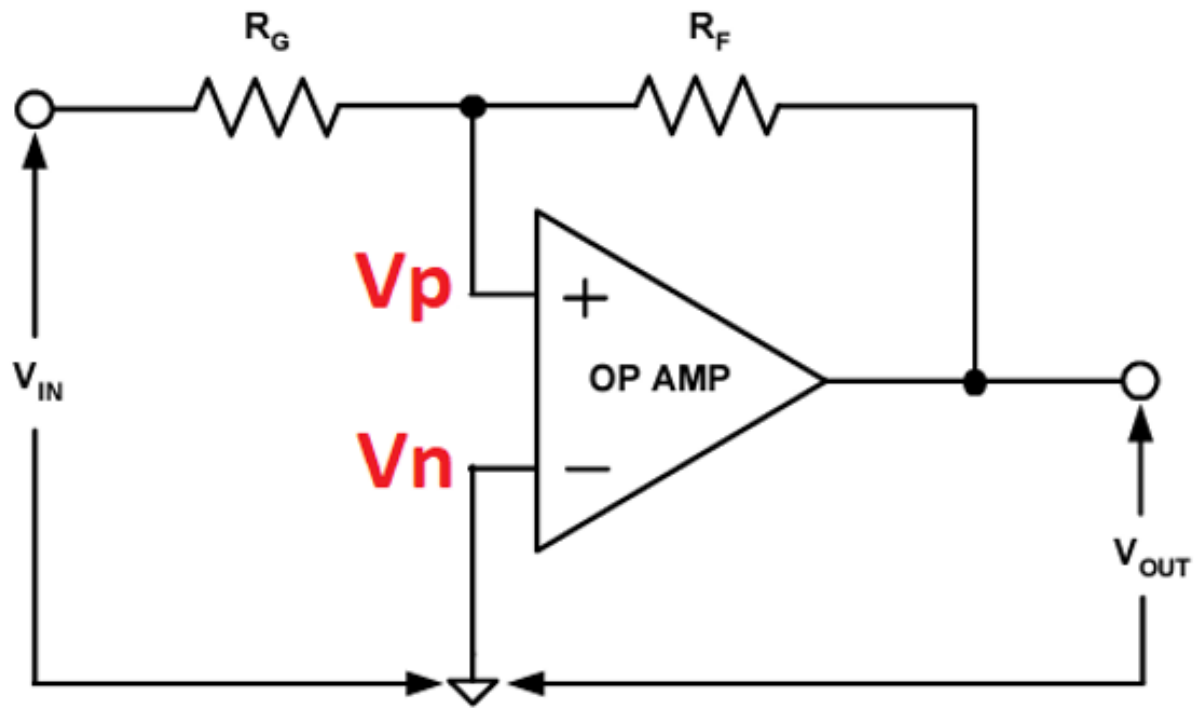

■ $A_v = ?$

Non-Inverting Amplifier

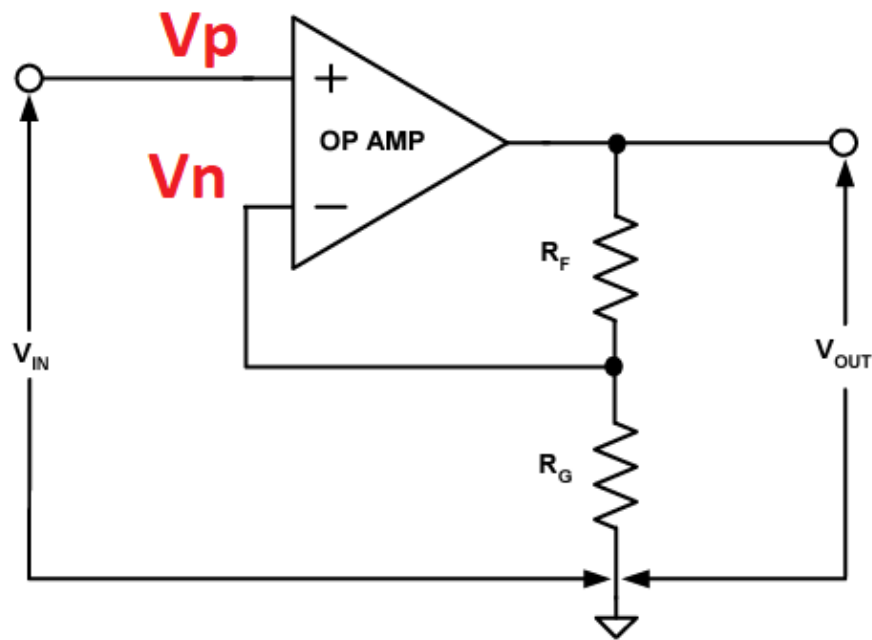

$$V_n = V_p = V_{IN}$$


$$\frac{V_{OUT} - V_n}{R_F} = \frac{V_n - 0}{R_G}$$

$$\frac{V_{OUT} - V_{IN}}{R_F} = \frac{V_{IN}}{R_G}$$

$$\frac{V_{OUT}}{R_F} = \frac{V_{IN}}{R_G} + \frac{V_{IN}}{R_F} = V_{IN} * \left(\frac{R_F + R_G}{R_F * R_G} \right)$$

$$A_v = \frac{V_{OUT}}{V_{IN}} = \frac{R_F + R_G}{R_G} = 1 + \frac{R_F}{R_G}$$

Left To Students (3)

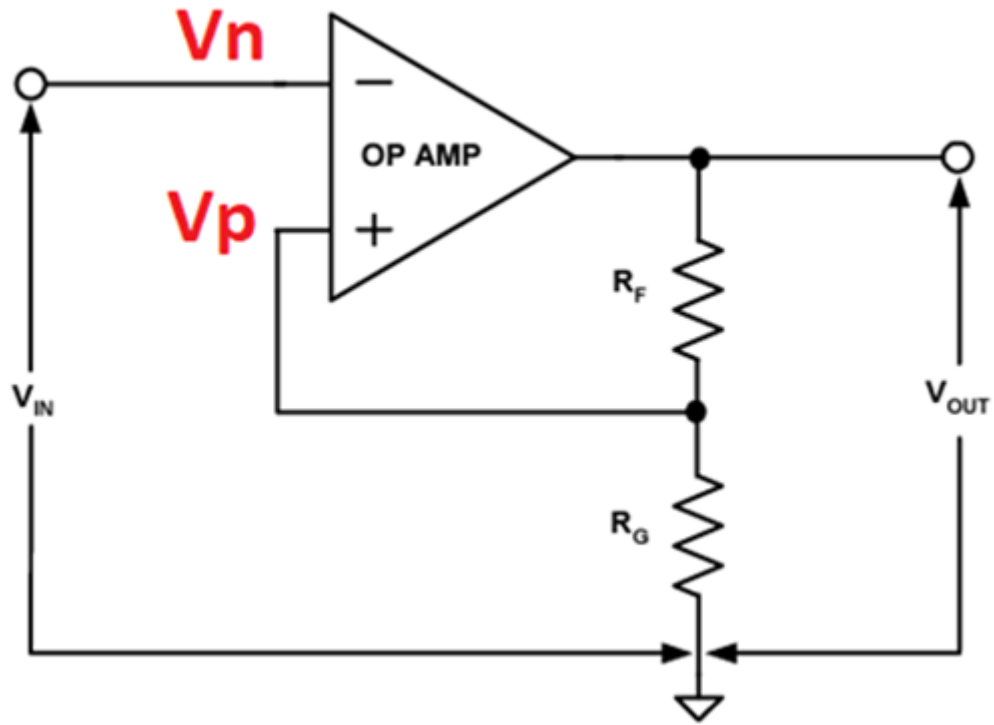

- $A_v = ?$



Thanks for
listening 😊

YALÇIN İŞLER

Assoc. Prof.