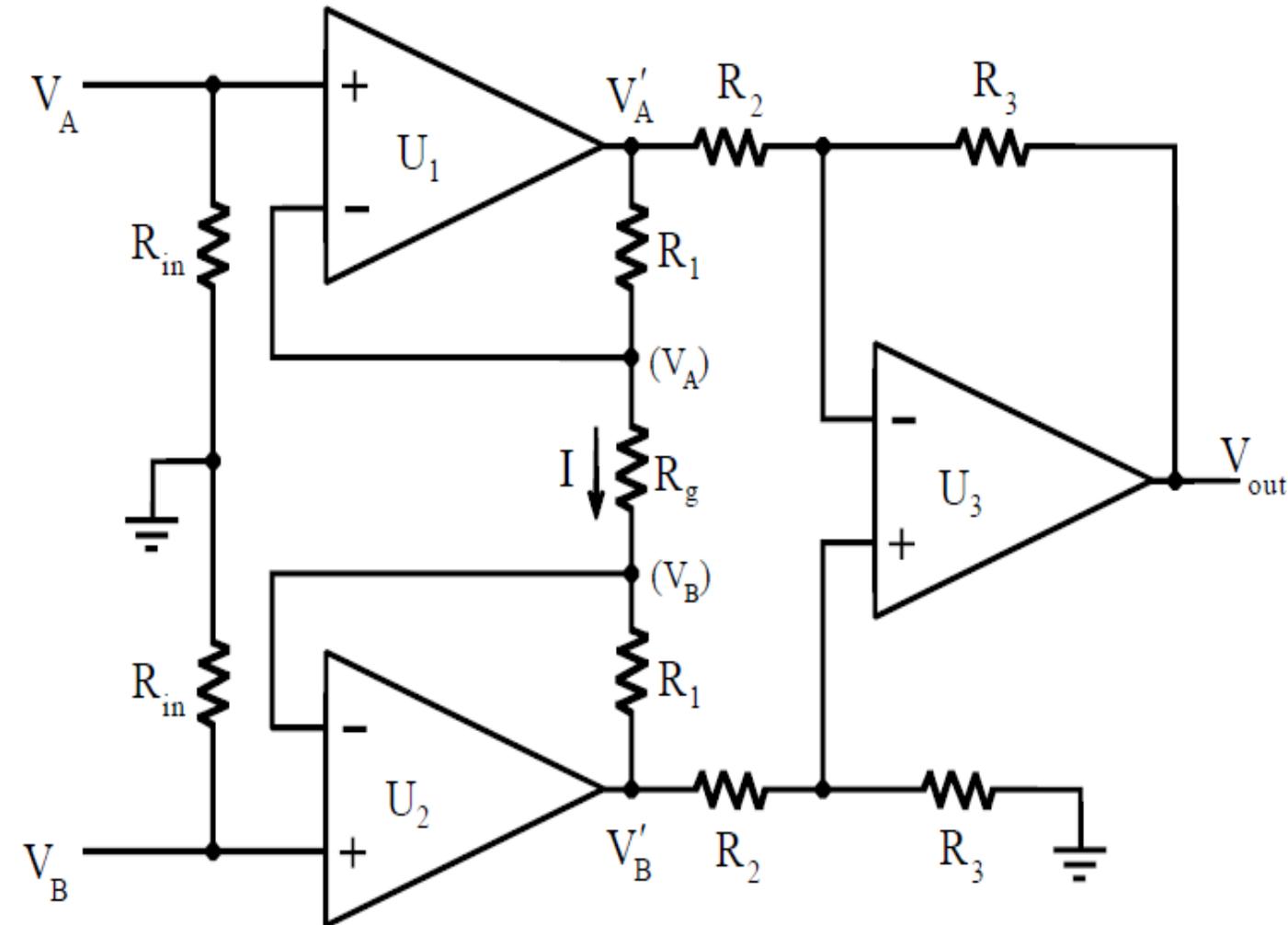


Electronic Circuits

Lecture 8.3: Instrumentation Amplifiers (IAs)

Instrumentation Amplifier with 3 OPAMPs




$$V_{out} = \frac{R_3}{R_2} (V'_B - V'_A)$$

$$I = \frac{V'_A - V'_B}{2R_1 + R_g} = \frac{V_A - V_B}{R_g}$$

$$V'_A - V'_B = \frac{2R_1 - R_g}{R_g} (V_A - V_B)$$

$$V_{out} = \frac{R_3}{R_2} \left(1 + \frac{2R_1}{R_g} \right) (V_B - V_A)$$

AD625

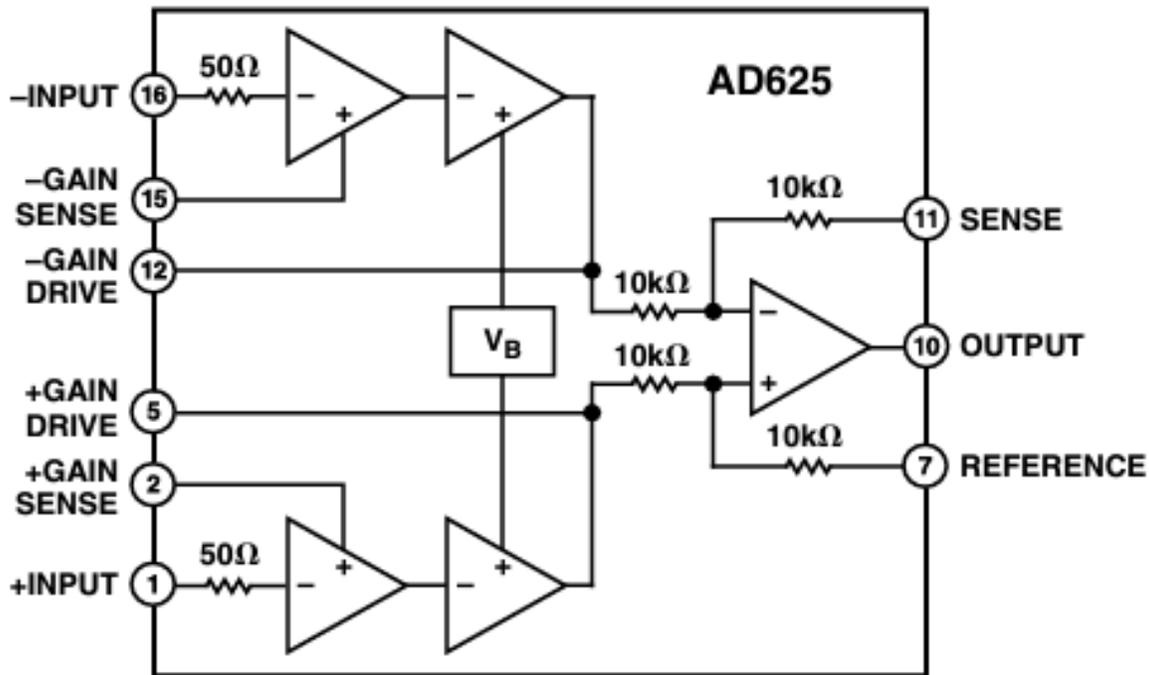

$$A_v = 2 \cdot R_f / R_g + 1$$

Where R_f are connected between Gain Sense and Gain Drive inputs

And R_g is connected between Gain Driver inputs

FEATURES

User Programmed Gains of 1 to 10,000

Low Gain Error: 0.02% Max

Low Gain TC: 5 ppm/°C Max

Low Nonlinearity: 0.001% Max

Low Offset Voltage: 25 μ V

Low Noise 4 nV/ $\sqrt{\text{Hz}}$ (at 1 kHz) RTI

Gain Bandwidth Product: 25 MHz

16-Lead Ceramic or Plastic DIP Package,

20-Terminal LCC Package

Standard Military Drawing Available


MIL-Standard Parts Available

Low Cost

* Sense and Output are short-circuit

* Reference is connected to GND

INA12x

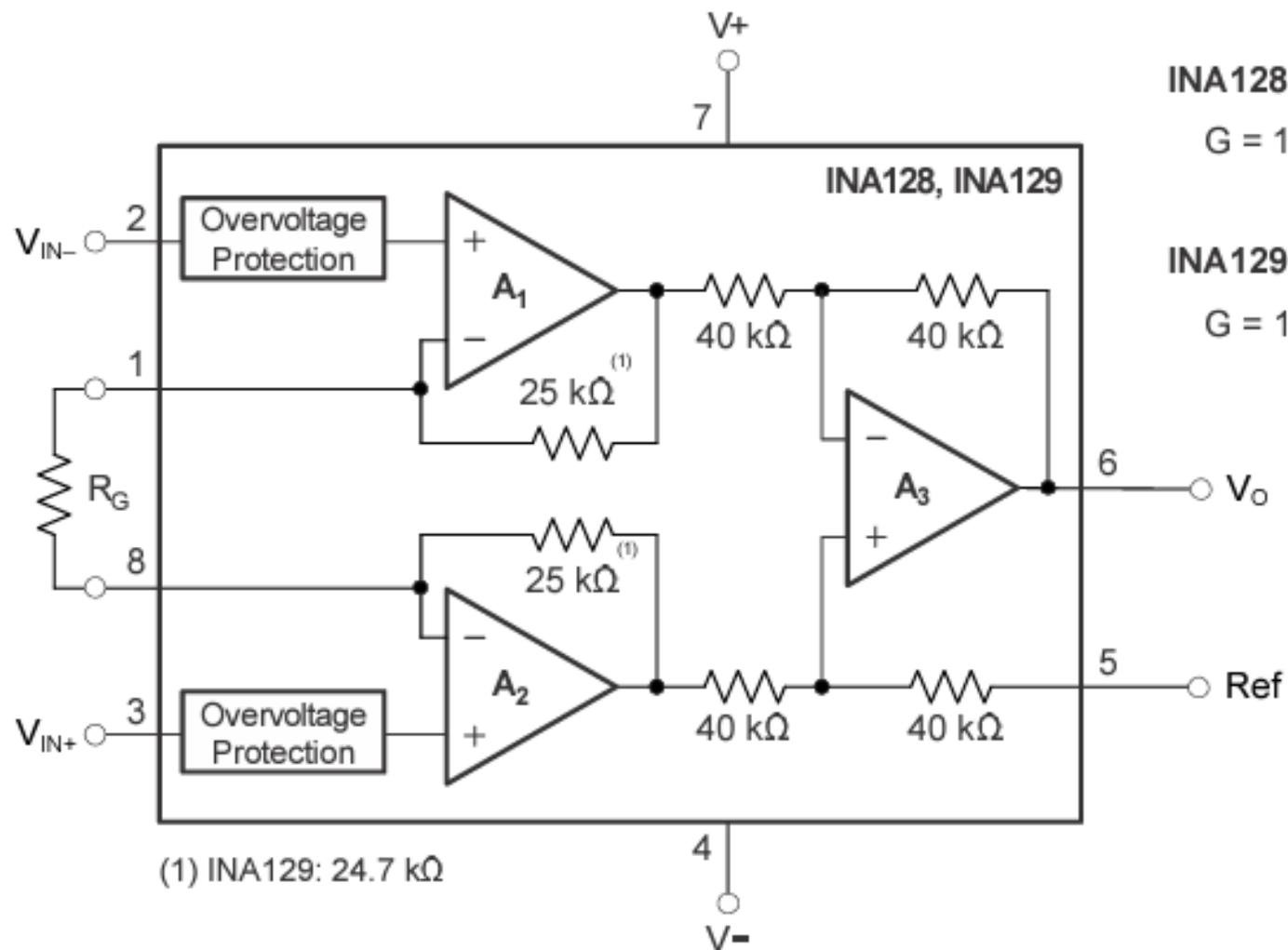

INA128:

$$G = 1 + \frac{50 \text{ k}\Omega}{R_G}$$

INA129:

$$G = 1 + \frac{49.4 \text{ k}\Omega}{R_G}$$



Thanks for
listening 😊

YALÇIN İŞLER

Assoc. Prof.