

# Registers & Counters

BME208 – Logic Circuits

Yalçın İŞLER

[islerya@yahoo.com](mailto:islerya@yahoo.com)


<http://me.islerya.com>

# Registers

- Registers are clocked sequential circuits
- A register is a group of flip-flops
  - Each flip-flop capable of storing one bit of information
  - An n-bit register
    - consists of n flip-flops
    - capable of storing n bits of information
  - besides flip-flops, a register usually contains combinational logic to perform some simple tasks
  - In summary
    - flip-flops to hold information
    - combinational logic to control the state transition
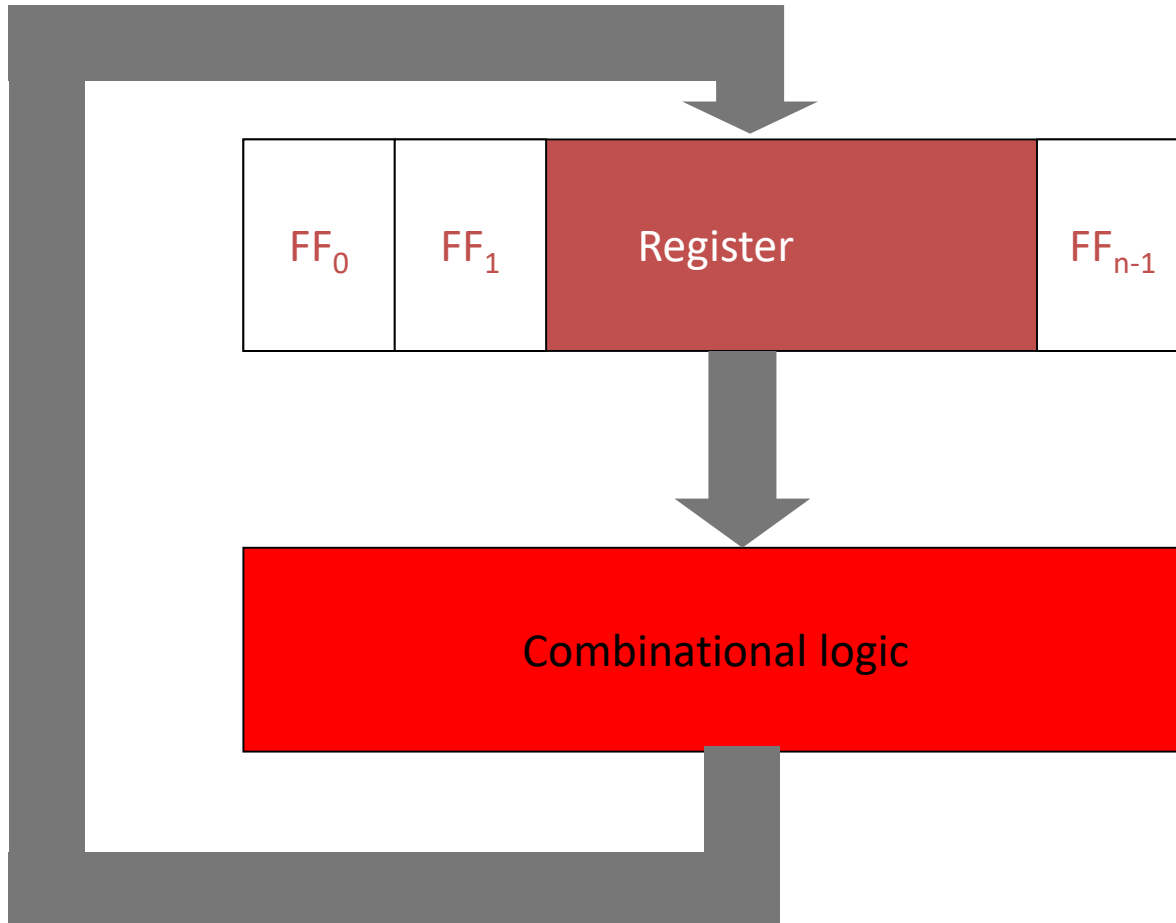
# Counters




- A counter is essentially a register that goes through a predetermined sequence of states
- “Counting sequence”



# Uses of Registers and Counters

- Registers are useful for storing and manipulating information
  - internal registers in microprocessors to manipulate data
- Counters are extensively used in control logic
  - PC (program counter) in microprocessors


# 4-bit Register

  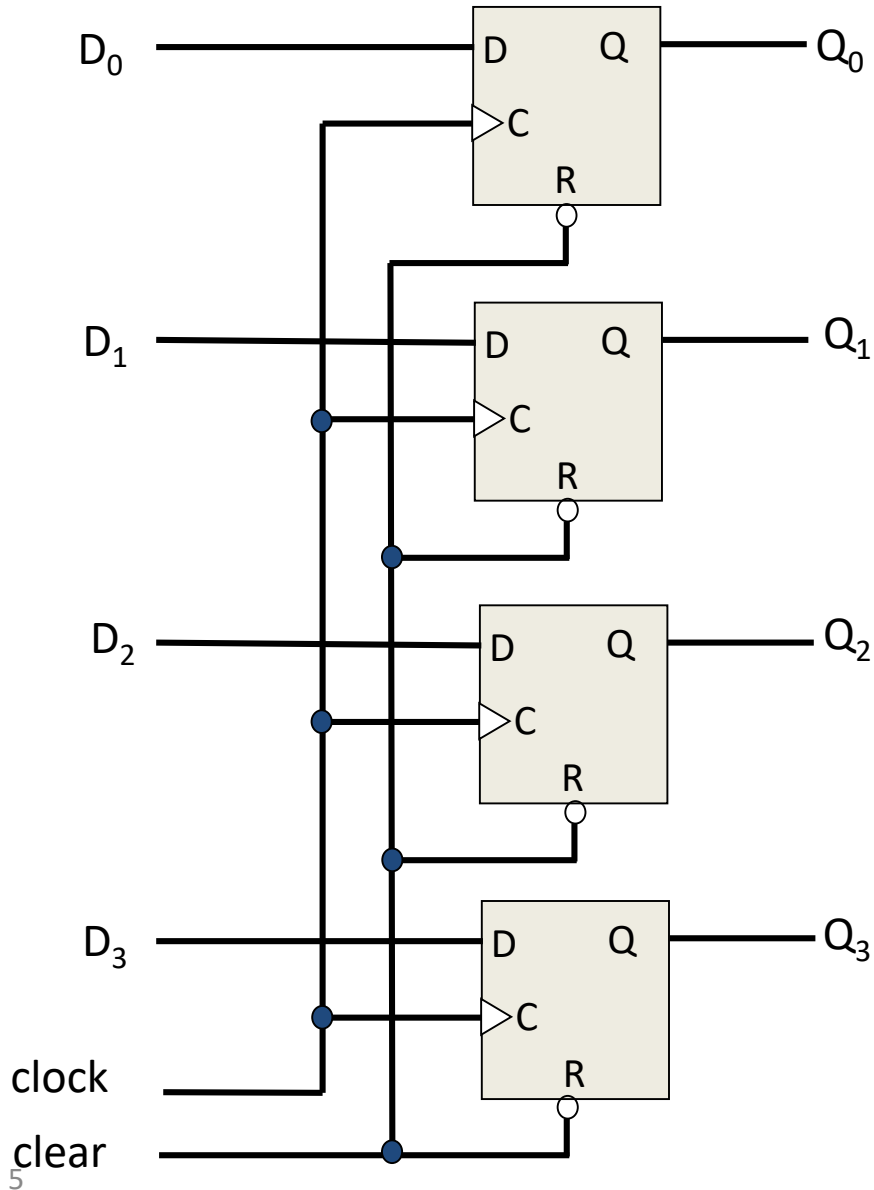



# Verilog Code of FD16CE

```
always @ (posedge C or posedge CLR)
  begin
    if (CLR)
      Q <= 4'b0000;
    else
      begin
        if (CE)
          Q <= D;
      end
    end
  end
```

# Register with Parallel Load

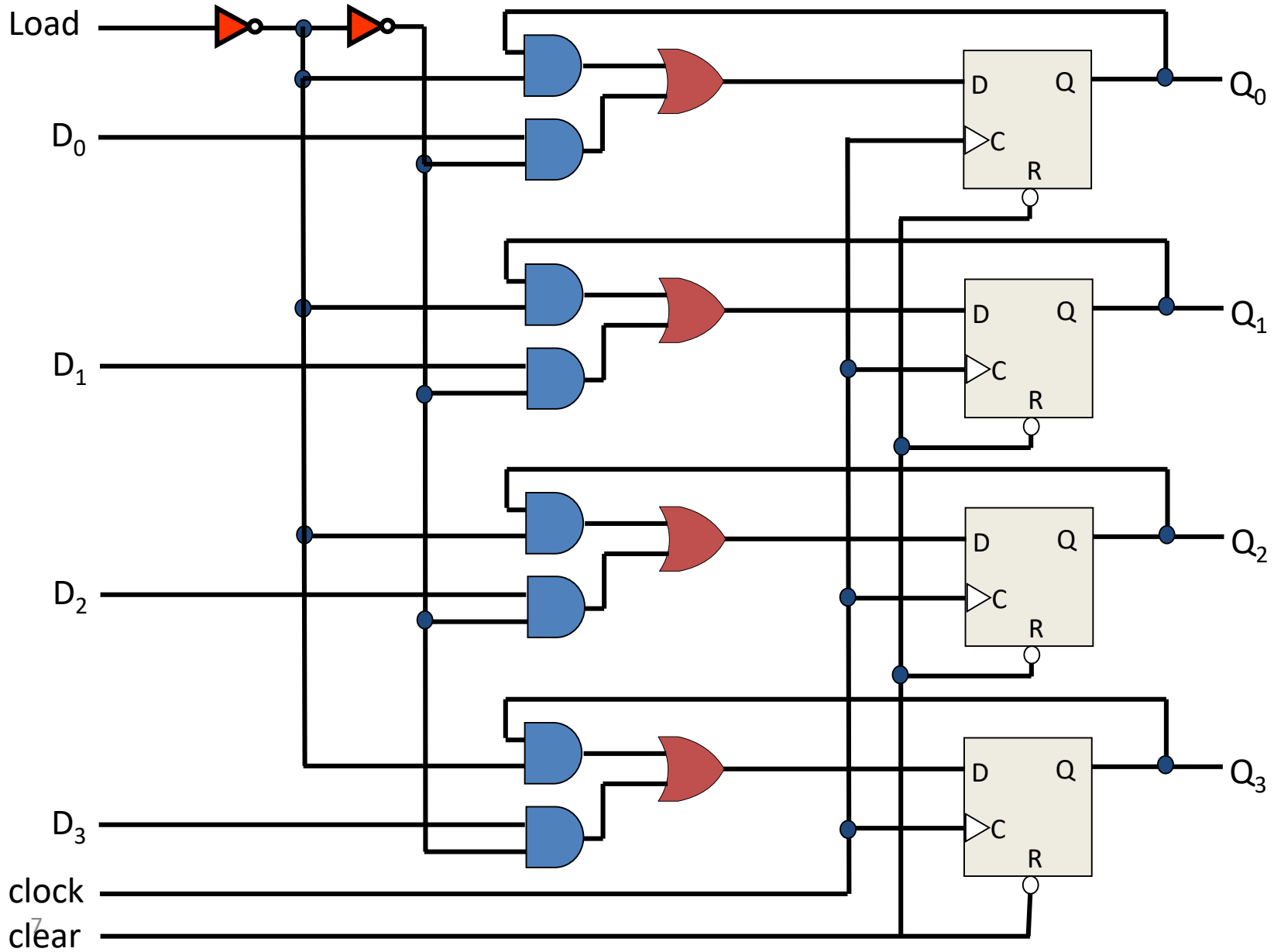


# Register Transfer 1/2

  




# Register Transfer 2/2

 

$$R_1 \leftarrow R_1 + R_2$$
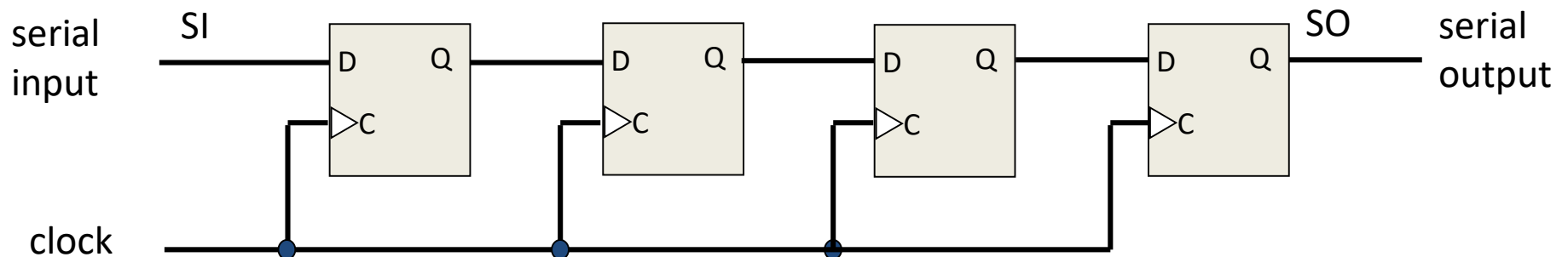
# Shift Registers


- A register capable of shifting its content in one or both directions
  - Flip-flops in cascade



- The current of n-bit shift register state can be transferred in n clock cycles
 
# Serial Mode

- A digital system is said to operate in serial mode when information is transferred and manipulated one bit a time.





$B \leftarrow A$

# Serial Transfer


- Suppose we have two 4-bit shift registers

Timing pulse	Shift register A				Shift register B			
initial value	1	0	1	1	0	0	1	0
After $T_1$								
After $T_2$								
After $T_3$								
After $T_4$	1	0	1	1	1	0	1	1

  

 
# Serial Addition

- In digital computers, operations are usually executed in parallel, since it is faster
- Serial mode is sometimes preferred since it requires less equipment



# Example: Serial Addition


- A and B are 2-bit shift registers

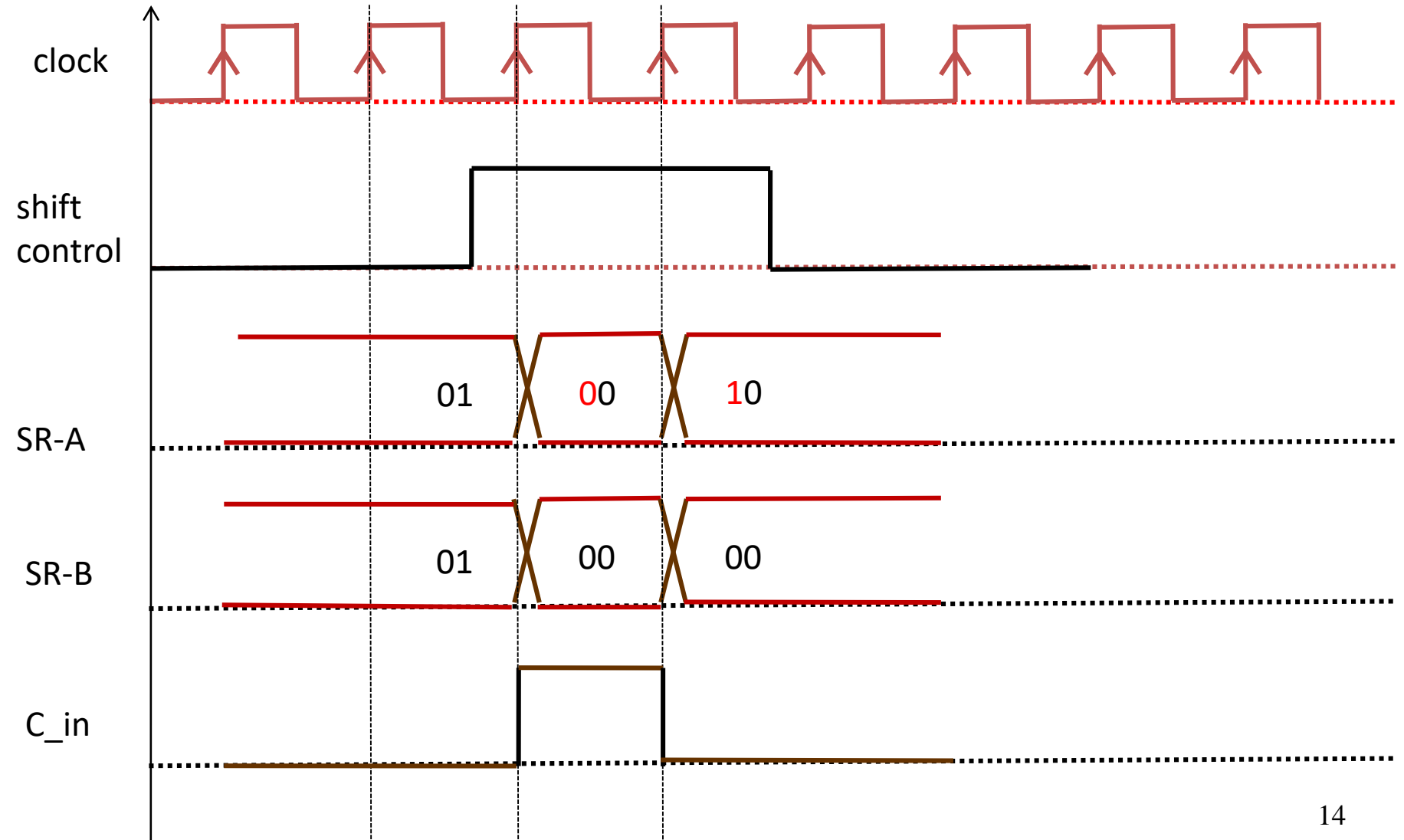

# Universal Shift Register

- Capabilities:
  1. A “clear” control to set the register to 0.
  2. A “clock” input
  3. A “shift-right” control
  4. A “shift-left” control
  5. n input lines & a “parallel-load” control
  6. n parallel output lines

# 4-Bit Universal Shift Register

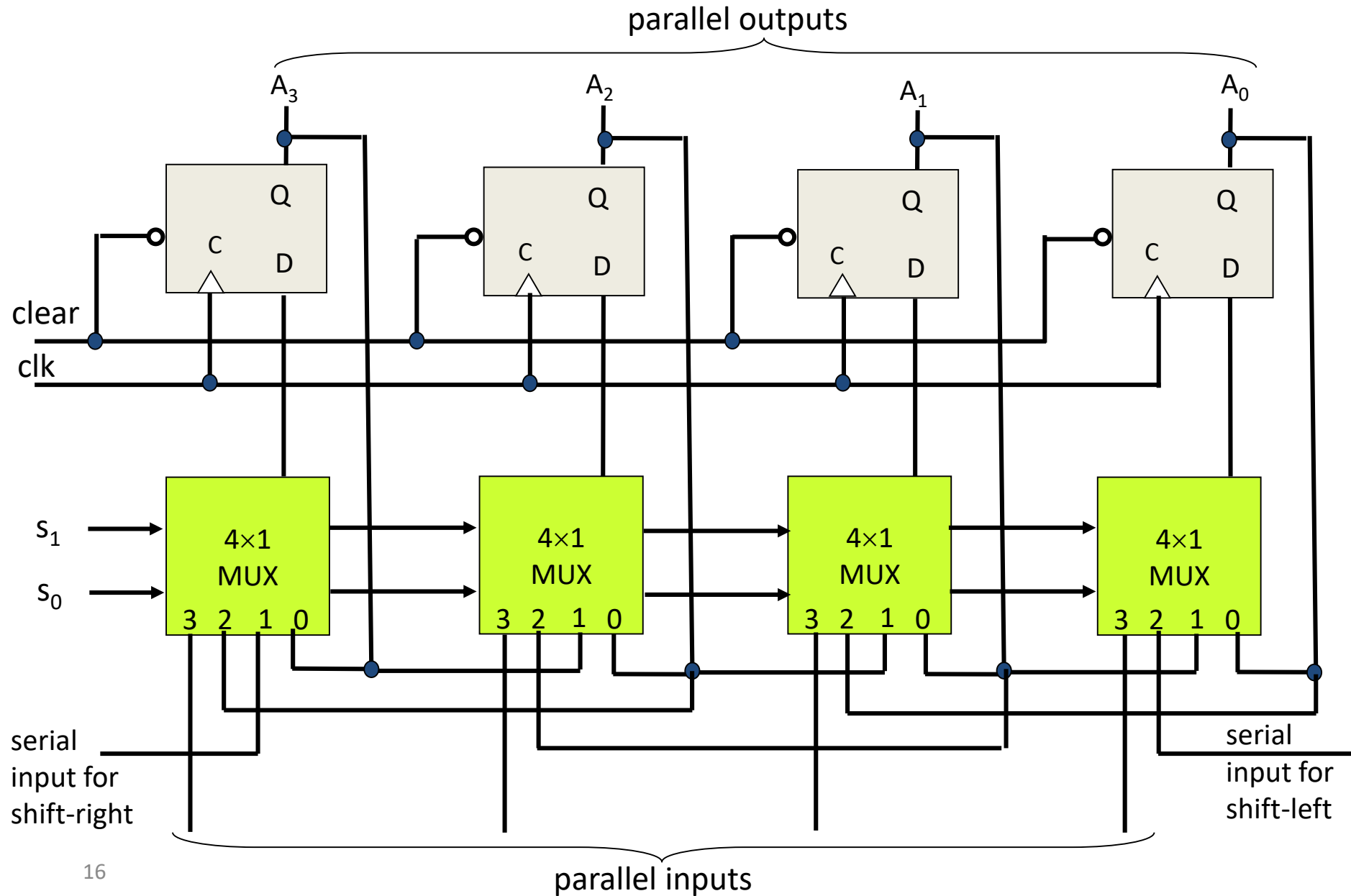



# Verilog Code – v1

```
// Behavioral description of a 4-bit universal shift register
// Fig. 6.7 and Table 6.3
module Shift_Register_4_beh (           // V2001, 2005
output reg [3: 0] A_par,              // Register output
input [3: 0] I_par,                  // Parallel input
input s1, s0,                        // Select inputs
MSB_in, LSB_in,                       // Serial inputs
CLK, Clear_b                          // Clock and Clear
always @ ( posedge CLK, negedge Clear_b) // V2001, 2005
    if (Clear_b == 0) A_par <= 4'b0000;
    else
        case ({s1, s0})
            2'b00: A_par <= A_par;           // No change
            2'b01: A_par <= {MSB_in, A_par[3: 1]}; // Shift right
            2'b10: A_par <= {A_par[2: 0], LSB_in}; // Shift left
            2'b11: A_par <= I_par;          // Parallel load of input
        endcase
endmodule
```

# Verilog Code – v2

```
// Behavioral description of a 4-bit universal shift register
// Fig. 6.7 and Table 6.3
module Shift_Register_4_beh (           // V2001, 2005
output reg [3: 0] A_par,              // Register output
input [3: 0] I_par,                  // Parallel input
input s1, s0,                        // Select inputs
MSB_in, LSB_in,                       // Serial inputs
CLK, Clear_b                          // Clock and Clear
always @ ( posedge CLK, negedge Clear_b) // V2001, 2005
    if (Clear_b == 0) A_par <= 4'b0000;
    else
        case ({s1, s0})
            // 2'b00: A_par <= A_par; // No change
            2'b01: A_par <= {MSB_in, A_par [3: 1]}; // Shift right
            2'b10: A_par <= {A_par [2: 0], LSB_in}; // Shift left
            2'b11: A_par <= I_par; // Parallel load of input
        endcase
endmodule
```

# Universal Shift Register

Mode Control		Register operation
$s_1$	$s_0$	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

# Counters

- registers that go through a prescribed sequence of states upon the application of input pulses
  - input pulses are usually clock pulses
- Example: n-bit binary counter
  - count in binary from 0 to  $2^n-1$
- Classification
  1. Synchronous counters
    - flip-flops receive the same common clock as *the* pulse
  2. Ripple counters
    - flip-flop output transition serves as *the* pulse to trigger other flip-flops


# Binary Ripple Counter

3-bit binary ripple counter


0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
0	0	0	0

- Idea:
  - to connect the output of one flip-flop to the C input of the next high-order flip-flop
- We need “complementing” flip-flops
  - We can use T flip-flops to obtain complementing flip-flops or
  - JK flip-flops with its inputs are tied together or
  - D flip-flops with complement output connected to the D input.


# 4-bit Binary Ripple Counter

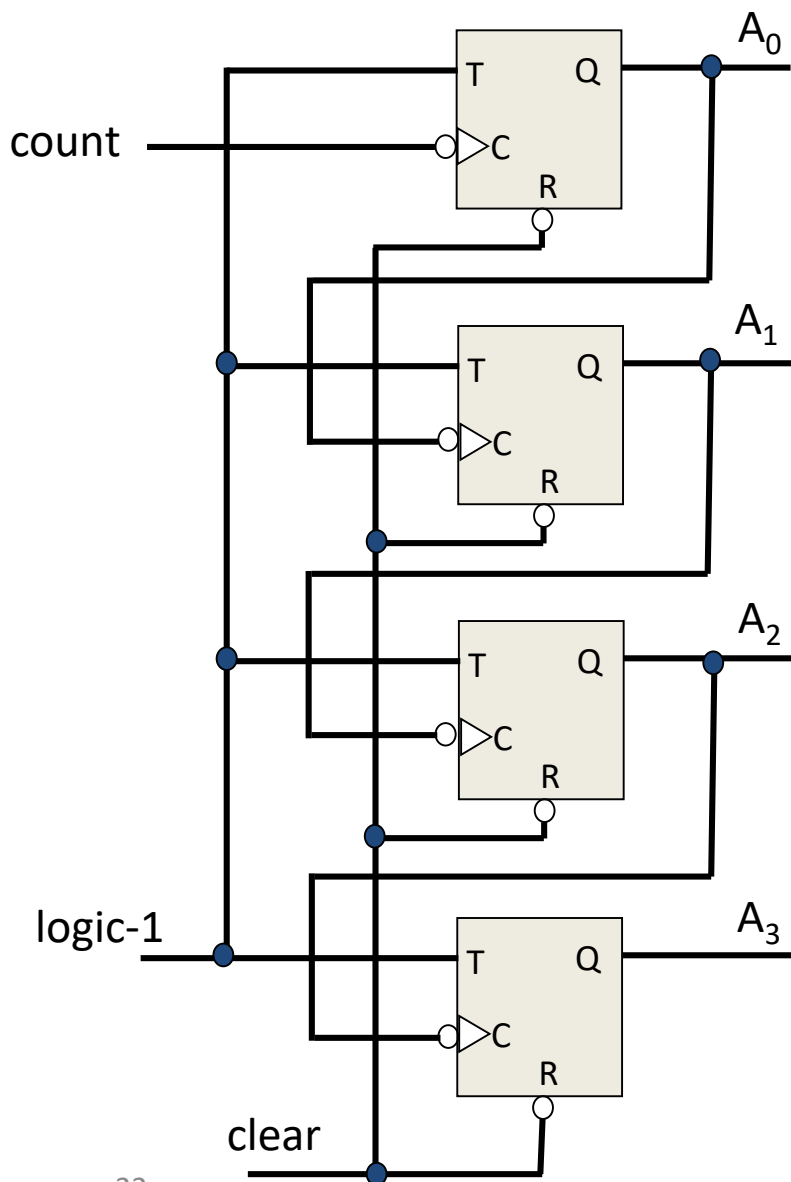

0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1
0	0	0	0	0

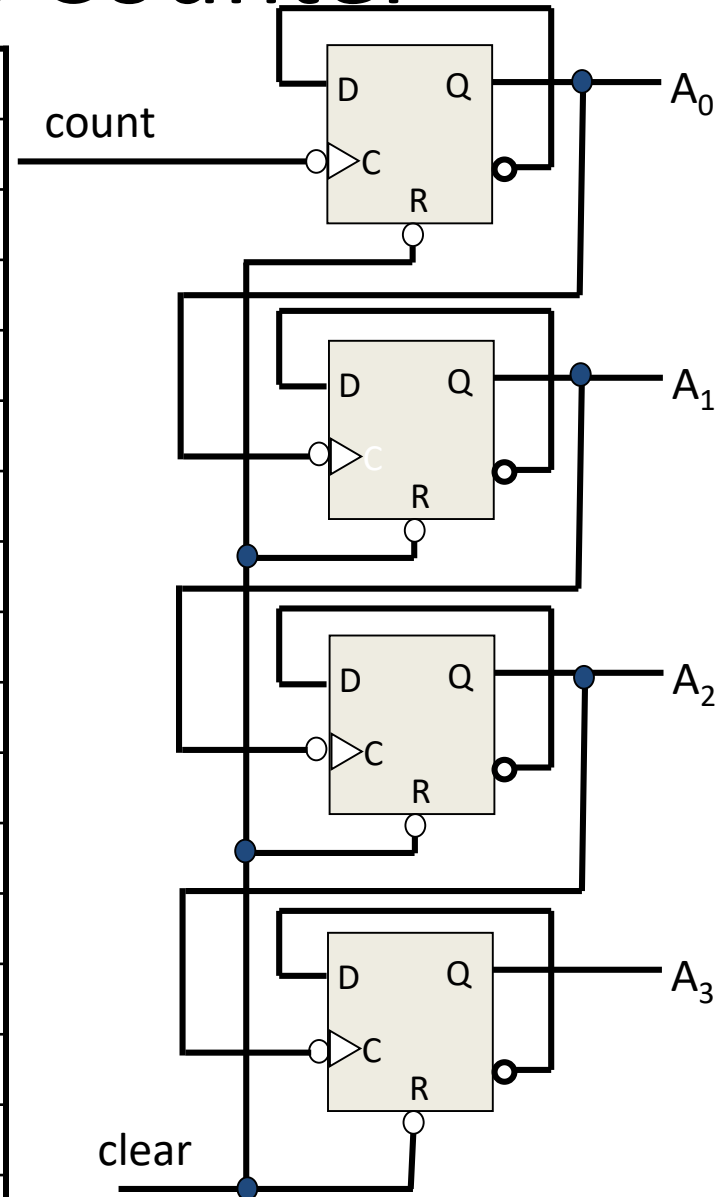

# 4-bit Binary Ripple Counter

 


# Synchronous Counters

- There is a common clock
  - that triggers all flip-flops simultaneously
  - If  $T = 0$  or  $J = K = 0$  the flip-flop does not change state.
  - If  $T = 1$  or  $J = K = 1$  the flip-flop does change state.
- Design procedure is so simple
  - no need for going through sequential logic design process
  - $A_0$  is always complemented
  - $A_1$  is complemented when  $A_0 = 1$
  - $A_2$  is complemented when  $A_0 = 1$  and  $A_1 = 1$
  - so on


0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
0	0	0	0




# 4-bit Binary Synchronous Counter

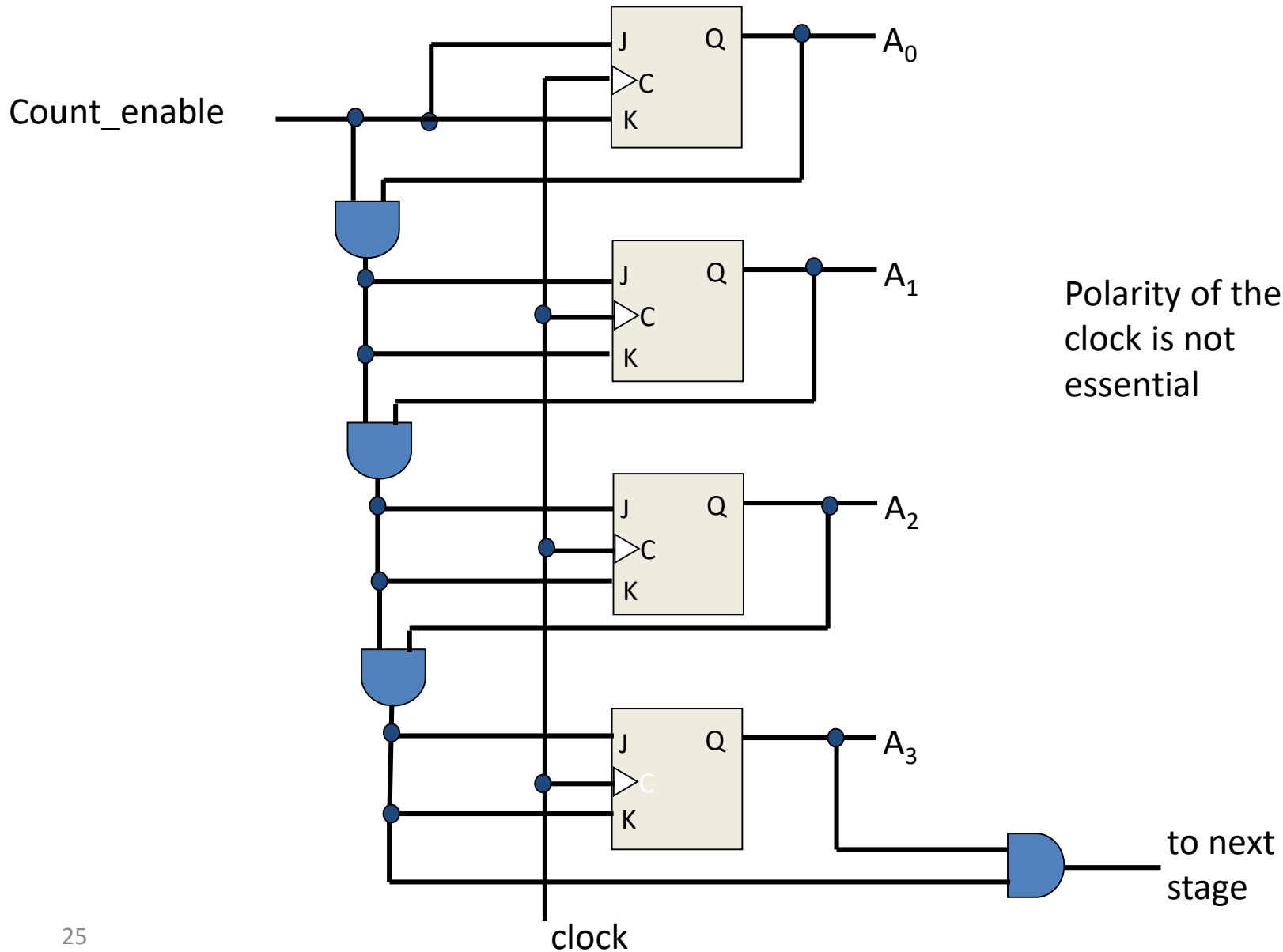

# Timing of Synchronous Counters

 

# Timing of Ripple Counters

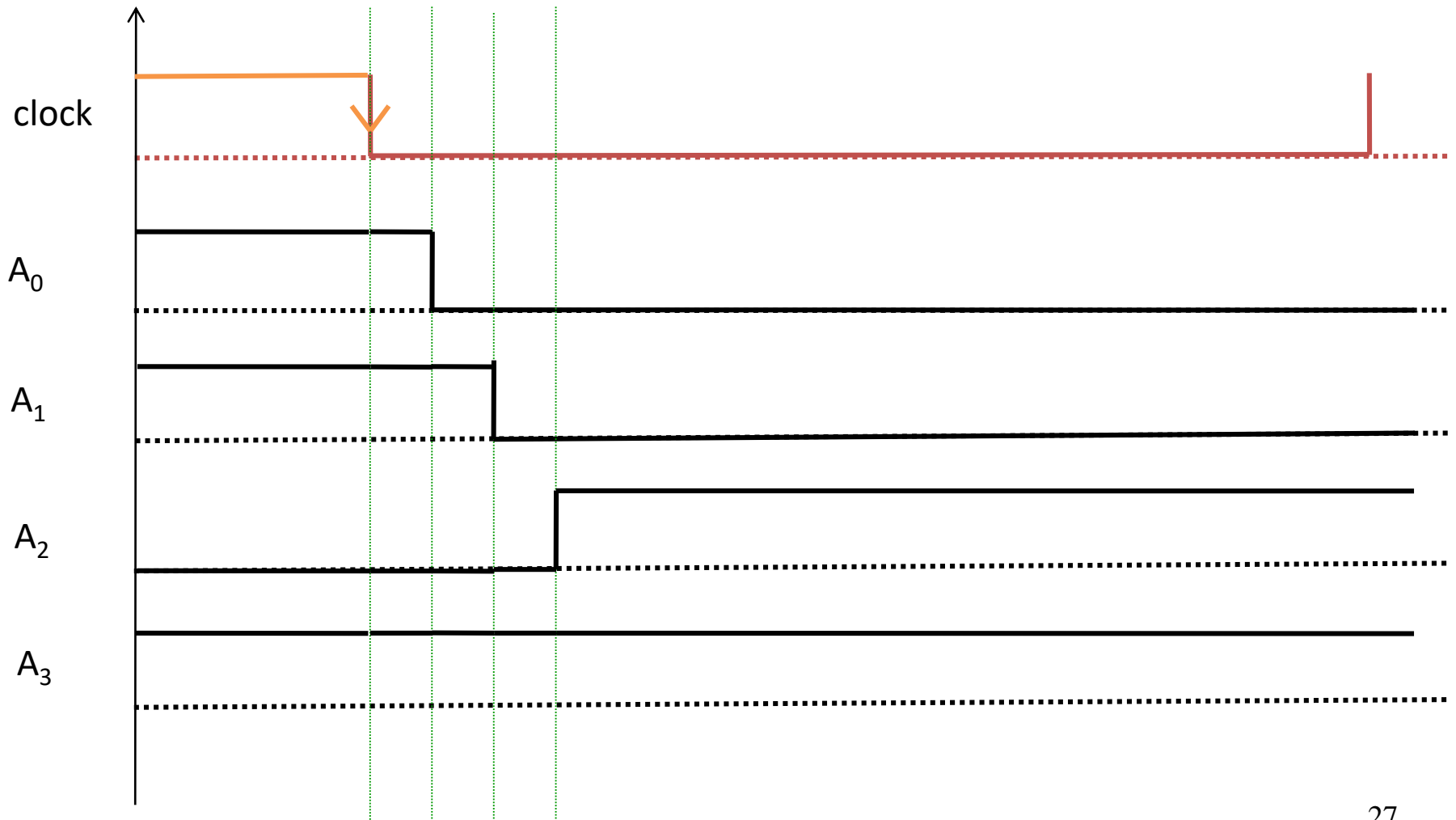


# Up-Down Binary Counter

- When counting downward
  - the least significant bit is always complemented (with each clock pulse)
  - A bit in any other position is complemented if all lower significant bits are equal to 0.
  - For example:                    **0 1 0 0**
    - Next state:
  - For example:                    **1 1 0 0**
    - Next state:


0	0 0 0
7	1 1 1
6	1 1 0
5	1 0 1
4	1 0 0
3	0 1 1
2	0 1 0
1	0 0 1
0	0 0 0

# Up-Down Binary Counter

 

- The circuit

# Binary Counter with Parallel Load

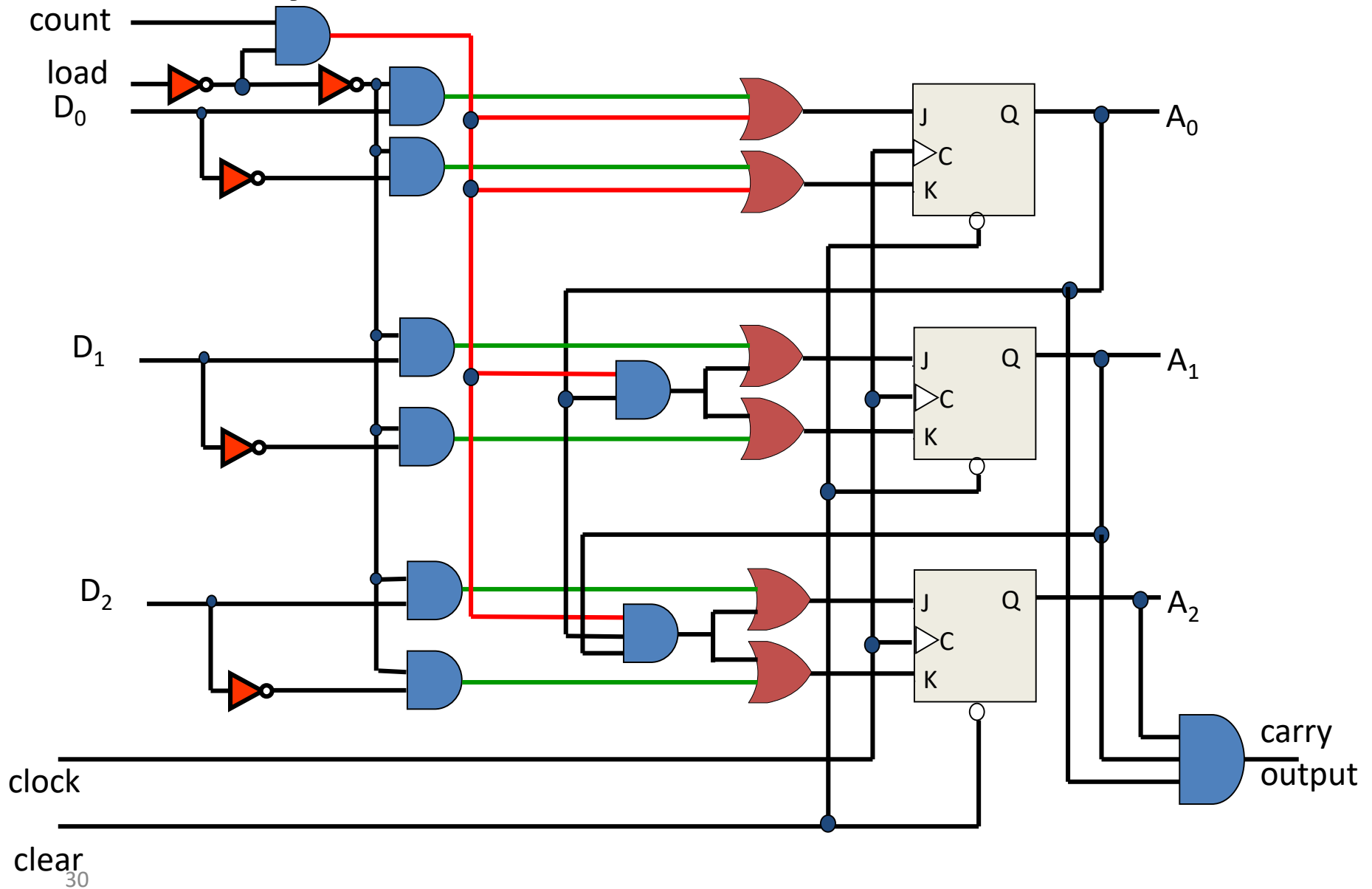


# Binary Counter with Parallel Load

Function Table

clear	clock	load	Count	Function
0	X	X	X	clear to 0
1	↑	1	X	load inputs
1	↑	0	1	count up
1	↑	0	0	no change
 
# Other Counters

- Ring Counter
  - A ring counter is a circular shift register with only one flip-flop being set at any particular time, all others are cleared.




- Usage
  - Timing signals control the sequence of operations in a digital system




# Ring Counter

- Sequence of timing signals

 
 
# Ring Counter

- To generate  $2^n$  timing signals,
  - we need a shift register with ? flip-flops
- or, we can construct the ring counter with a binary counter and a decoder



## Cost:


- 2 flip-flops
- 2-to-4 line decoder

## Cost in general case:

- n flip-flops
- n-to- $2^n$  line decoder
  - $2^n$  n-input AND gates
  - n NOT gates
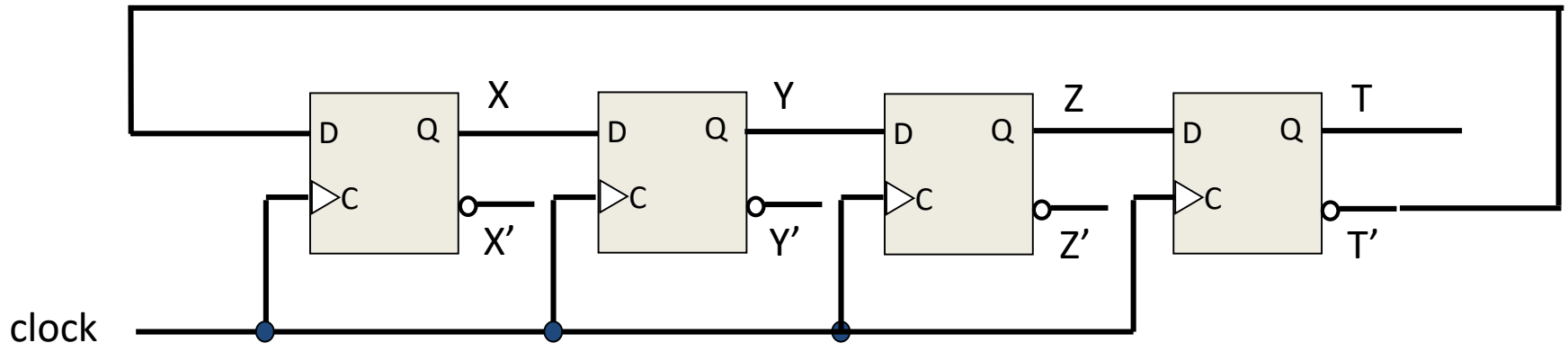
# Johnson Counter

- A k-bit ring counter can generate k distinguishable states
- The number of states can be doubled if the shift register is connected as a switch-tail ring counter




# Johnson Counter

- Count sequence and required decoding

sequence number	Flip-flop outputs				Output
	X	Y	Z	T	
1	0	0	0	0	$S_0 = X'T'$
2	1	0	0	0	$S_1 = XY'$
3	1	1	0	0	$S_2 = YZ'$
4	1	1	1	0	$S_3 = ZT'$
5	1	1	1	1	$S_4 = XT$
6	0	1	1	1	$S_5 = X'Y$
7	0	0	1	1	$S_6 = Y'Z$
8	0	0	0	1	$S_7 = Z'T$



# Johnson Counter

- Decoding circuit

 


# Unused States in Counters

- 4-bit Johnson counter

  

# Correction

 

# Johnson Counter

Present State				Next State			
X	Y	Z	T	X	Y	Z	T
0	0	0	0	1	0	0	0
1	0	0	0	1	1	0	0
1	1	0	0	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	0	1	1	1
0	1	1	1	0	0	1	1
0	0	1	1	0	0	0	1
0	0	0	1	0	0	0	0
0	0	1	0	1	0	0	1
1	0	0	1	0	0	0	0
0	1	0	0	1	0	1	0
1	0	1	0	1	1	0	1
1	1	0	1	0	1	1	0
0	1	1	0	1	0	1	1
1	0	1	1	0	1	0	1
0	1	0	1	0	0	1	0



# K-Maps

		ZT			
		00	01	11	10
XY	00	1			1
	01	1			1
	11	1			1
	10	1			1

$$X(t+1) = T'$$

		ZT			
		00	01	11	10
XY	00				
	01				
	11	1	1	1	1
	10	1	0	1	1

$$Y(t+1) = XY + XZ + XT'$$

		ZT			
		00	01	11	10
XY	00				
	01	1	1	1	1
	11	1	1	1	1
	10				

$$Z(t+1) = Y$$

		ZT			
		00	01	11	10
XY	00			1	1
	01			1	1
	11			1	1
	10			1	1

$$T(t+1) = Z$$

# Unused States in Counters

- Remedy  $X(t+1) = T'$        $Y(t+1) = XY + XZ + XT'$   
 $Z(t+1) = Y$        $T(t+1) = Z$

